

# ECGR2181 Logic Design I Spring 2005: Lab 3

## Objective

Design a carry lookahead full-adder circuit using Verilog code and load the executable onto the Spartan-3 FPGA board.

## General Information

The general steps for this lab are:

1. Write the Verilog code for a 4-bit Carry look ahead Fulladder. Bring it to the lab session. The adder must be carry look ahead for any credit.
2. Follow the instruction manual to synthesize the Verilog for your designs.
3. Obtain a development board and programming cable.
4. Load the Spartan-3 Board on PCs in Smith 347. Follow the instruction manual to download the full-adder Spartan-3 board.
5. Build the project and load onto your board. Run the program and observe the operation.
6. Demonstrate for a TA.

## Laboratory Assignment Requirements

1. Create a new directory for Lab03. Save the Verilog files as *filename.vl* in the same directory.
2. The code is well commented and easy to follow.
3. The code (and board) demonstrates the truth tables shown below.
4. The design uses the switch and light assignments defined below.
4. Turn in a lab report with your Verilog code.


*Hint: Refer Page 434-435 on your book. Have the given circuit as your reference design.*

## Test data/process:

| Cin | X0 | X1 | X2 | X3 | Y0 | Y1 | Y2 | Y3 | S0 | S1 | S2 | S3 | Carry out |
|-----|----|----|----|----|----|----|----|----|----|----|----|----|-----------|
| 0   | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0         |
| 0   | 1  | 1  | 1  | 1  | 1  | 1  | 1  | 1  | 0  | 1  | 1  | 1  | 1         |
| 0   | 1  | 0  | 0  | 0  | 1  | 0  | 0  | 0  | 0  | 1  | 0  | 0  | 0         |
| 1   | 1  | 1  | 1  | 1  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 0  | 1         |
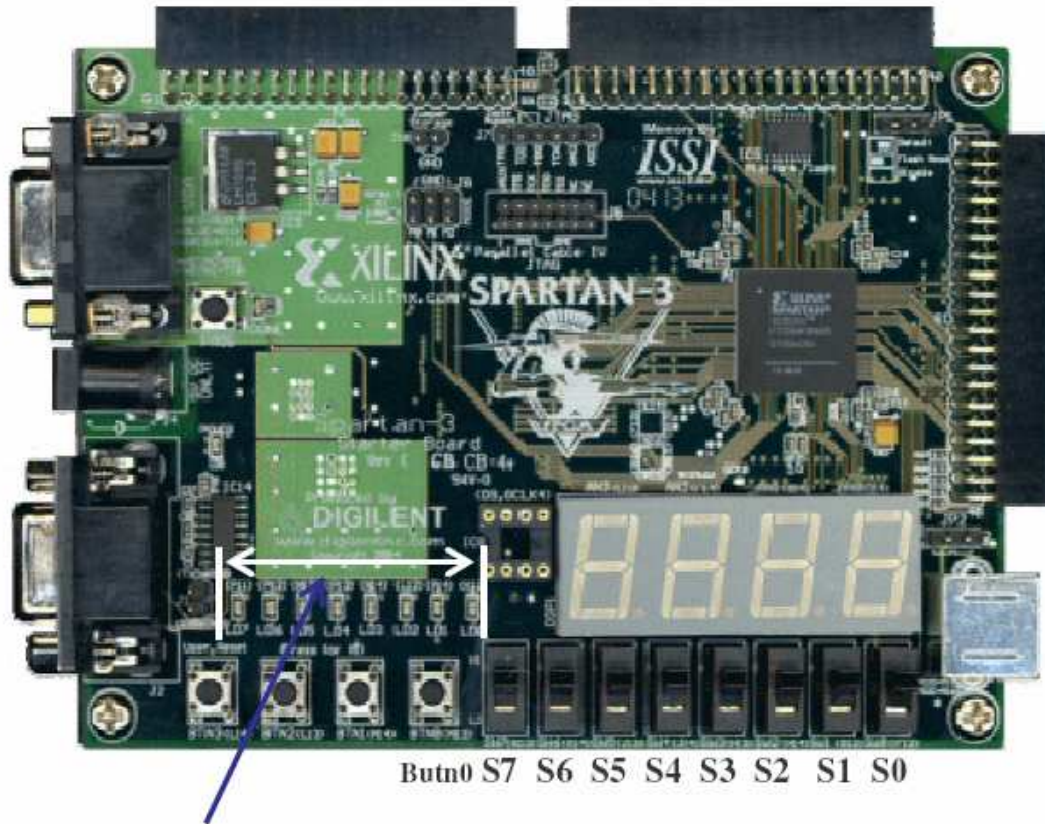
## Lab Report

Use the lab report format provided for the last lab. Write the one page report and include a hard copy of your Verilog code.



Butn0 S7 S6 S5 S4 S3 S2 S1 S0

L7 L6 L5 L4 L3 L2 L1 L0

|        |          |   |          |          |
|--------|----------|---|----------|----------|
| Input  | x0       | – | Switch 0 | Port f12 |
| Input  | x1       | – | Switch 1 | Port g12 |
| Input  | x2       | – | Switch 2 | Port h14 |
| Input  | x3       | – | Switch 3 | Port h13 |
| Input  | y0       | – | Switch 4 | Port j14 |
| Input  | y1       | – | Switch 5 | Port j13 |
| Input  | y2       | – | Switch 6 | Port k14 |
| Input  | y3       | – | Switch 7 | Port k13 |
| Input  | Carry-In | – | Button 0 | Port m13 |
| Output | Sum0     | – | LED0     | Port k12 |
| Output | Sum1     | – | LED1     | Port p14 |
| Output | Sum2     | – | LED2     | Port l12 |
| Output | Sum3     | – | LED3     | Port n14 |
| Output | Carry    | – | LED7     | Port p11 |