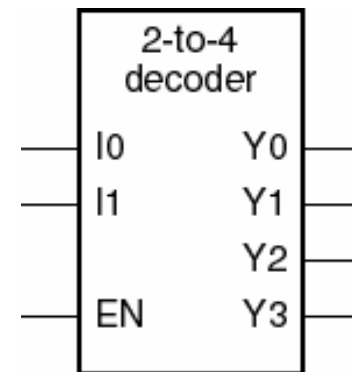


# Decoders and Encoders


ECGR2181



*Reading:* Chapter 5.4 and 5.5

# Decoders


## General decoder structure

 

Typically  $n$  inputs,  $2^n$  outputs

- 2-to-4, 3-to-8, 4-to-16, etc.


# Binary 2-to-4 decoder

 


<i>Inputs</i>			<i>Outputs</i>			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Note “x” (don’t care) notation.


# 2-to-4-decoder logic diagram

 

# Decoder Symbol


 


# MSI 2-to-4 decoder

 


Input buffering (less load)  
NAND gates (faster)

# Complete 74x139 Decoder

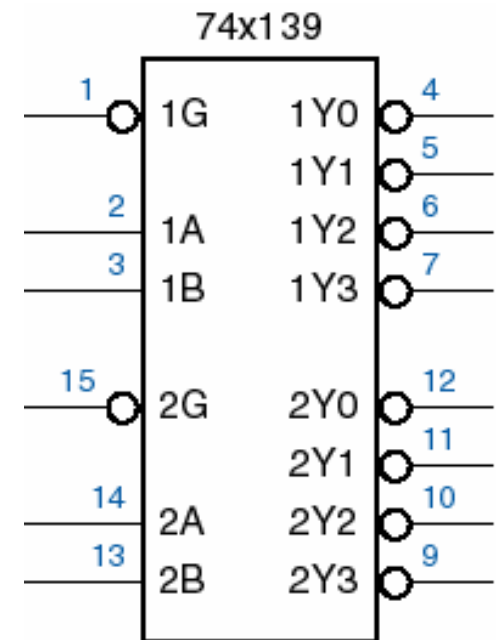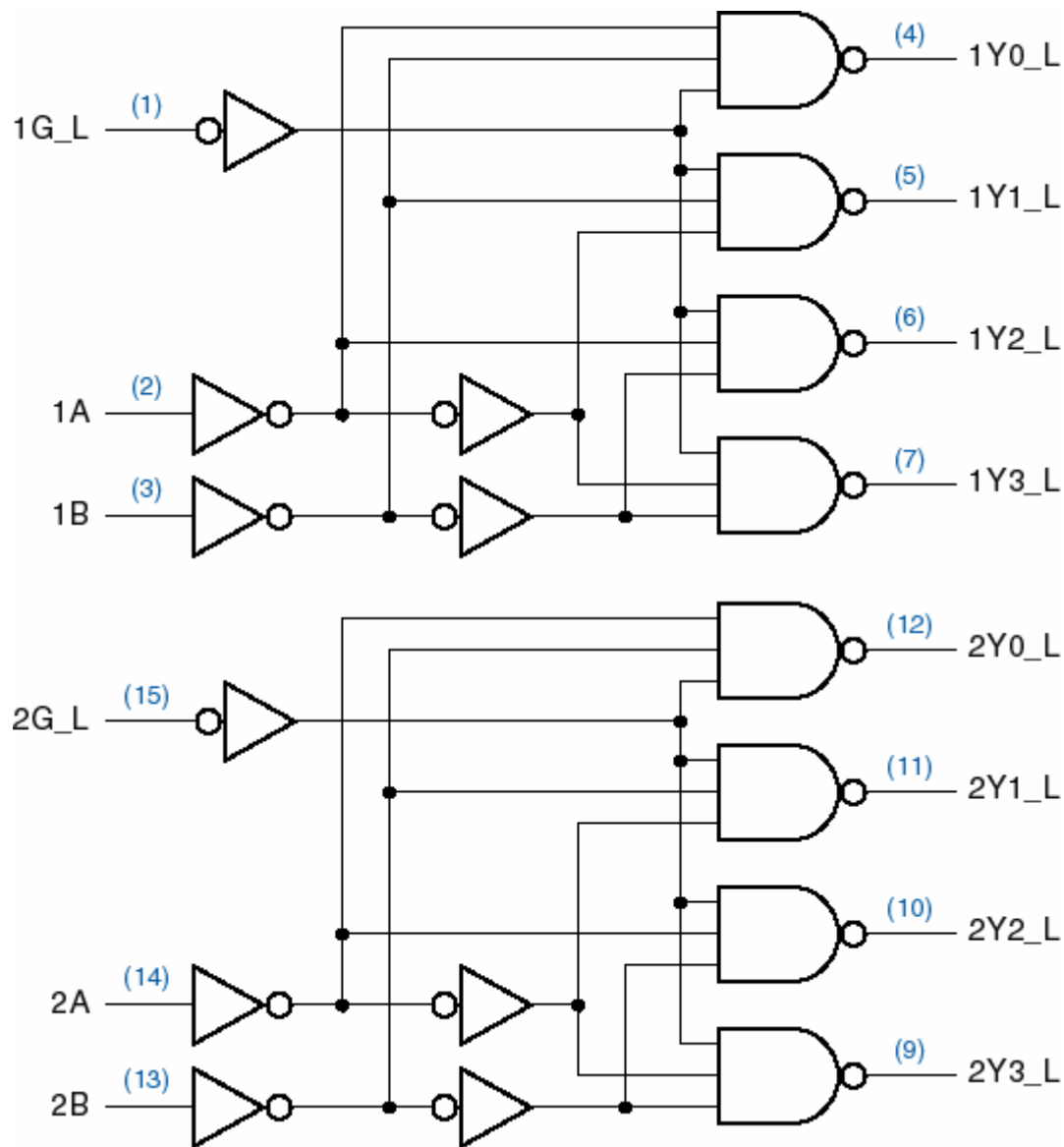


# 3-to-8 decoder

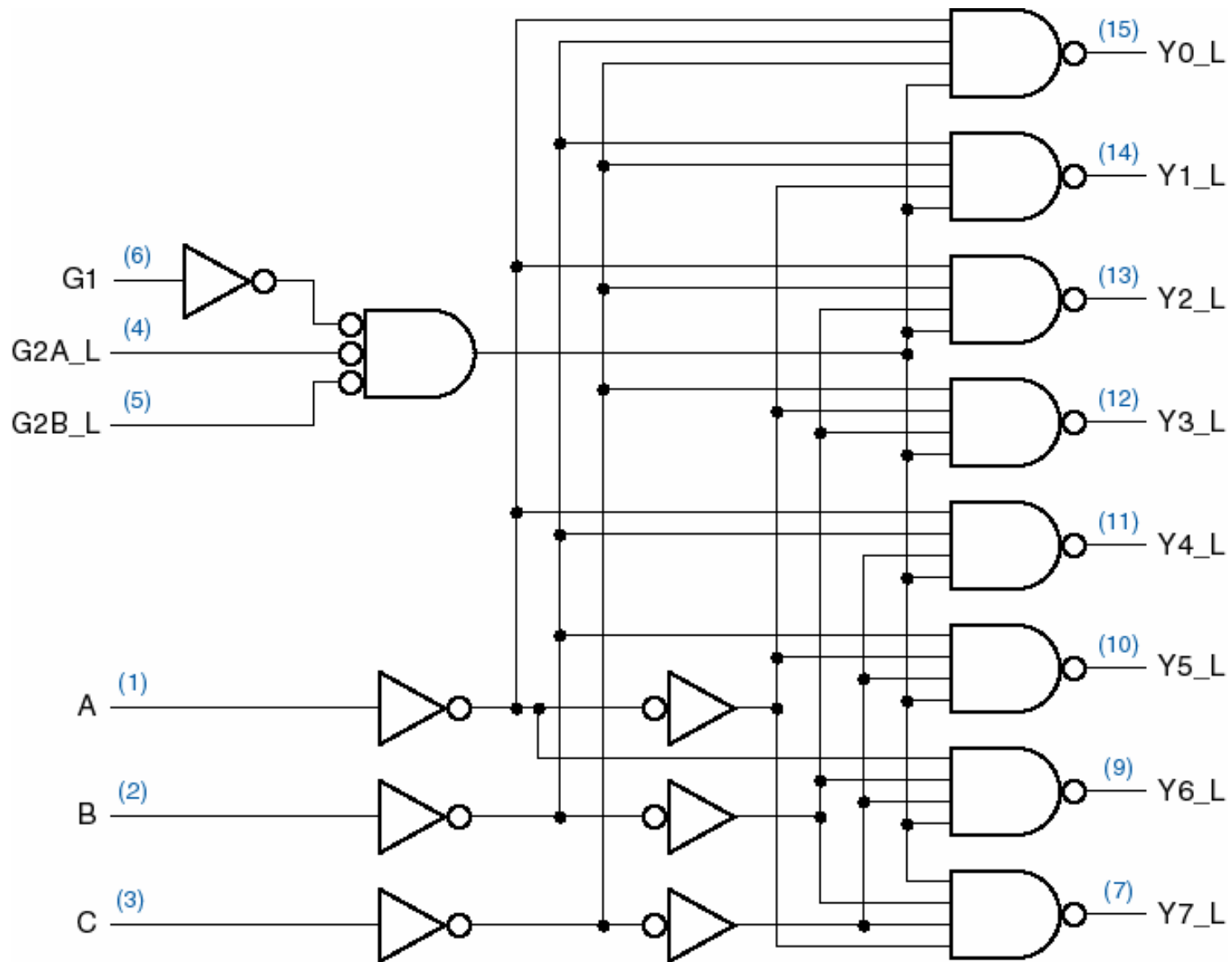




# 74x138 3-to-8-decoder symbol

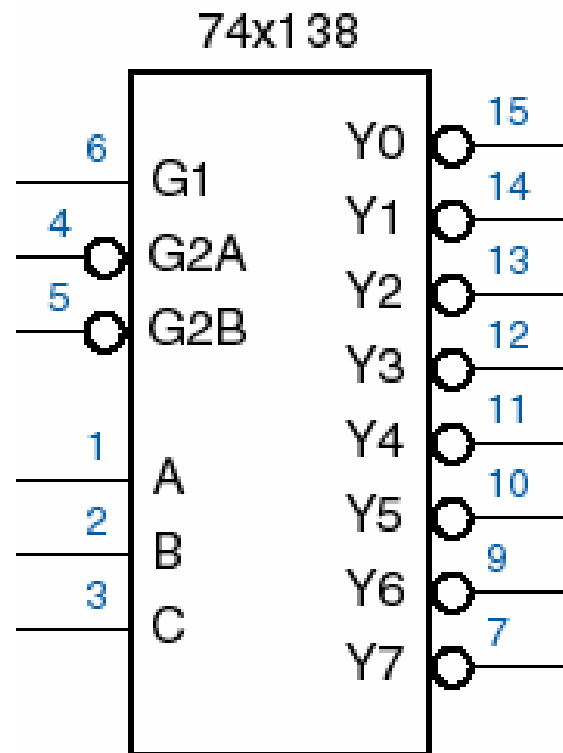


# Decoder cascading

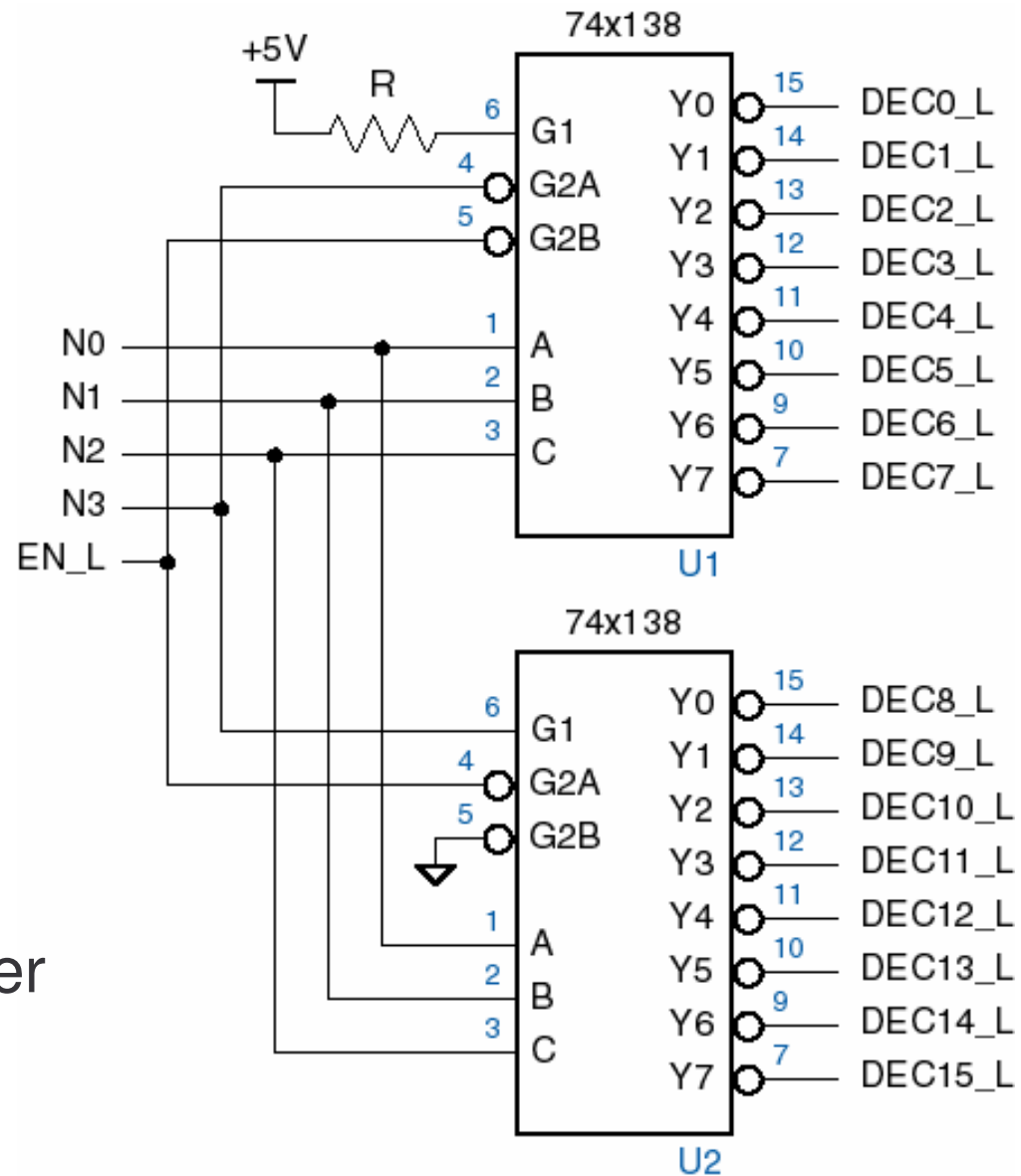

4-to-16 decoder

# More cascading

 

5-to-32 decoder

# Decoder applications

---

## Microprocessor memory systems

- selecting different banks of memory

## Microprocessor input/output systems

- selecting different devices

## Microprocessor instruction decoding



- enabling different functional units

## Memory chips



- enabling different rows of memory depending on address

# Encoders vs. Decoders


---

  


# Binary encoders

  

# Need priority in most applications

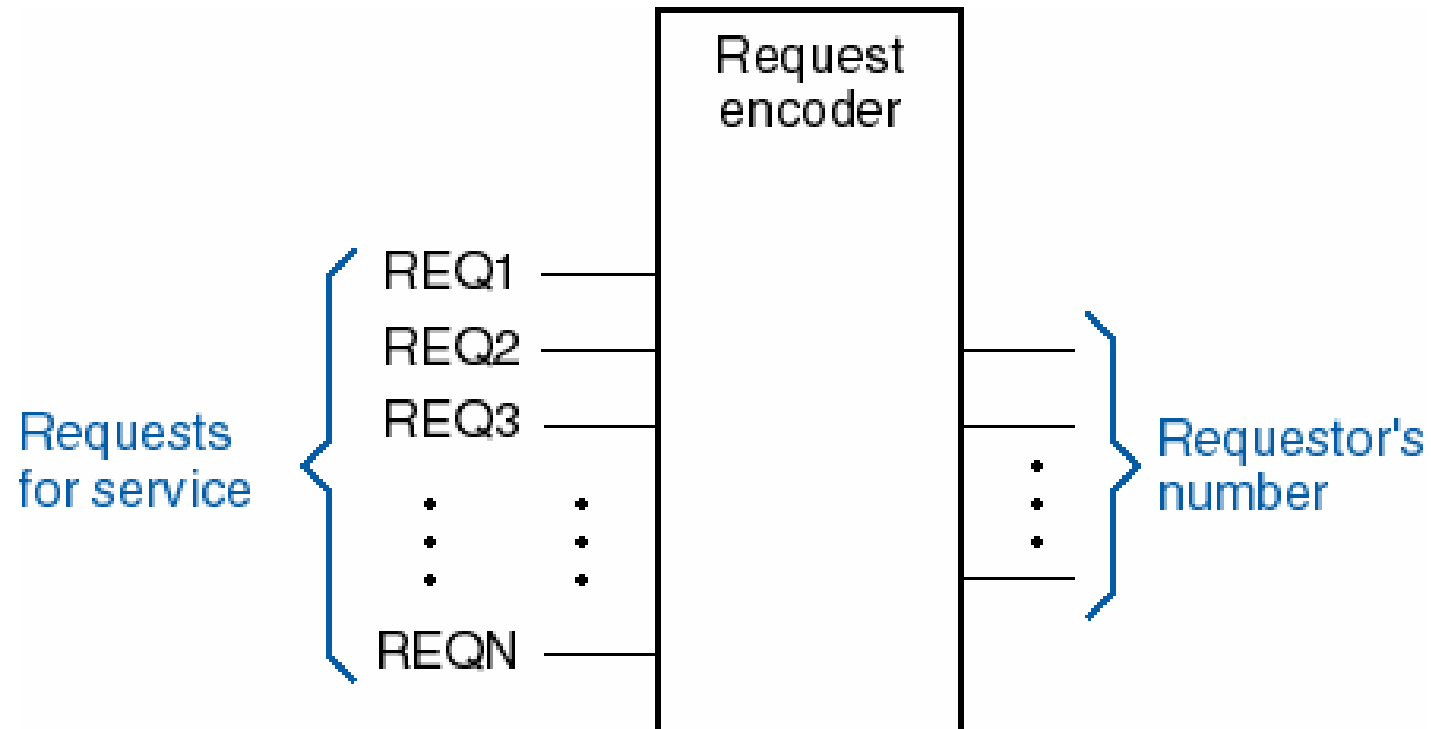

# 8-input priority encoder

 



# Priority-encoder logic equations

$$H7 = I7$$

$$H6 = I6 \cdot I7'$$

$$H5 = I5 \cdot I6' \cdot I7'$$

...

$$H0 = I0 \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$$

$$A2 = H4 + H5 + H6 + H7$$


$$A1 = H2 + H3 + H6 + H7$$

$$A0 = H1 + H3 + H5 + H7$$

$$\text{IDLE} = (I0 + I1 + I2 + I3 + I4 + I5 + I6 + I7)'$$


$$= I0' \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$$

# 74x148 8-input priority encoder

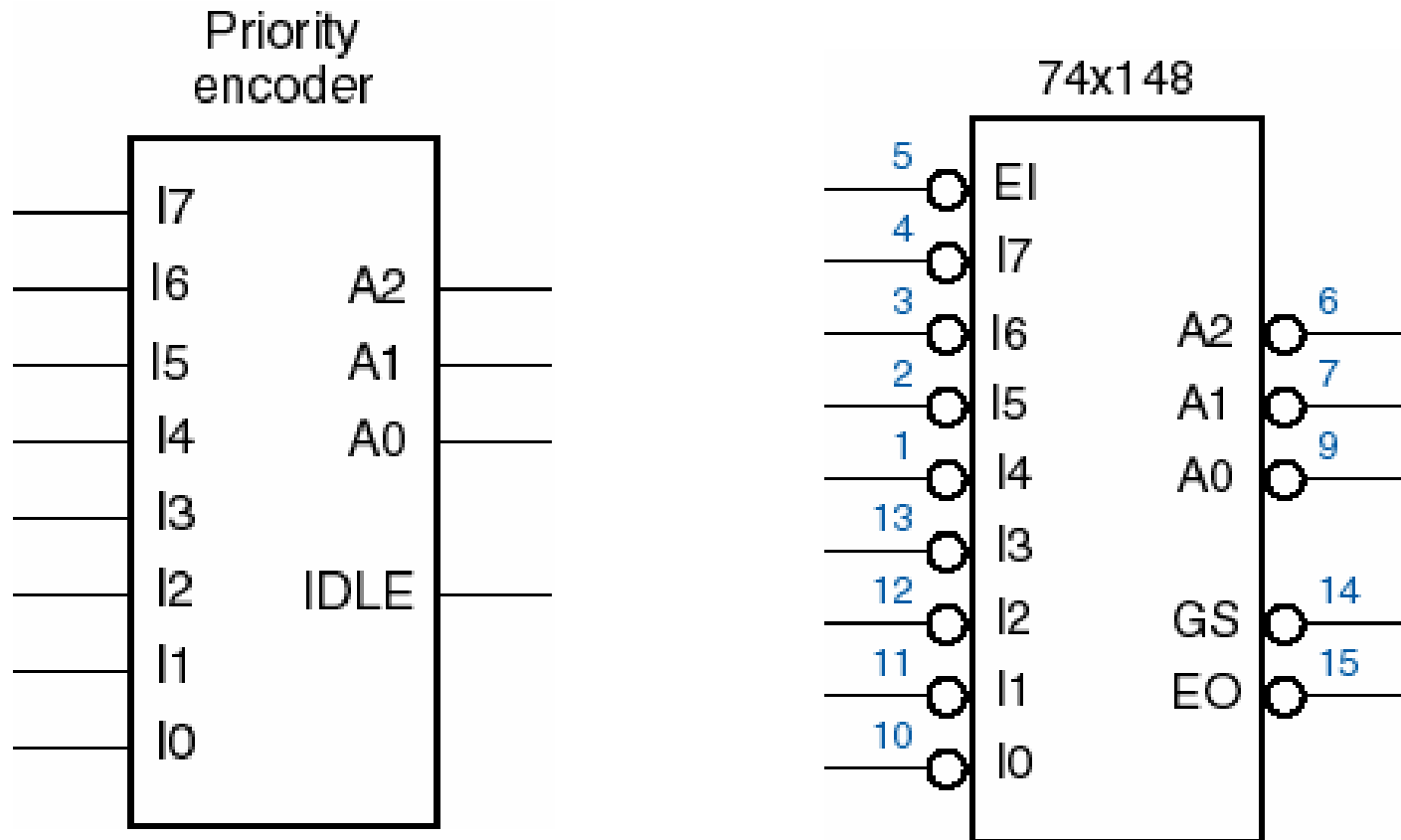

- Active-low I/O
- Enable Input
- “Got Something”
- Enable Output

# 74x148 circuit

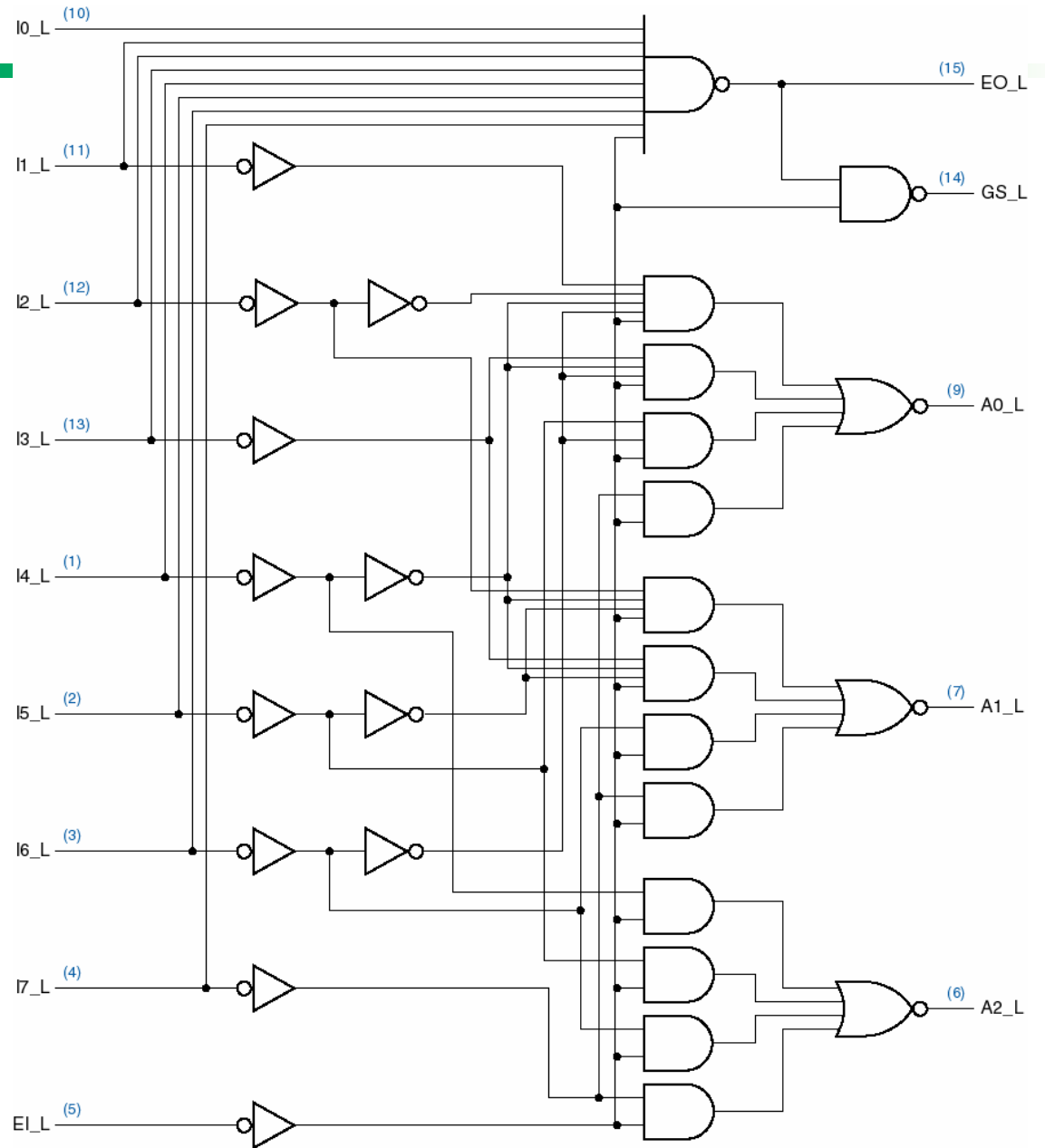

# 74x148 Truth Table

<i>Inputs</i>									<i>Outputs</i>				
E_L	I0_L	I1_L	I2_L	I3_L	I4_L	I5_L	I6_L	I7_L	A2_L	A1_L	A0_L	GS_L	EO_L
1	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	1	0	1
0	x	x	x	x	x	0	1	1	0	1	0	0	1
0	x	x	x	x	0	1	1	1	0	1	1	0	1
0	x	x	0	1	1	1	1	1	1	0	1	0	1
0	x	0	1	1	1	1	1	1	1	1	0	0	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	1	0

# Cascading priority encoders

## 32-input priority encoder

