 



# More Digital Design

ECGR2181

Reading: Chapter 5.1, 2, 3, 8, 10




# SHIFT-AND-ADD MULTIPLIER






 


Block Diagram

# Flat schematic structure

 

# Hierarchical schematic structure

 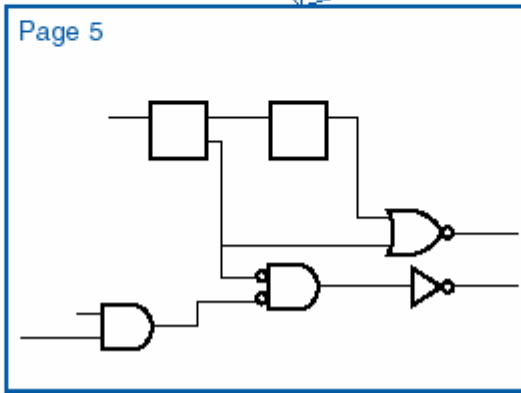  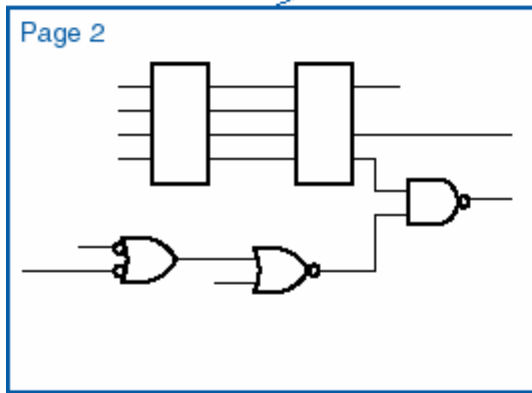 

# Other Documentation

---

## Timing diagrams

- Output from simulator
- Specialized timing-diagram drawing tools

## Circuit descriptions

- Text (word processing)
- Can be as big as a book
- Typically incorporate other elements (block diagrams, timing diagrams, etc.)

# Signal names and active levels


Signal names are chosen to be descriptive.


Active levels -- HIGH or LOW

- named condition or action occurs in either the HIGH or the LOW state, according to the active-level designation in the name.


<i>Active Low</i>	<i>Active High</i>
READY-	READY+
ERROR.L	ERROR.H
ADDR15(L)	ADDR15(H)
RESET*	RESET
ENABLE~	ENABLE
-GO	GO
/RECEIVE	RECEIVE
TRANSMIT_L	TRANSMIT

# Example


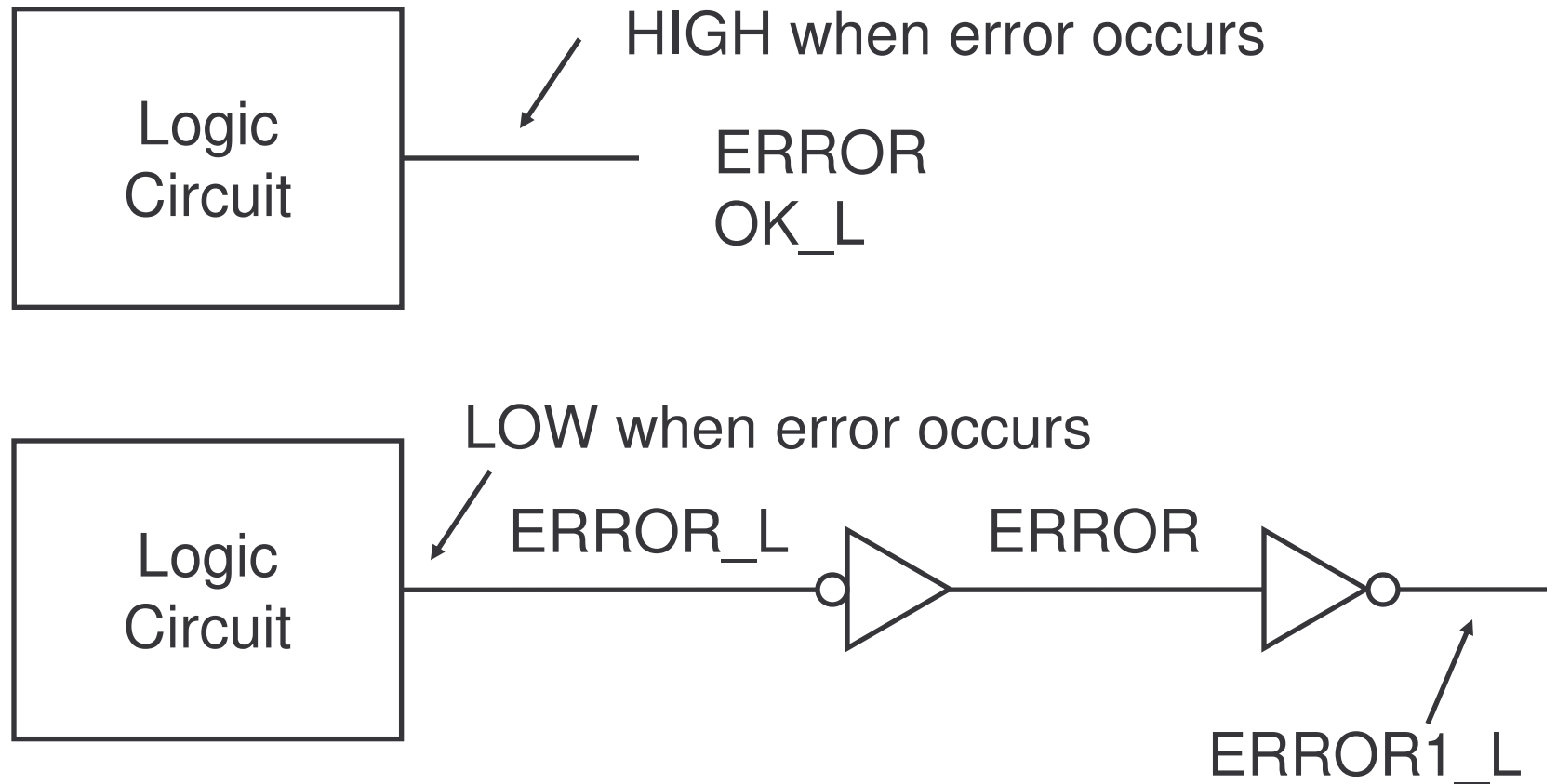


 




 


  Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e



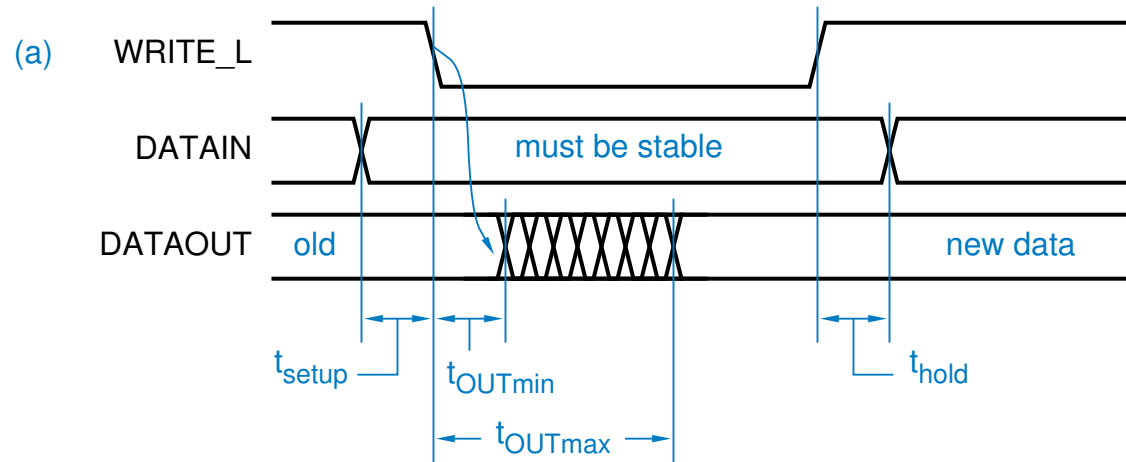

 Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e




# Programmable Logic Arrays (PLAs)

Any combinational logic function can be realized as a sum of products.

Idea: Build a large AND-OR array with lots of inputs and product terms, and programmable connections.

- $n$  inputs
  - AND gates have  $2n$  inputs -- true and complement of each variable.
- $m$  outputs, driven by large OR gates
  - Each AND gate is programmably connected to each output's OR gate.
- $p$  AND gates ( $p \ll 2^n$ )

# Example: 4x3 PLA, 6 product terms

 

# Programmable Array Logic (PALs)


How beneficial is product sharing?


- Not enough to justify the extra AND array

PALs ==> *fixed* OR array

- Each AND gate is permanently connected to a certain OR gate.

Example: PAL16L8

 

 

10 primary inputs

8 outputs, with 7 ANDs per output

1 AND for 3-state enable

6 outputs available as inputs

- more inputs, at expense of outputs

- two-pass logic, helper terms

Note inversion on outputs

- output is complement of sum-of-products

- newer PALs have selectable inversion

# Designing with PALs

---

Compare number of inputs and outputs of the problem with available resources in the PAL.

Write equations for each output using HDL.

Compile the HDL program, determine whether minimized equations fit in the available AND terms.

If no fit, try modifying equations.

# Documentation Standards

---

Block diagrams

- first step in hierarchical design

Schematic diagrams



HDL programs (ABEL, Verilog, VHDL)

Timing diagrams


Circuit descriptions



# Multiplexers

 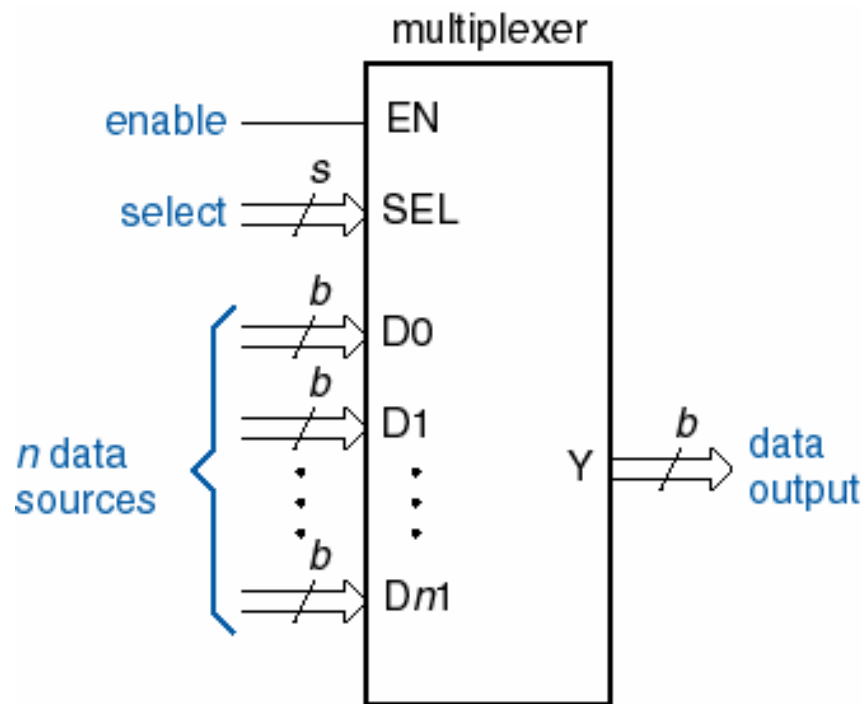



# 74x151 8-input multiplexer

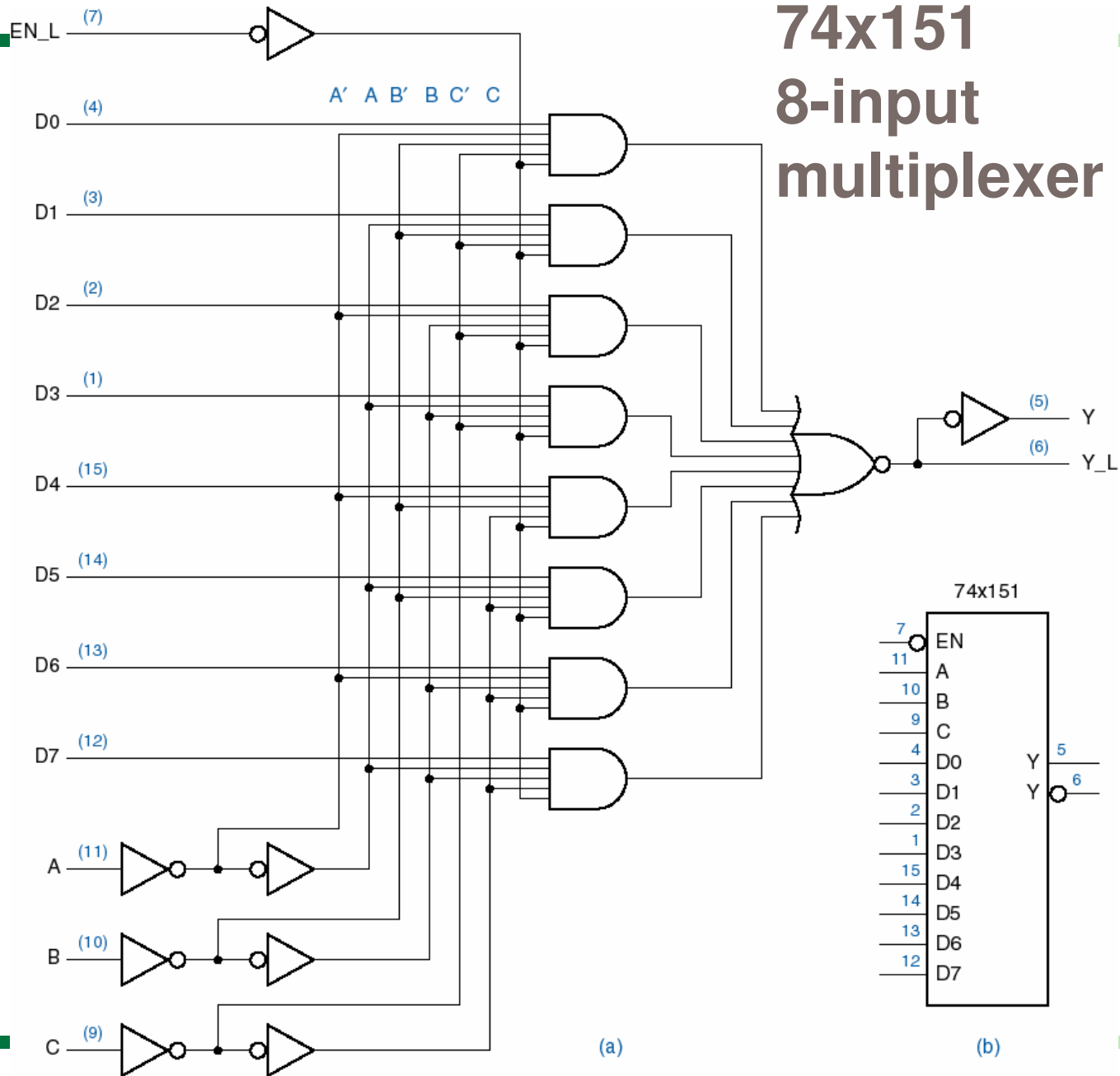

# 74x151 truth table

<i>Inputs</i>				<i>Outputs</i>	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

# CMOS transmission gates

 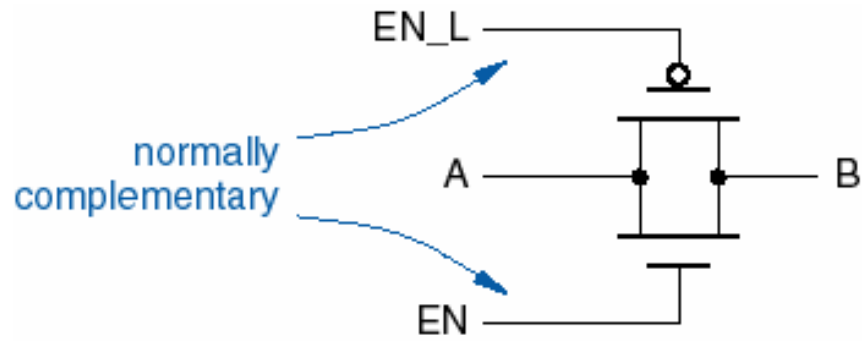

# Other multiplexer varieties

2-input, 4-bit-wide  
– 74x157

<i>Inputs</i>		<i>Outputs</i>			
G_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

4-input, 2-bit-wide  
– 74x153

# Barrel shifter design example

---

$n$  data inputs,  $n$  data outputs

Control inputs specify number of positions to rotate or shift data inputs


Example:  $n = 16$

–  $DIN[15:0]$ ,  $DOUT[15:0]$ ,  $S[3:0]$  (shift amount)


Many possible solutions, all based on multiplexers
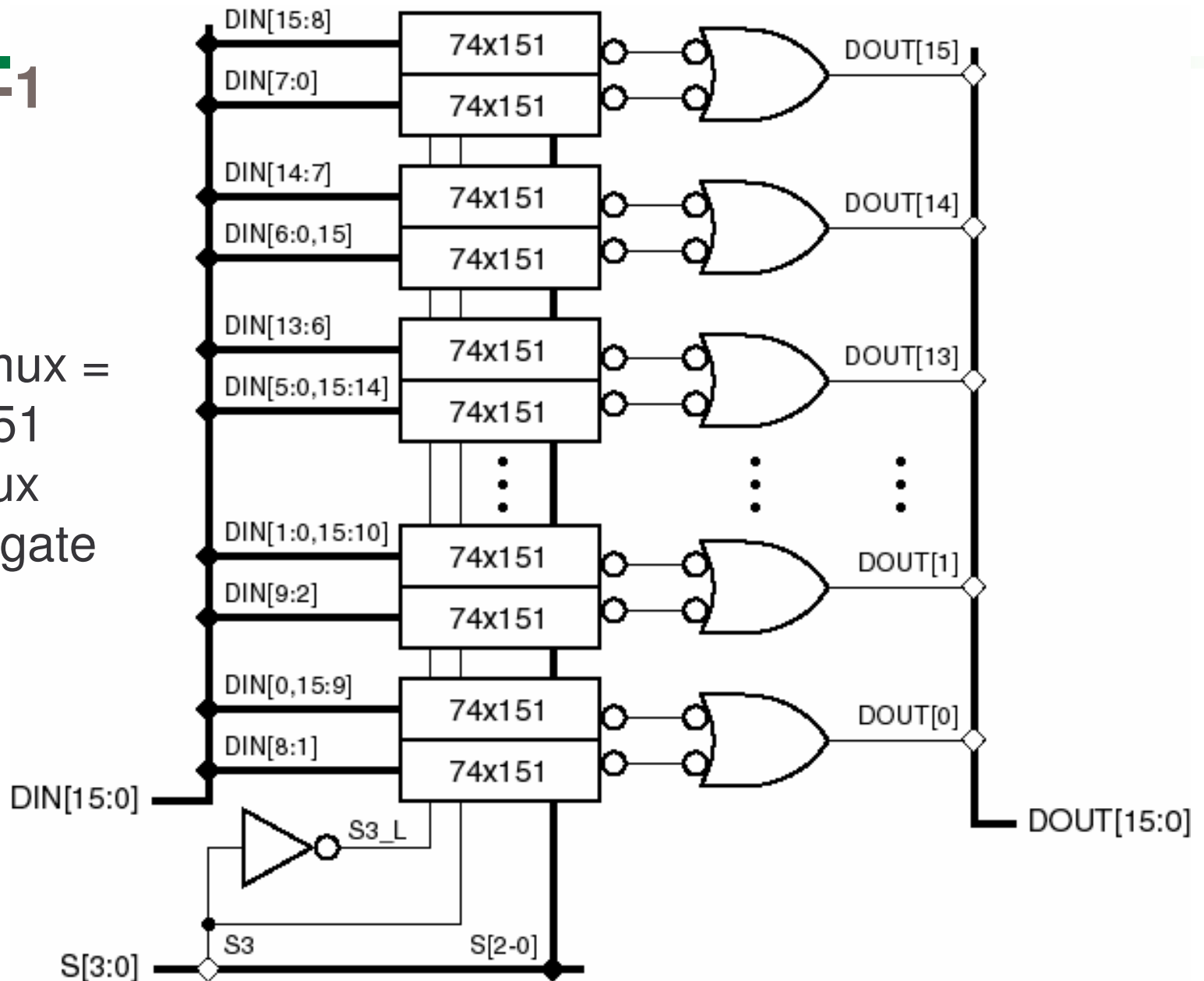
# 16 16-to-1 muxes

16-to-1 mux =  
2 x 74x151  
8-to-1 mux  
+ NAND gate



# 4 16-bit 2-to-1 muxes

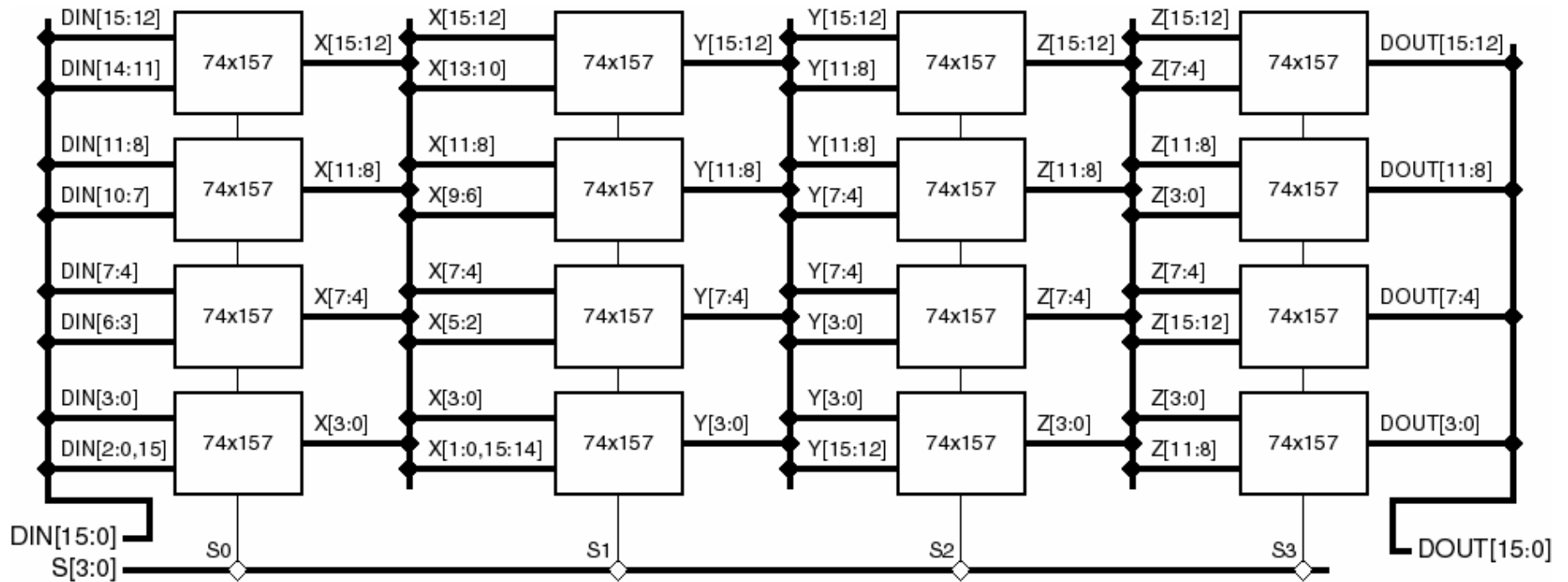

16-bit 2-to-1 mux = 4 x 74x157 4-bit 2-to-1 mux



## Properties of different approaches

<i><b>Multiplexer Component</b></i>	<i><b>Data Loading</b></i>	<i><b>Data Delay</b></i>	<i><b>Control Loading</b></i>	<i><b>Total ICs</b></i>
74x151	16	2	32	36
74x251	16	1	32	32
74x153	4	2	8	16
74x157	2	4	4	16


## 2-input XOR gates

Like an OR gate, but ***excludes*** the case where both inputs are 1.

$X$	$Y$	$X \oplus Y$ (XOR)	$(X \oplus Y)'$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1



XNOR: complement of XOR

# XOR and XNOR symbols

 

  
# Gate-level XOR circuits

No direct realization with just a few transistors.




# Equality Comparators



1-bit comparator

 


4-bit comparator

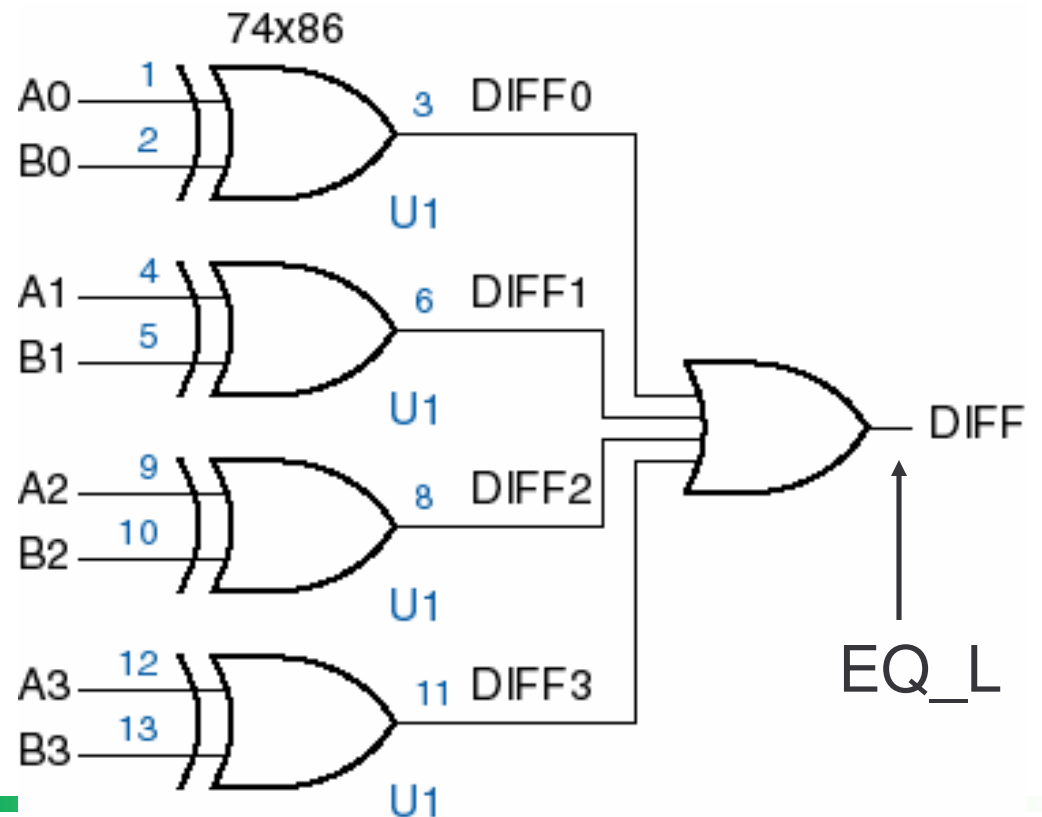

# 8-bit Magnitude Comparator

 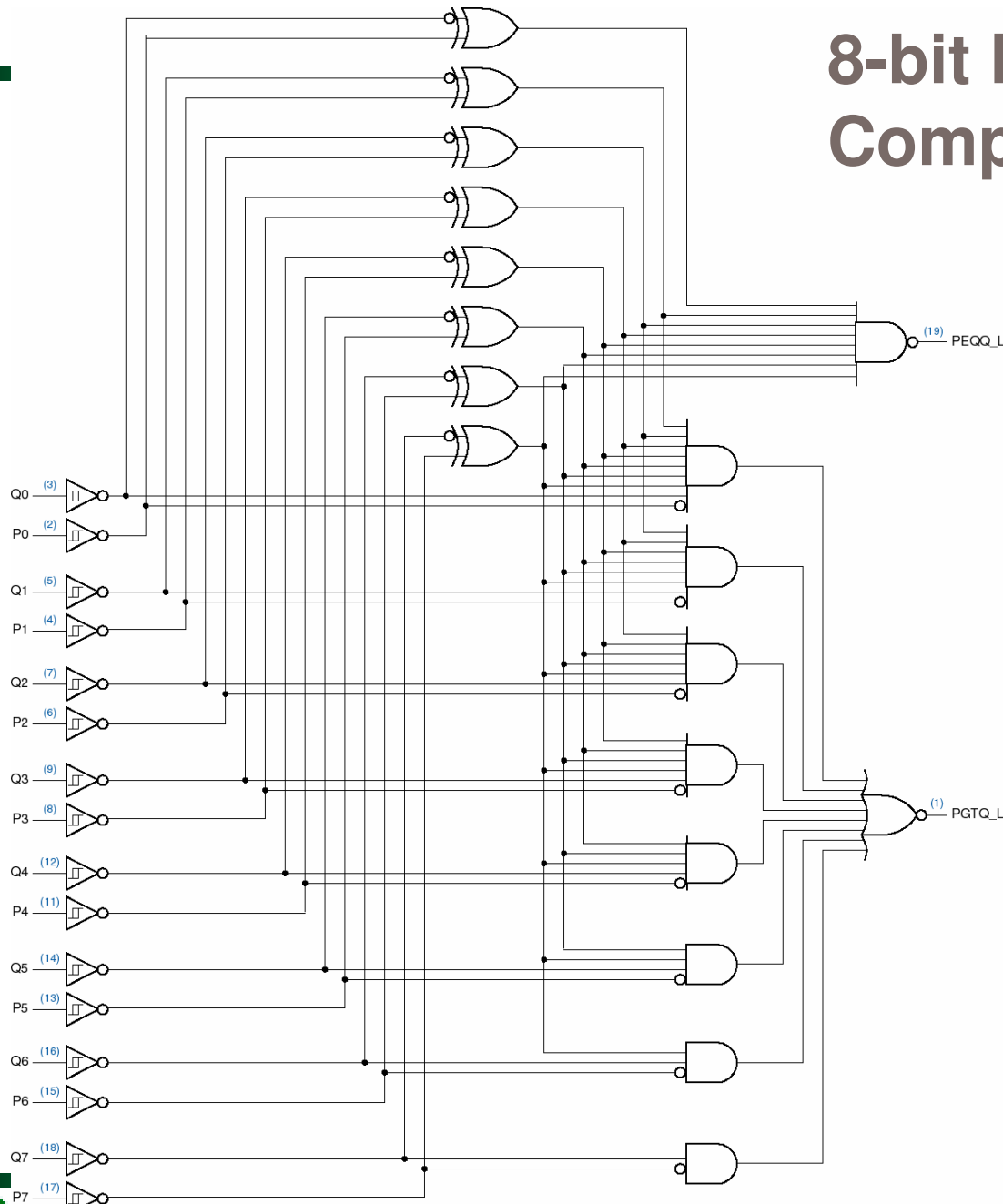

## Other conditions

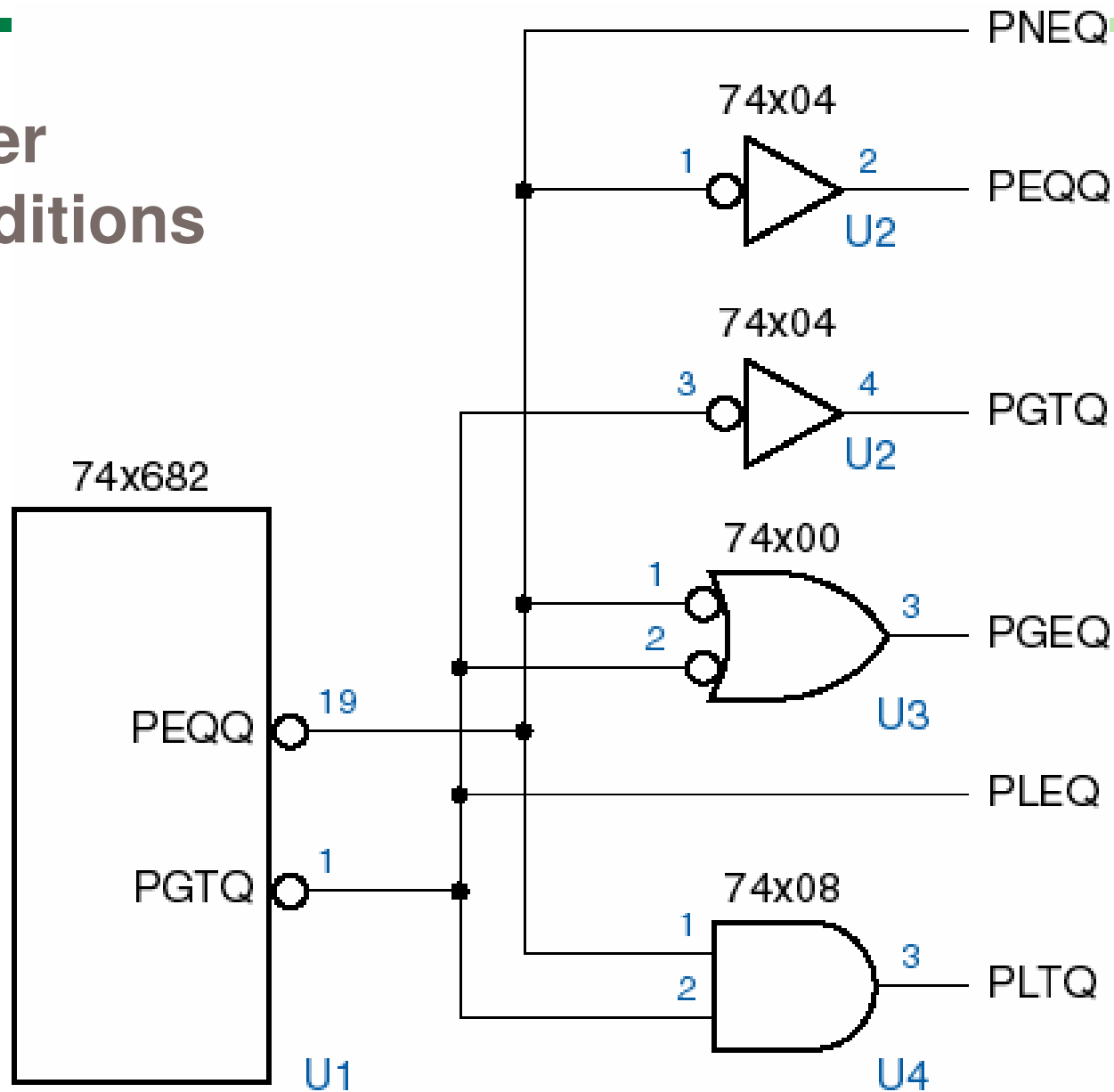

# Adders

Basic building block is “full adder”




- 1-bit-wide adder, produces sum and carry outputs

Truth table:


X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



# Full-adder circuit

 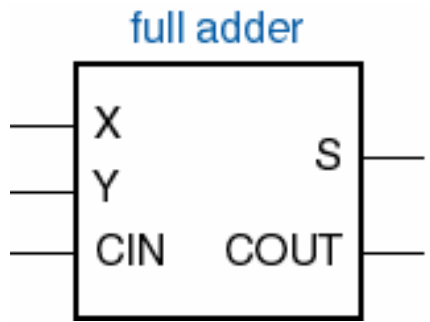 

# Ripple adder

 


Faster adders eliminate or limit carry chain


- 2-level AND-OR logic  $\implies 2^n$  product terms
- 3 or 4 levels of logic, carry lookahead

# 74x283


## 4-bit adder

Uses carry  
lookahead  
internally


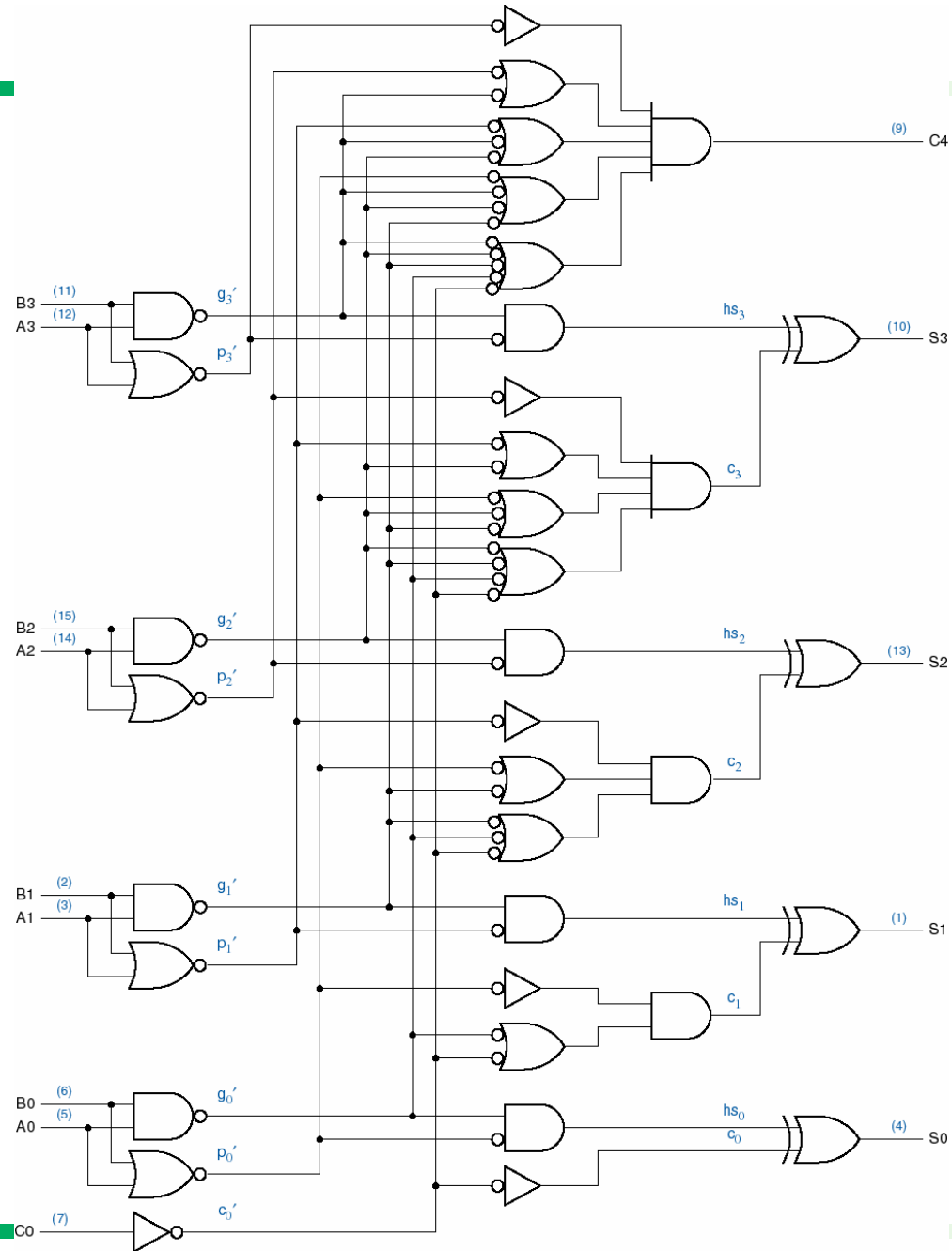


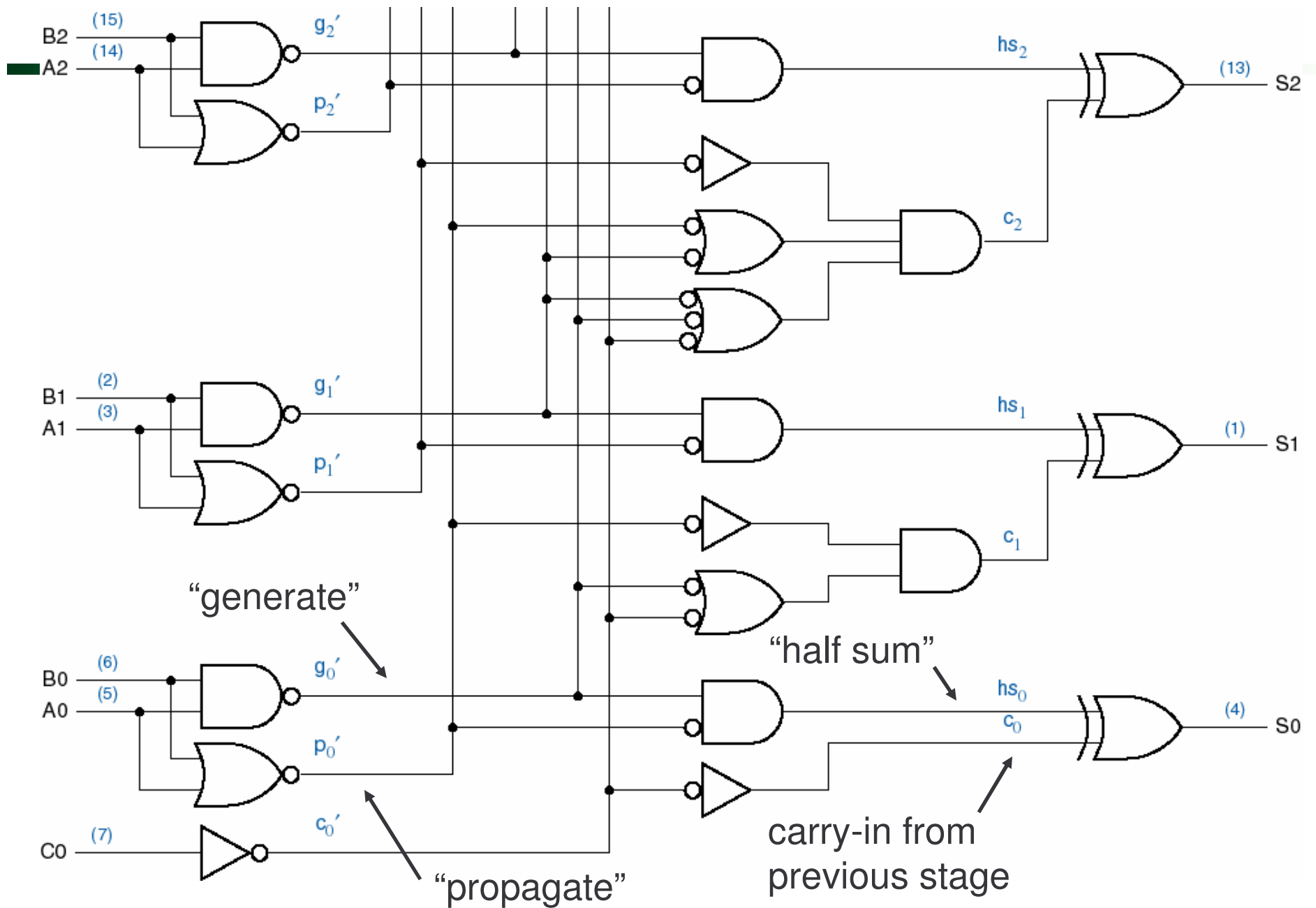

# Ripple carry between groups

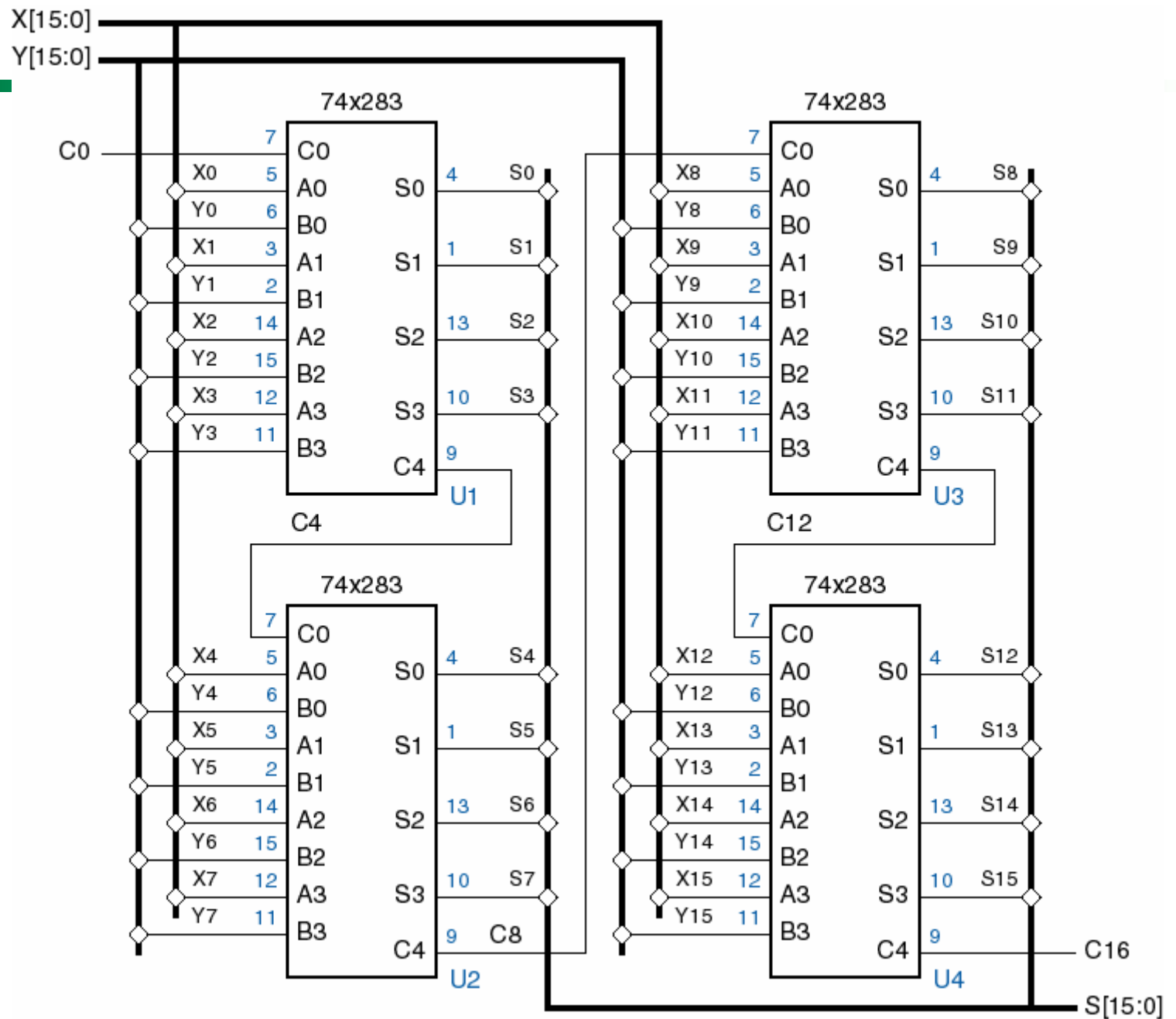

# Lookahead carry between groups

 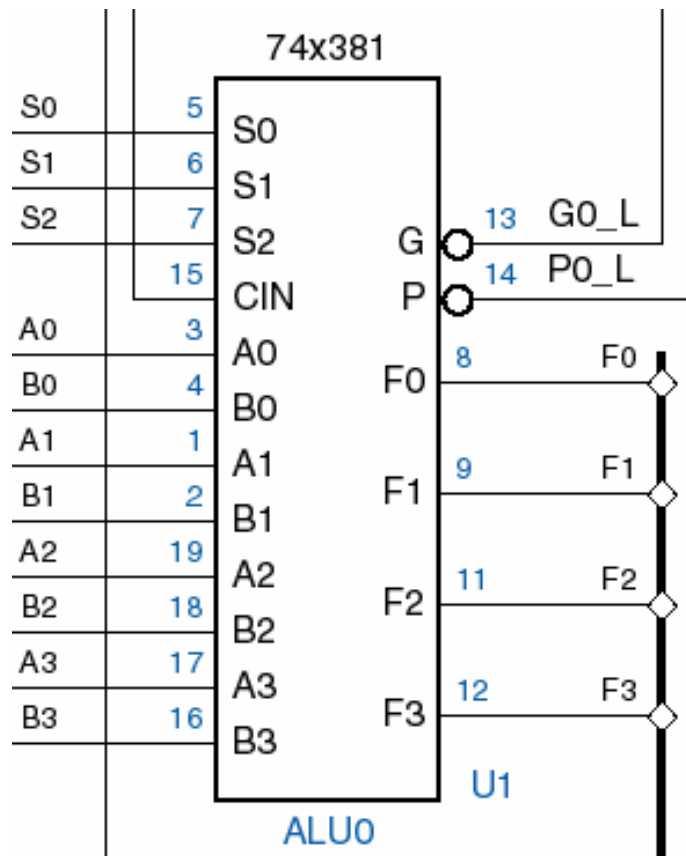

# Subtraction

---

Subtraction is the same as addition of the two's complement.



The two's complement is the bit-by-bit complement plus 1.

Therefore,  $X - Y = X + Y + 1$  .

- Complement Y inputs to adder, set  $C_{in}$  to 1.
- For a borrow, set  $C_{in}$  to 0.

—


# Full subtractor = full adder, almost

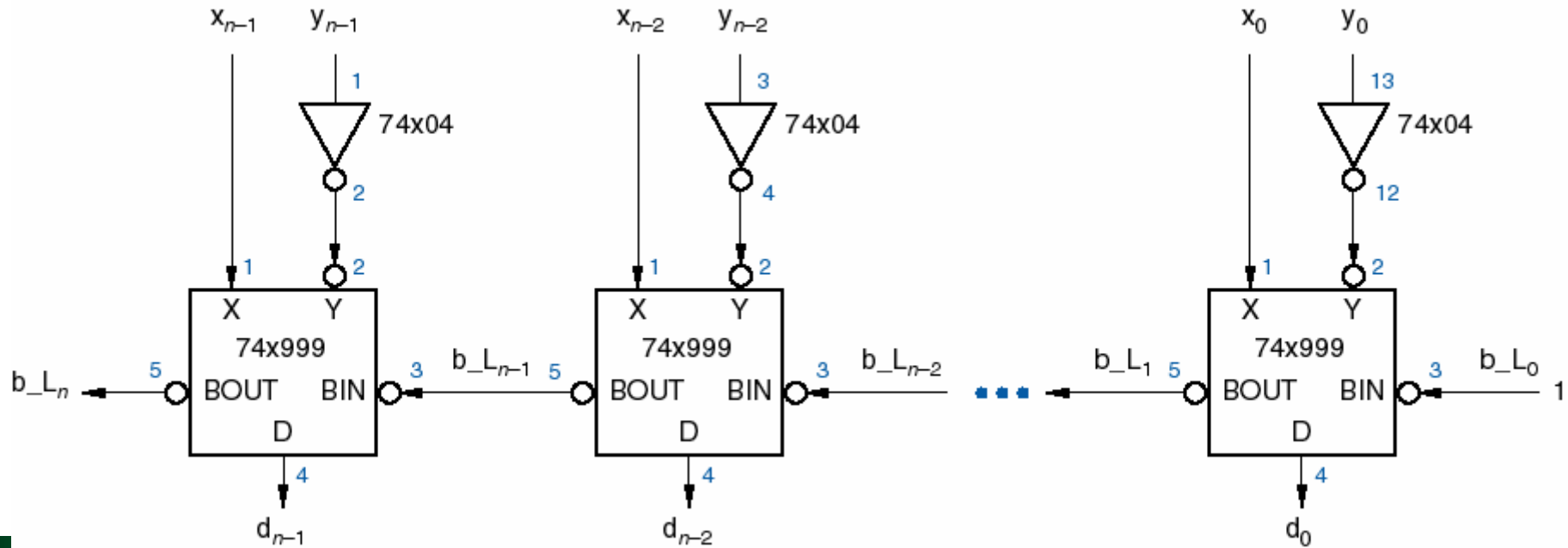 




# Multipliers


## 8x8 multiplier

 


# Full-adder array

 


# Faster carry chain

 

# Memory Hierarchy

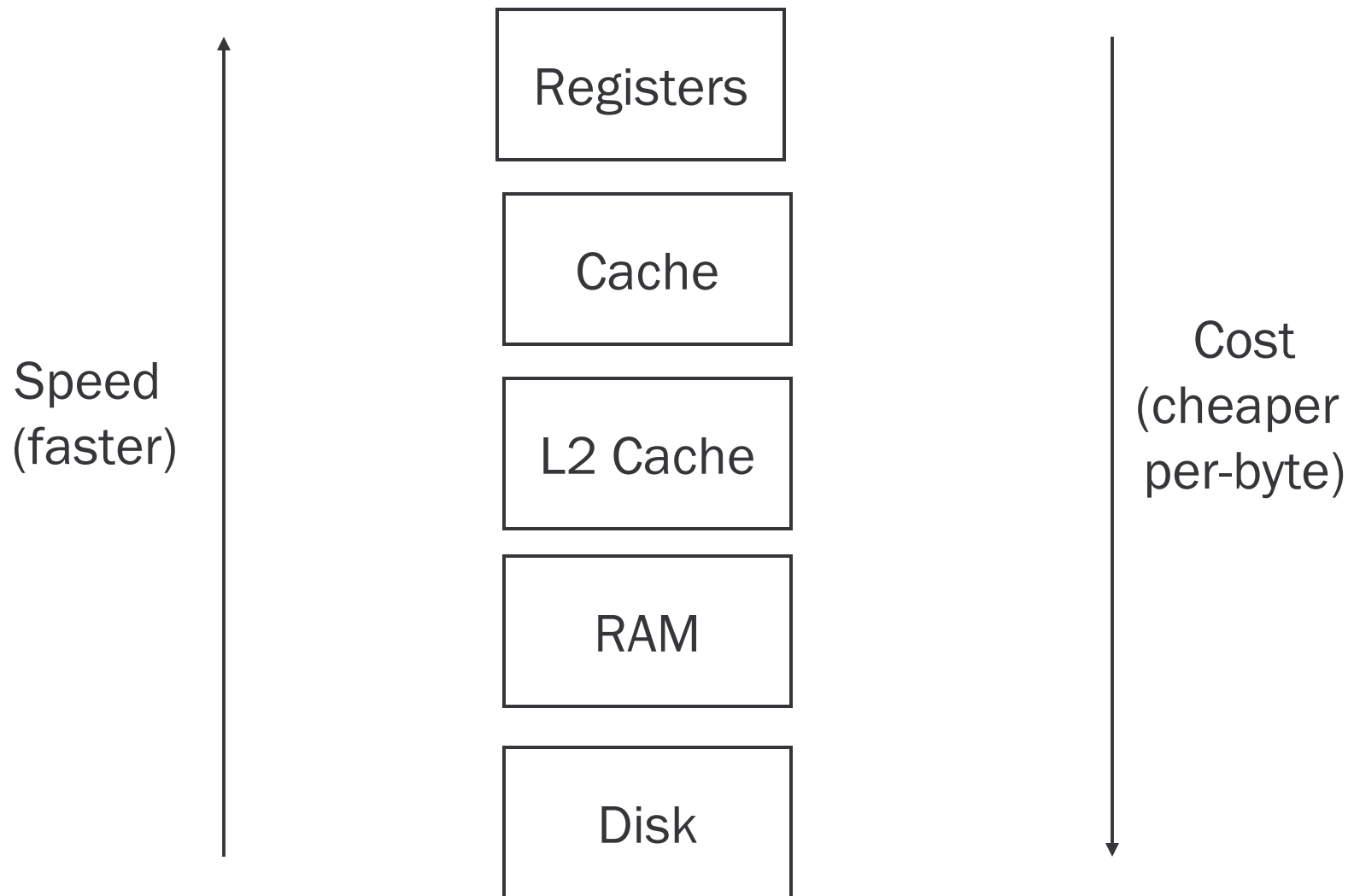

# View of Computer System

 


# Memory

To build a memory -- a logical  $k \times m$  array of stored bits.

**Address Space:**  
number of locations  
(usually a power of 2)


$k = 2^n$   
locations

 

**Addressability:**  
number of bits per location  
(e.g., byte-addressable)

$m$  bits

# 2<sup>2</sup> x 3 Memory

 

# More Memory Details

---

This is not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable

Two basic kinds of memory (RAM = Random Access Memory)

Static RAM (SRAM)

- fast, maintains data without power refresh

Dynamic RAM (DRAM)

- slower but denser, bit storage must be periodically refreshed



# Even More Memory Details

---

There are other types of “non-volatile” memory devices:

- ROM
- PROM
- EPROM
- EEPROM
- Flash

Can you think of other memory devices?


# Electronics Packaging

---


- There are several packaging technologies available that an engineer can use to create electronic devices.
- Some are suitable for inexpensive toys but not miniature consumer products, and some are suitable for miniature consumer products but not inexpensive toys.
- These packages have metal leads that are the conductive wire that connect electricity from the outside world to the silicon inside the package.
- Leads between packages are connected with small copper traces on a printed circuit board (PCB), and the package leads are soldered to the PCB.
 
# Examples of Electronics Packages

Dual In-line Package (DIP) Older technology, requires the metal leads to go through a hole in the printed circuit board.




 Dual Flat Pack (DFP) - A fairly recent technology, metal leads solder to the surface of the printed circuit board.



 
# Examples of Electronics Packages

Quad Flat Pack (QFP) - like the Dual Flat Pack, except here are metal leads are on four sides.



 Ball Grid Array (BGA) - The connections to the component are on the bottom of the chip, and have balls of solder on these connections.




# Driving Force: The Clock

The clock is a signal that keeps the control unit moving.


- At each clock “tick,” control unit moves to the next machine cycle -- may be next instruction or next phase of current instruction.

Clock generator circuit:

 - Based on crystal oscillator
- Generates regular sequence of “0” and “1” logic levels
- Clock cycle (or machine cycle) -- rising edge to rising edge



# Read-Only Memories

 

# Why “ROM”?


---

## Program storage


- Boot ROM for personal computers
- Complete application storage for embedded systems.

Actually, a ROM is a combinational circuit, basically a truth-table lookup.

 - Can perform any combinational logic function
- Address inputs = function inputs
- Data outputs = function outputs




## Logic-in-ROM example

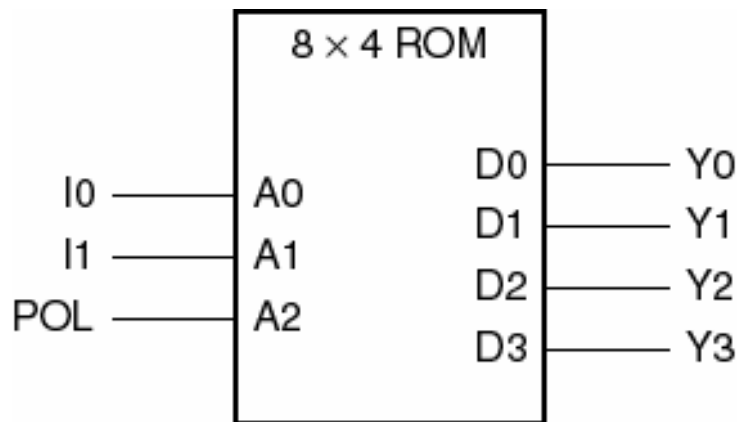


Inputs			Outputs			
A2	A1	A0	D3	D2	D1	D0
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0




# 4x4 multiplier example

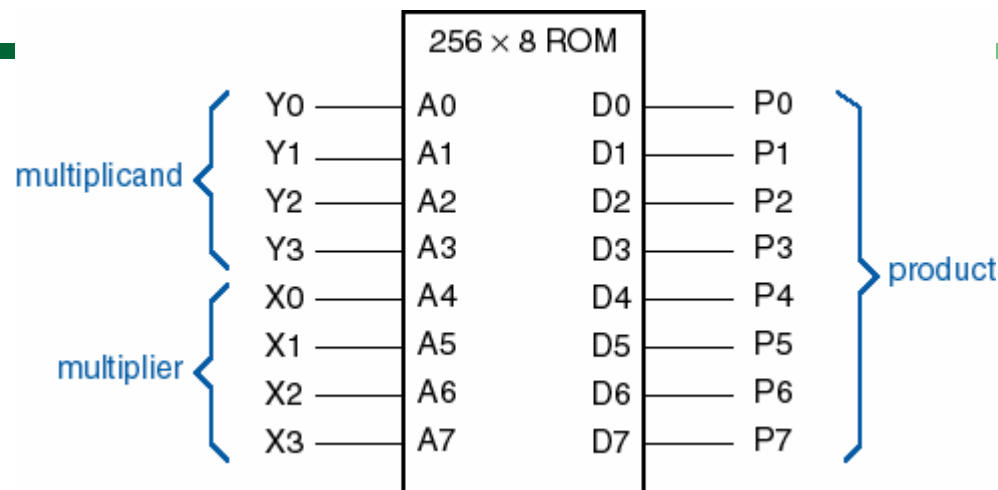

00:	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	
10:	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
20:	00	02	04	06	08	0A	0C	0E	10	12	14	16	18	1A	1C	1E
30:	00	03	06	09	0C	0F	12	15	18	1B	1E	21	24	27	2A	2D
40:	00	04	08	0C	10	14	18	1C	20	24	28	2C	30	34	38	3C
50:	00	05	0A	0F	14	19	1E	23	28	2D	32	37	3C	41	46	4B
60:	00	06	0C	12	18	1E	24	2A	30	36	3C	42	48	4E	54	5A
70:	00	07	0E	15	1C	23	2A	31	38	3F	46	4D	54	5B	62	69
80:	00	08	10	18	20	28	30	38	40	48	50	58	60	68	70	78
90:	00	09	12	1B	24	2D	36	3F	48	51	5A	63	6C	75	7E	87
A0:	00	0A	14	1E	28	32	3C	46	50	5A	64	6E	78	82	8C	96
B0:	00	0B	16	21	2C	37	42	4D	58	63	6E	79	84	8F	9A	A5
C0:	00	0C	18	24	30	3C	48	54	60	6C	78	84	90	9C	A8	B4
D0:	00	0D	1A	27	34	41	4E	5B	68	75	82	8F	9C	A9	B6	C3
E0:	00	0E	1C	2A	38	46	54	62	70	7E	8C	9A	A8	B6	C4	D2
F0:	00	0F	1E	2D	3C	4B	5A	69	78	87	96	A5	B4	C3	D2	E1

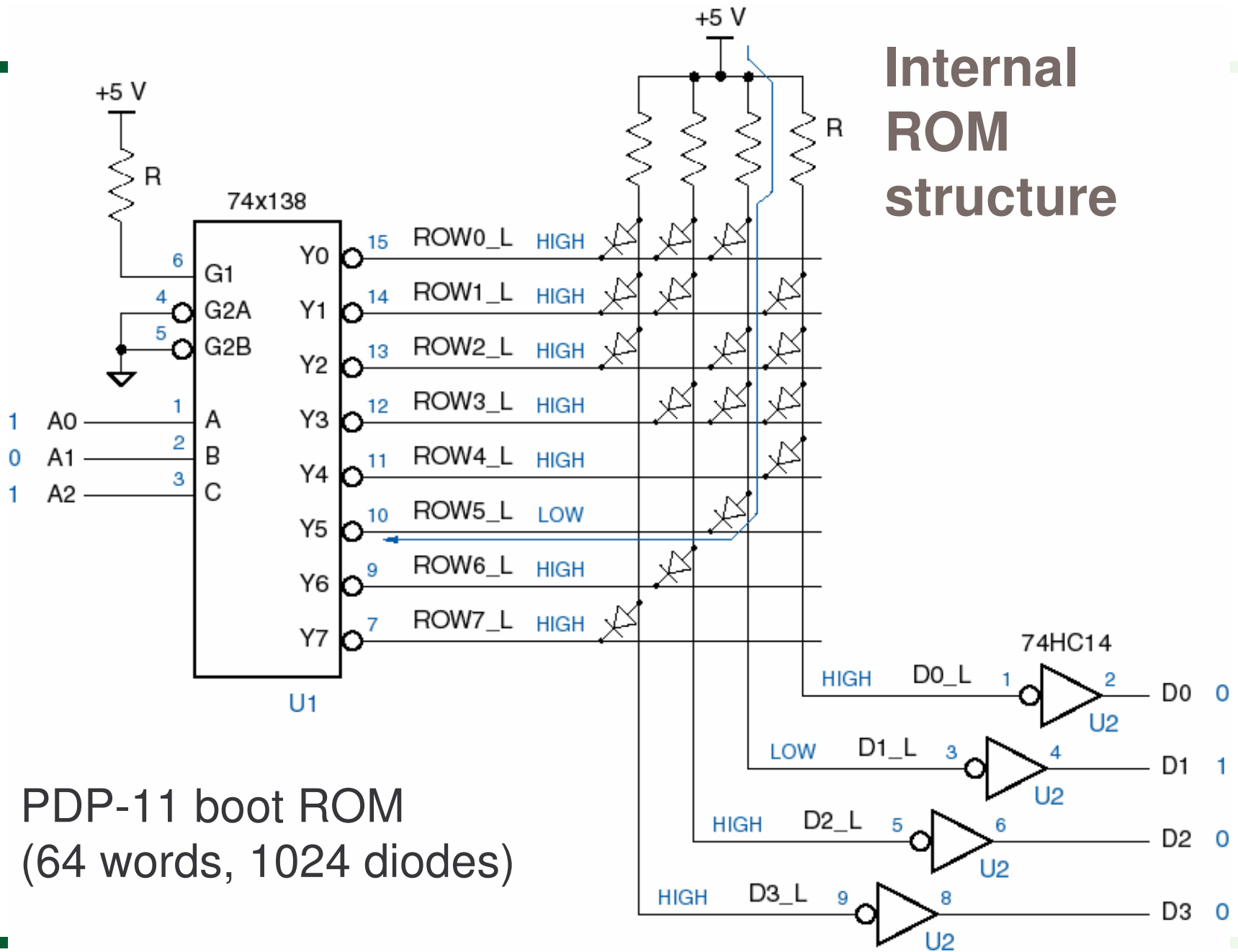


# Two-dimensional decoding

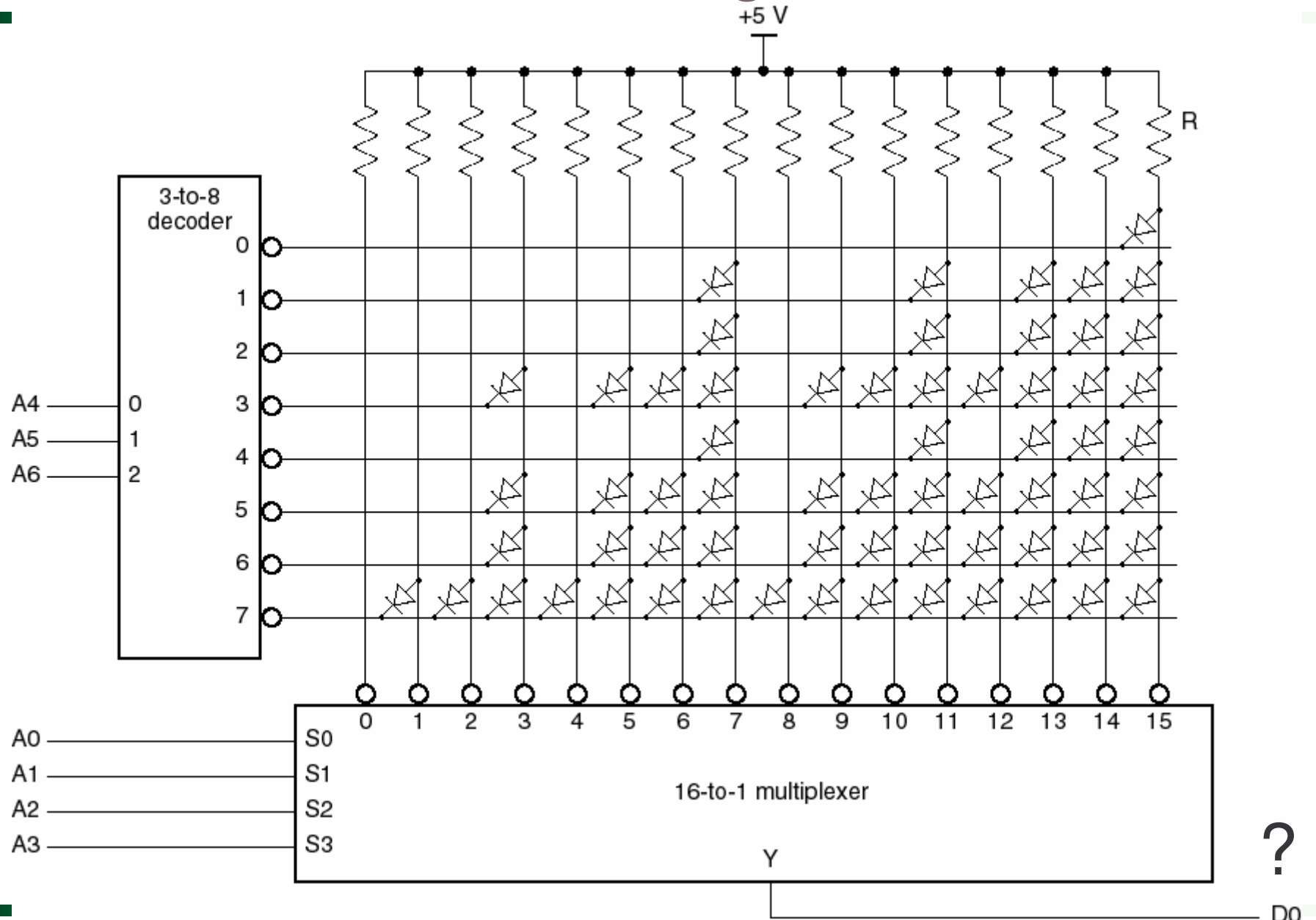

?


# Larger example, 32Kx8 ROM

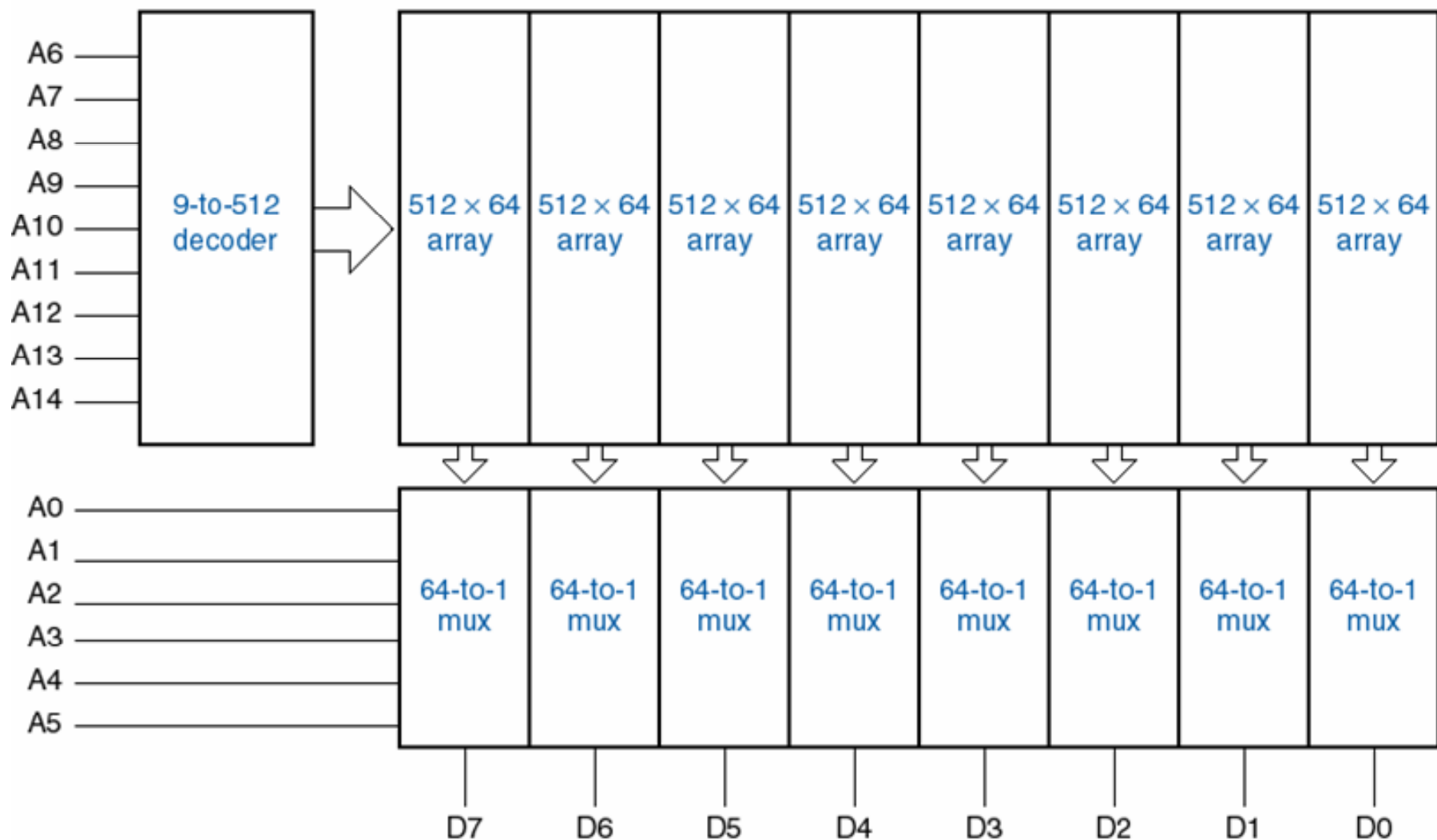


# Today's ROMs

256K bytes, 1M byte, or larger

Use MOS transistors

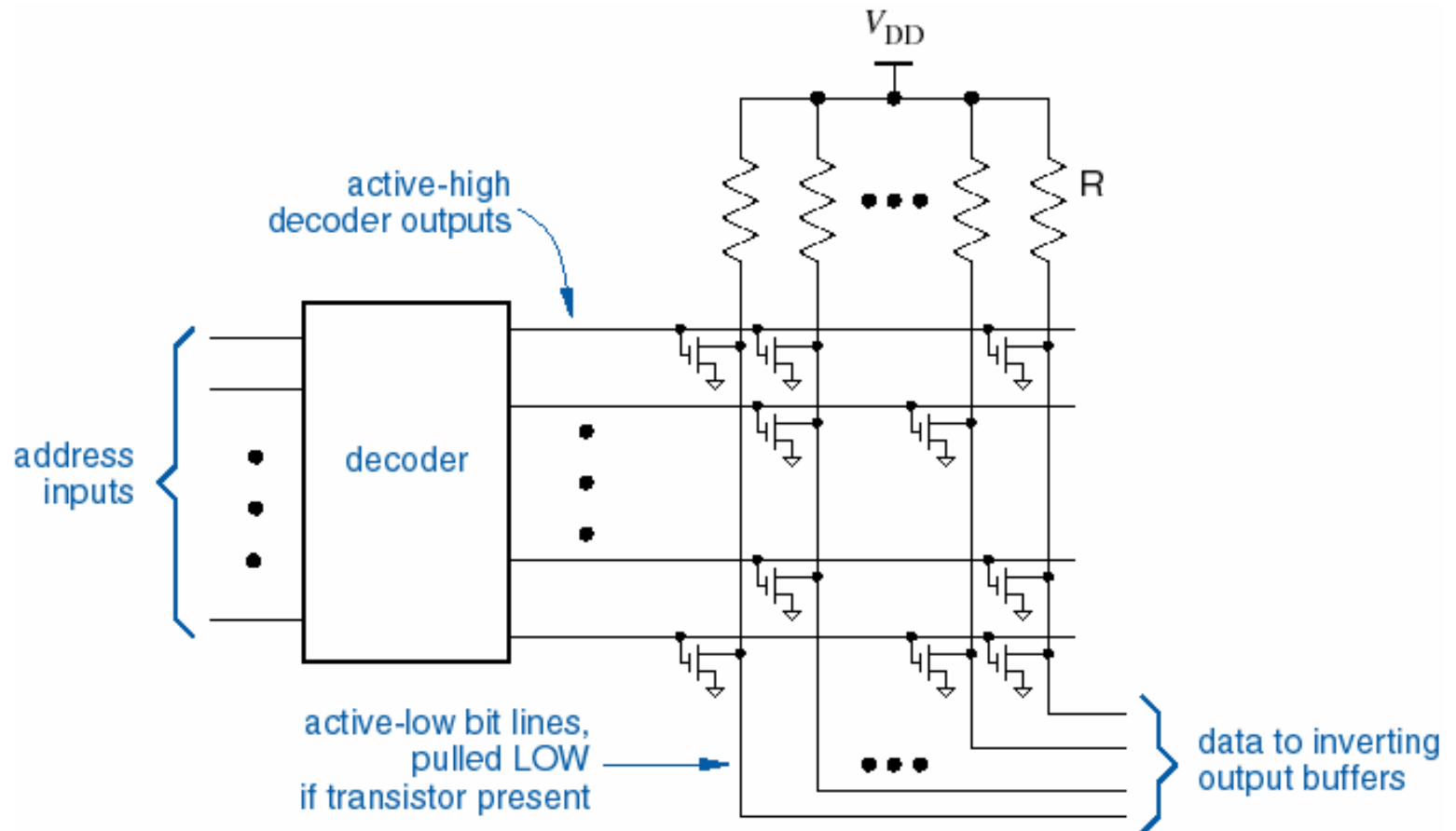


# EEPROMs, Flash PROMs

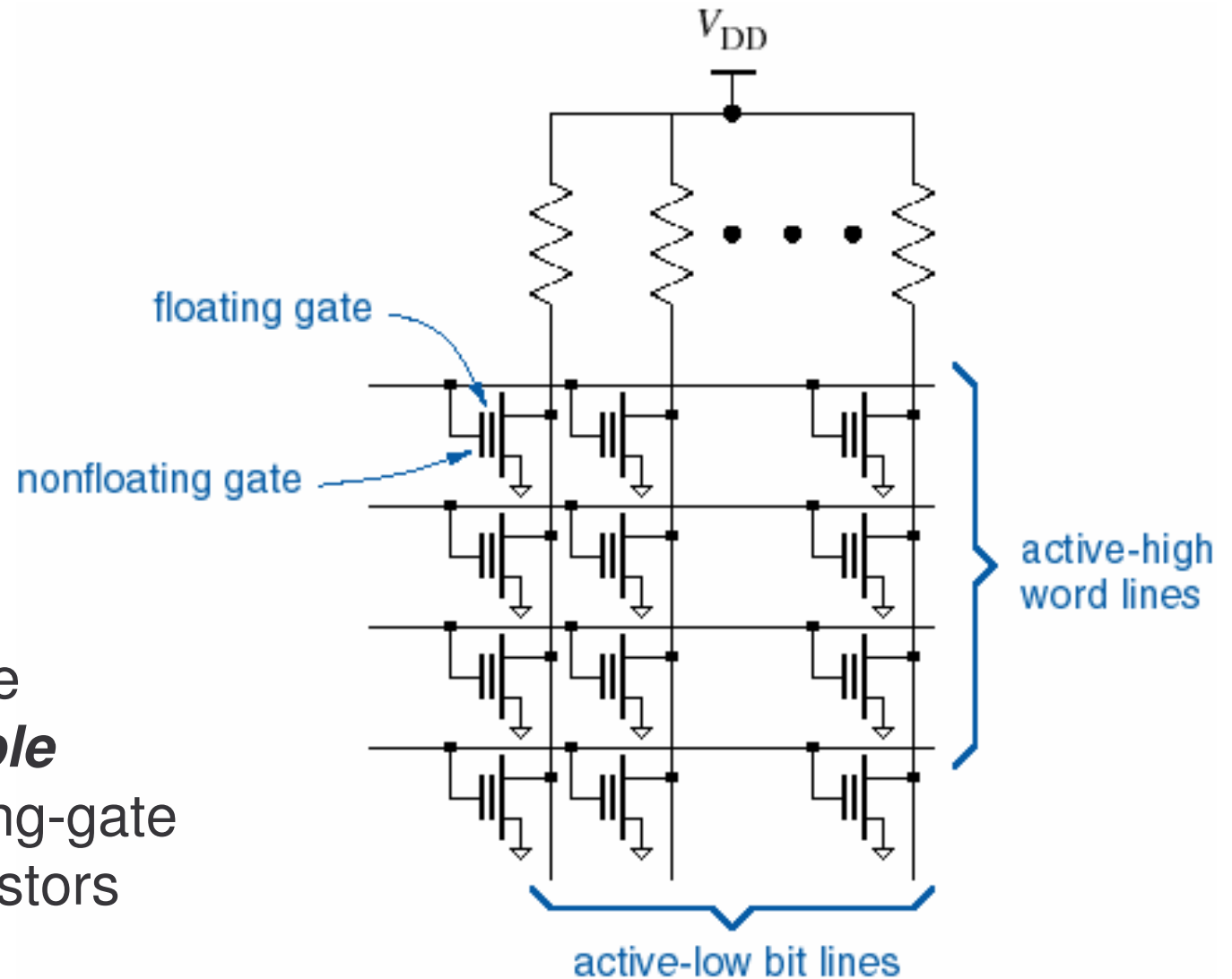

Programmable  
and ***erasable***  
using floating-gate  
MOS transistors

# Typical commercial EEPROMs

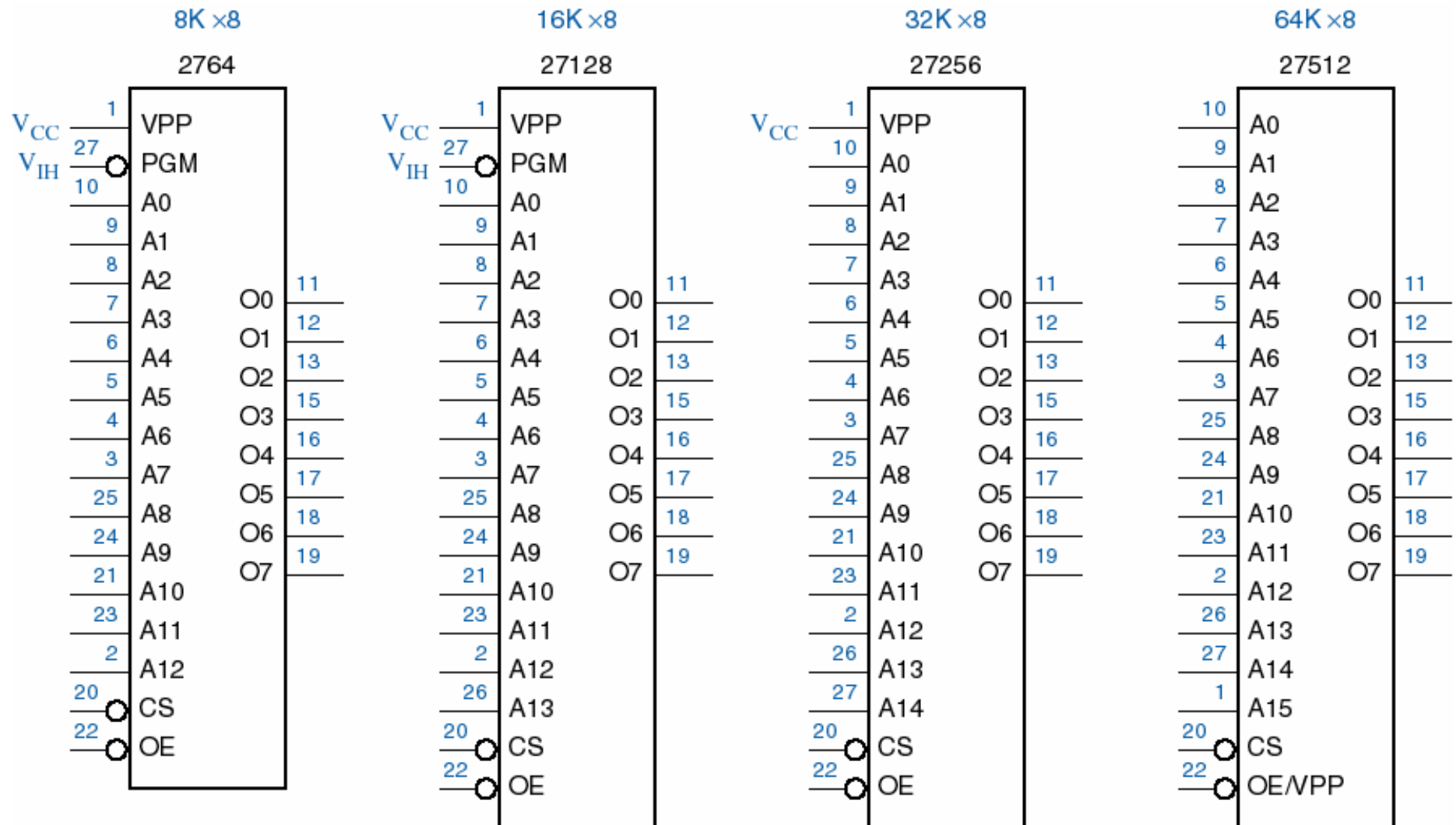

# EEPROM programming

---

Apply a higher voltage to force bit change

- E.g.,  $V_{PP} = 12\text{ V}$
- On-chip high-voltage “charge pump” in newer chips


Erase bits

- Byte-byte
- Entire chip (“flash”)
- One block (typically 32K - 66K bytes) at a time


Programming and erasing are a lot slower than reading  
(milliseconds vs. 10's of nanoseconds)



# Microprocessor EPROM application

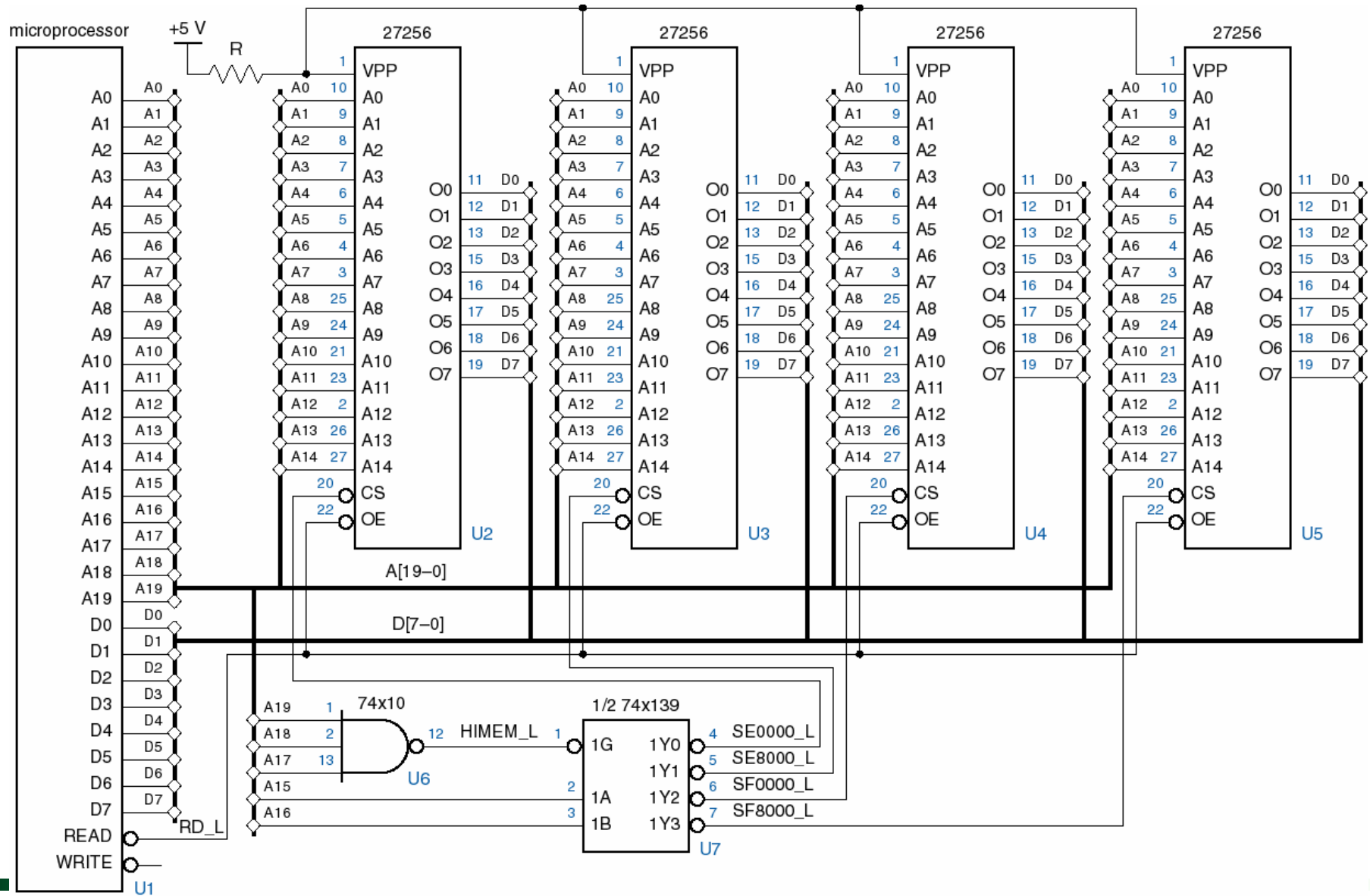

# ROM control and I/O signals

 

# ROM timing

