

UNC Charlotte – Spring 2005 - Exam 1 – February 15, 2005

Name: _____ Student MOSAIC ID: _____

Question	1-4	5	6	7	8	9	10	11	Total
Score	/25	/15	/20	/15	/15	/20	/20	/20	/150

Short Answers

- 1) (10 points) Convert -265_{10} to hexadecimal (16 bits two's complement notation) by hand. Show your work below.

Solution:

$265 = 0000000100001001$ in binary

$= 0x109$ (3 points)

Taking Two's complement:

111111011110110

+

1

$111111011110111 = 0xFEF7$ (7 points)

Answer: 0xFE7

- 2) (3 points) Translate the following ASCII codes into strings of characters by interpreting each group of eight bits as an ASCII character: $0x74696B3721$

Answer: tik7! (.5 for trying, .5 for each correct character)

- 3) (2 points) Sign extend the 6-bit 2's complement binary number 111000 to a 8-bit 2's complement binary number. Then express this number in hexadecimal.

Answer: 0xF8 (all or none)

- 4) (10 points) What is the range of numbers which can be represented by 9 bits if we are representing two's complement integers? (express as the formula and as decimal numbers)

Formula: 2^{n-1} to $2^{n-1} - 1$ (5 points or none)

Decimal: -256 to 255 (5 points or none)

5) (15 points) Perform the operation x3E8 divided by x1B. Show your result in binary (hint: Perform the division in binary). Show your work below.

Answer:

100101, R = 1

100101 (Result) (10 points)


(0x1B) 11011	1111101000 (0x3E8)
	11011 ↓ ↓ ↓ ↓
	00100010
	11011 ↓ ↓
	001100
	11011 ↓
	00001 (Remainder) (5 points)

*Must show work for full credit

*


Long Answer

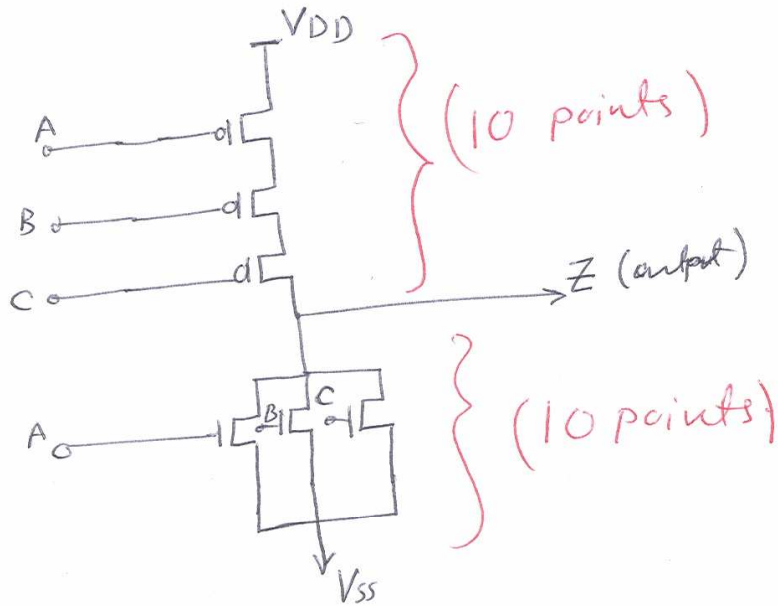- 6) (20 points) Draw a Transistor-Level Schematic Diagram of a three-input NOR Gate, similar to what was done in the homework assignment (similar to Figure 3-16a in the book).



~~ser~~

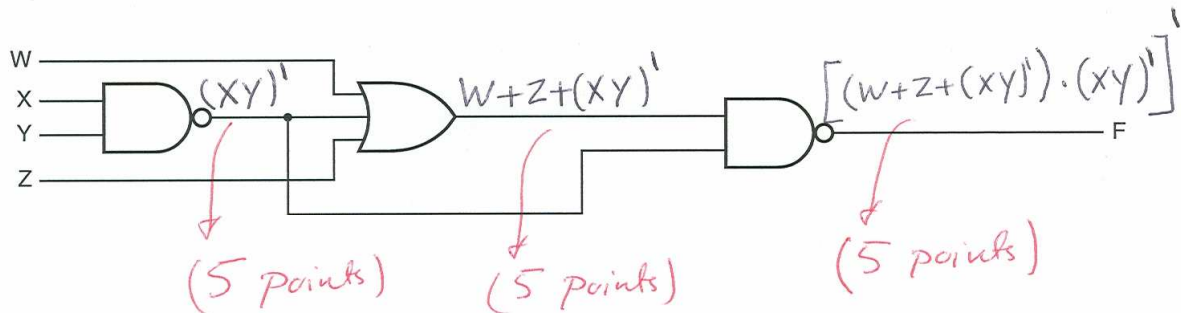- 7) (15 pts.) Combinational Circuit Analysis. Write a logic expression for the output F of the circuit below as a function of the circuit inputs (W, X, Y, and Z). Derive the expression directly from the structure of the circuit; do not simplify.



$$F = \left[(W+Z+(XY)') \cdot (XY)' \right]'$$

- 8) (15 pts.) Complete the Truth Table for the following function: $F = \Sigma A,B,C(1,4,5,7)$ and give the Canonical Sum representation.


Row	A	B	C	F	Minterm
0	0	0	0	0	
1	0	0	1	1	$A' \cdot B' \cdot C$
2	0	1	0	0	
3	0	1	1	0	
4	1	0	0	1	$A \cdot B' \cdot C'$
5	1	0	1	1	$A \cdot B' \cdot C$
6	1	1	0	0	
7	1	1	1	1	$A \cdot B \cdot C$

1-point for each correct entry.
~~15~~ = 12 points.

$$F = (A' \cdot B' \cdot C) + (A \cdot B' \cdot C') + (A \cdot B' \cdot C) + (A \cdot B \cdot C)$$

3-points.

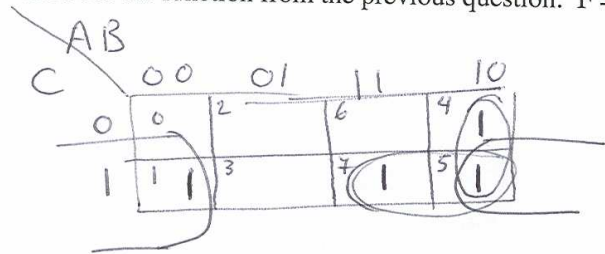
9) (20 pts.) Combinational Circuit Minimization. Using a Karnaugh map, find a minimal sum of products expression for the function from the previous question: $F = \Sigma A, B, C(1, 4, 5, 7)$. Show all of your work.



Points:
 2: box for map
 2: correct labels
 2: correct column & row values
 4: correct entries
 10: correct F.

$F = A \cdot B' + B' \cdot C + A \cdot C$

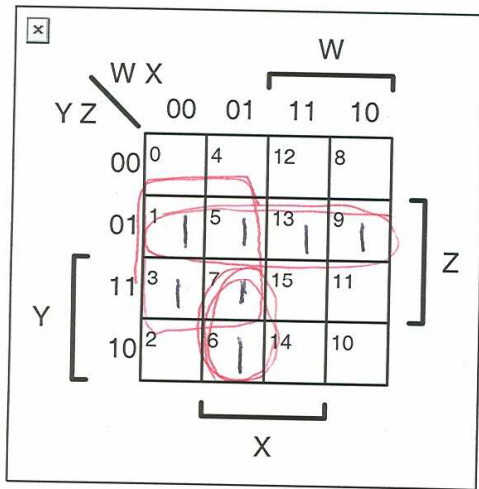10) (20 pts.) Combinational Circuit Minimization. Fill in the Karnaugh map and find a minimal sum of products expression for the function: $F = \Sigma W, X, Y, Z(1, 3, 5, 6, 7, 9, 13)$.



Points:
 5: correct entries
 5: correct "circles"
 10: correct F.

$F = Y'Z + W'Z + W'XY$

11) (20 pts.) Draw the logic diagram (gate-level schematic) for the minimal sum of products expression derived in the question above.

