 


Digital Circuits

ECGR2181
Chapter 3 Notes



Reading: Chapter 3

What is a digital system?

It is a organized collection of digital elements which is designed to perform specified operations on a set of digital inputs and to generate a set of digital responses.


A digital system can be as simple as a block of combinational logic or as complex as a microprocessor.

Characteristics of Digital Systems

What are the characteristics of a digital system?

- Coordinate and sequence its internal operations.
- Data processing and storage.
- Cooperate in transferring data to & from itself.
- Sequences operations of external entities.

Overview of a digital system

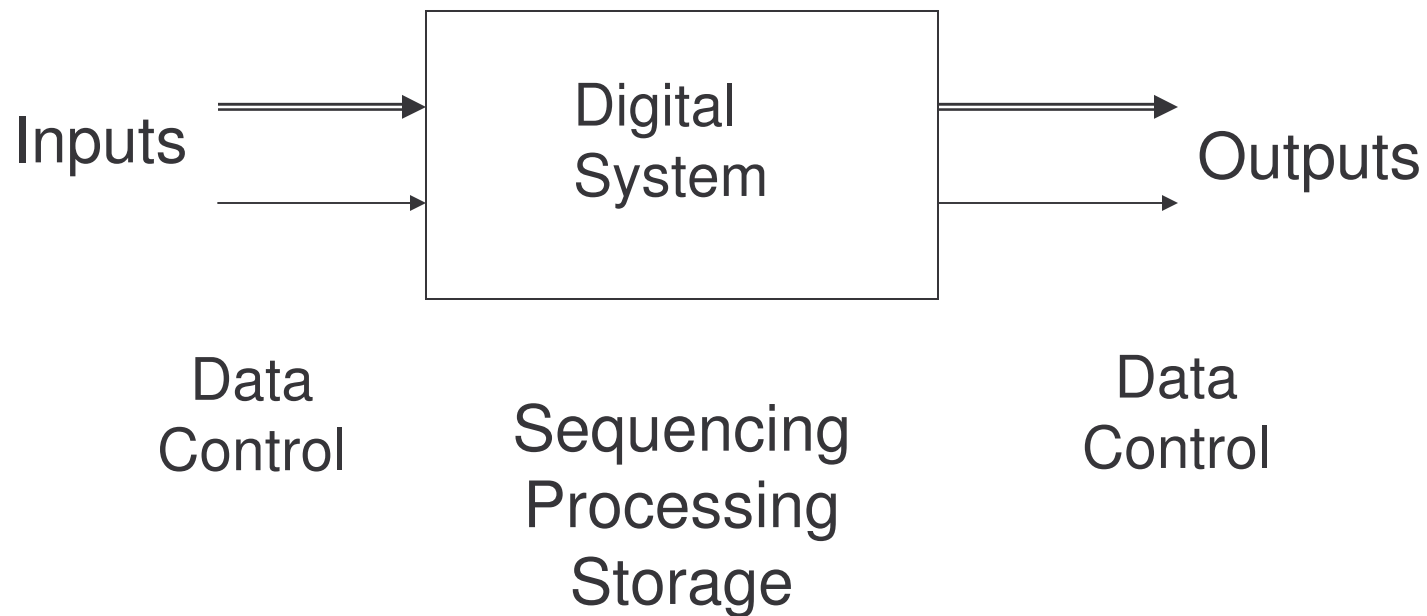

Input & Output Signals

Data:

- Multi-bit: “values”
- Single-bit: decision-making / information

Control: {generally single-bit signals}

- Sequencing operations of system
- Coordinating operations with external units

Introduction to Digital Systems

Nomenclature: (Terms to know.)

Word: A group of binary bits. Typically represents some element of data. The number of bits in a word is indeterminate unless specified. [Example: “24-bit word”]

Byte: An 8-bit word.

Nibble: A 4-bit word.


Introduction to Digital Systems

Structure of digital systems: “system” vs. “module”

- A digital system can be created as a monolithic structure.
- Complex systems often need to be partitioned into some number of subsystems -- “modules”
- For small systems which can be conveniently designed monolithically the terms “system” and “module” may be used interchangeably.


Introduction to Digital Systems

Single module system:

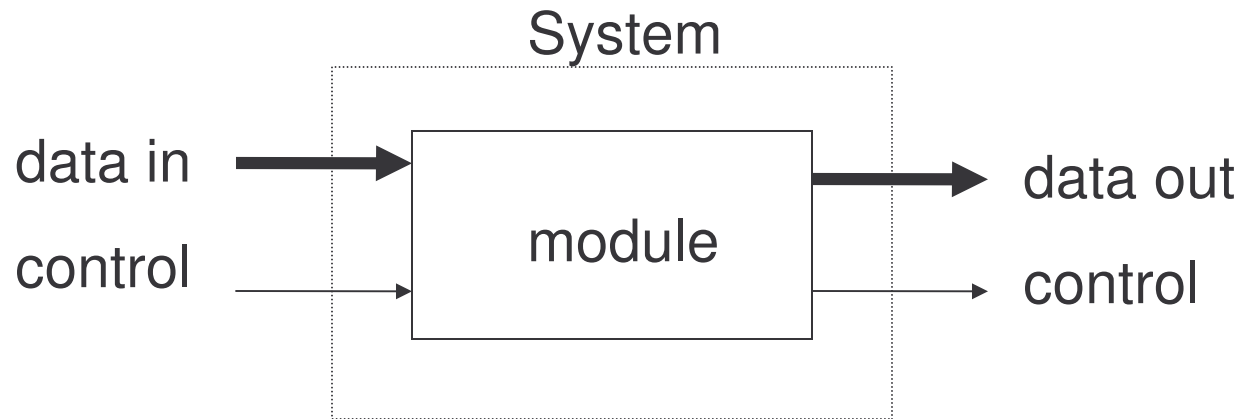

Introduction to Digital Systems

Multiple module system:

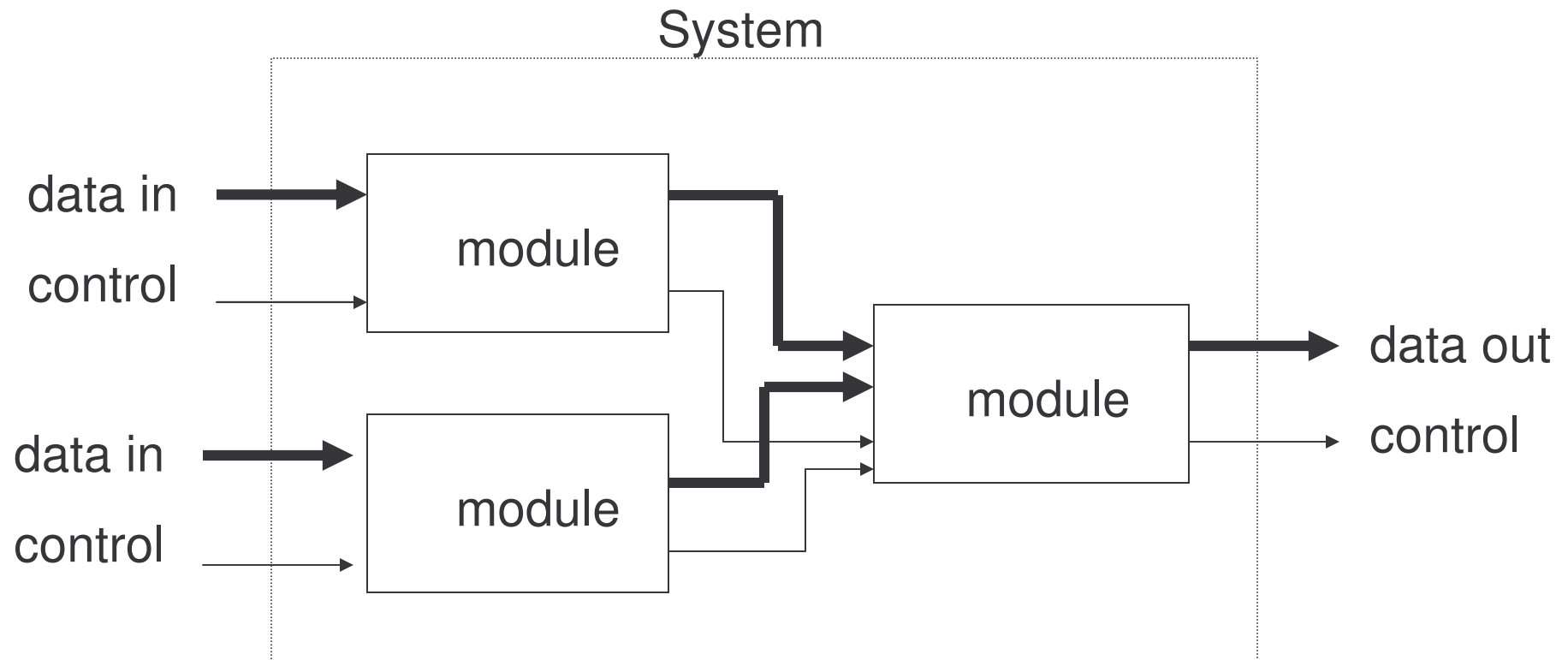

Examples of digital systems

- Data Selector: Route input data to one of two outputs.
- Data Converter: Inputs a 32-bit data word and outputs it as 4 bytes.
- Message Generator: Outputs a fixed message when a “start” command is received
- Communications Buffer: Receives and stores a “block” of data. When the block is complete, it resends the stored data.
- Microprocessor: “Does everything!”


A first look at the design process

1. Understand the functional specification.
2. Create a block diagram from the external viewpoint.
3. Fill in the major internal components.
4. Determine the sequence of operations which must occur within the module

Data Selector

Route input data to one of two outputs.

 
Specification: When a new data word arrives at the input, the module inspects the state of the most significant bit and routes the data to output A if the bit is true and to B if the bit is false. The last value sent to either output is retained until replaced.



Data Converter

Inputs 32-bit data word and outputs it as 4 bytes.

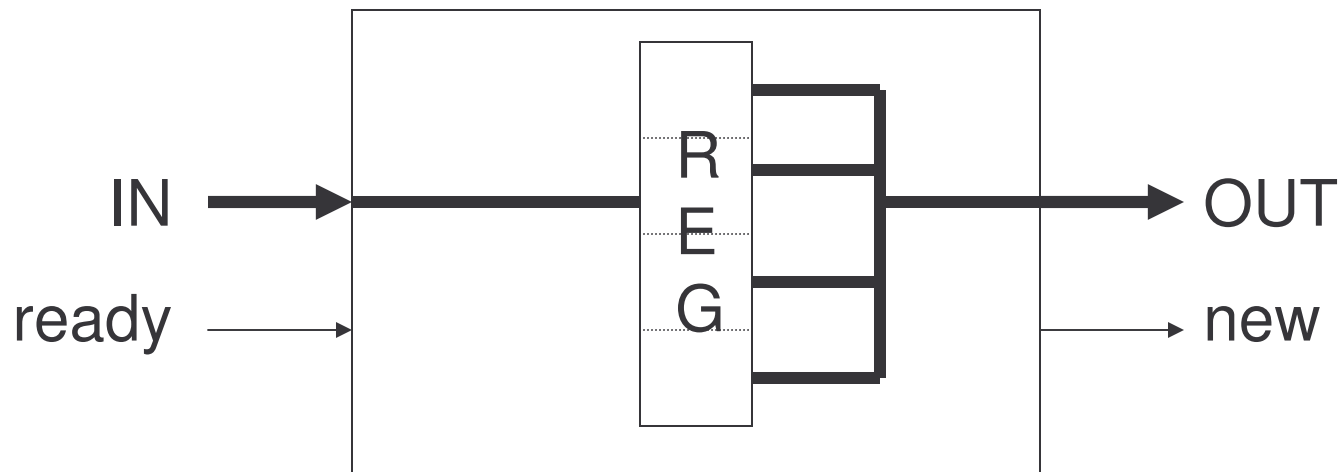
Specification: When a new data word arrives at the input, the module accepts it and then outputs the word as 4 bytes.



Message Generator


Outputs a fixed message when a “start” command is received.

 Specification: When a “start” command is received, the module retrieves the bytes of a message stored in an internal ROM and outputs them sequentially.




Digital Logic

 
Binary system -- 0 & 1, LOW & HIGH, negated and asserted.
Basic building blocks -- AND, OR, NOT



X	Y	X AND Y
0	0	0
0	1	0
1	0	0
1	1	1

 


X	Y	X OR Y
0	0	0
0	1	1
1	0	1
1	1	1

 


X	NOT X
0	1
1	0

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

NAND and NOR

 


X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

 

X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Truth Tables

 


X	Y	Z	XY	X'	Y'	X'+Y'+Z	F

More Practice

X	Y	Z	F

Many representations of digital logic


Transistor-level circuit diagrams

 

Truth tables


Table 1-1
Truth table for the
multiplexer function.

Logic diagrams

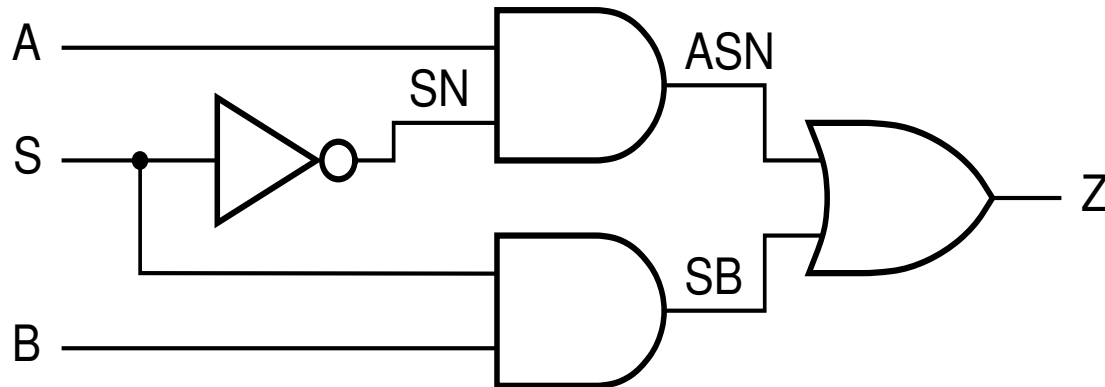

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Logic levels

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Switching threshold varies with voltage, temp, process, etc.


- need “noise margin”

Operating closer to the tolerances requires an increase in attention to “analog” behavior.

Logic voltage levels decreasing with process

- 5 -> 3.3 -> 2.5 -> 1.8 V


MOS Transistors

 

Voltage-controlled resistance

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

PMOS

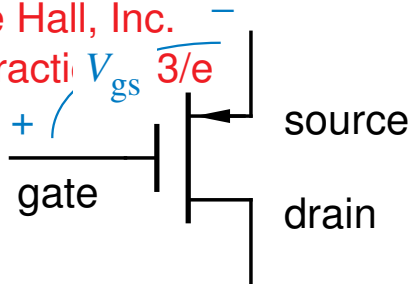


Voltage-controlled resistance:
decrease $V_{gs} \implies$ decrease R_{ds}

Note: normally, $V_{gs} \leq 0$

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

NMOS

 


Voltage-controlled resistance:
increase $V_{gs} \implies$ decrease R_{ds}

Note: normally, $V_{gs} \geq 0$

CMOS Inverter

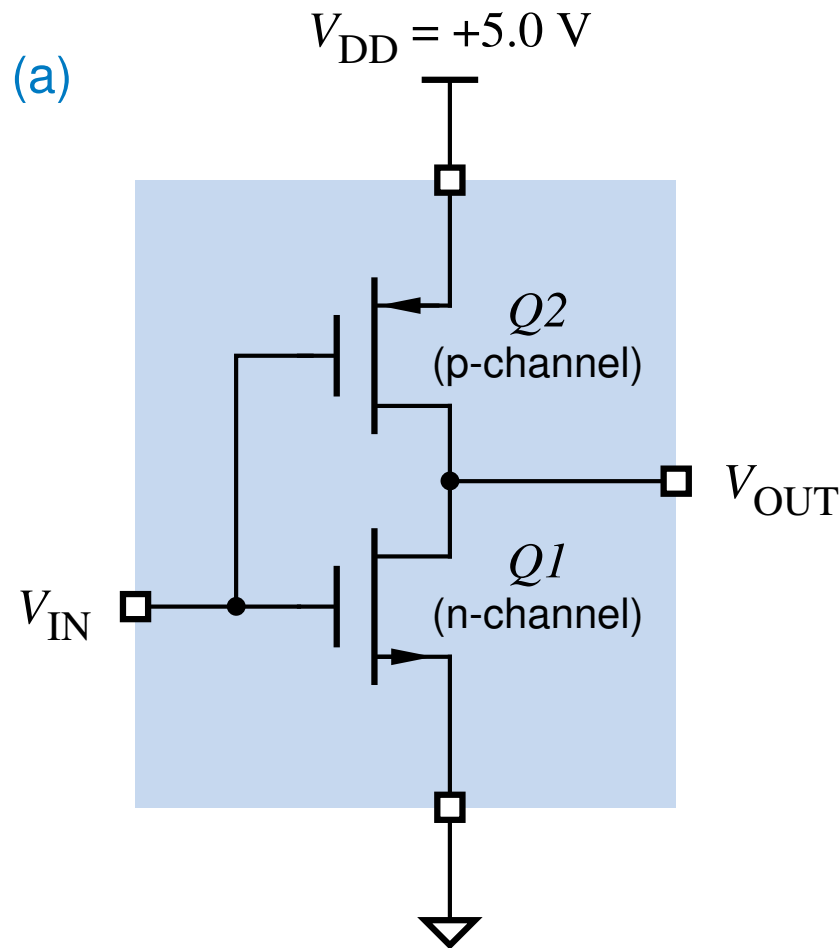
Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e




(b)

V_{IN}	$Q1$	$Q2$	V_{OUT}
0.0 (L)	off	on	5.0 (H)
5.0 (H)	on	off	0.0 (L)

(c)


 


Alternate transistor symbols

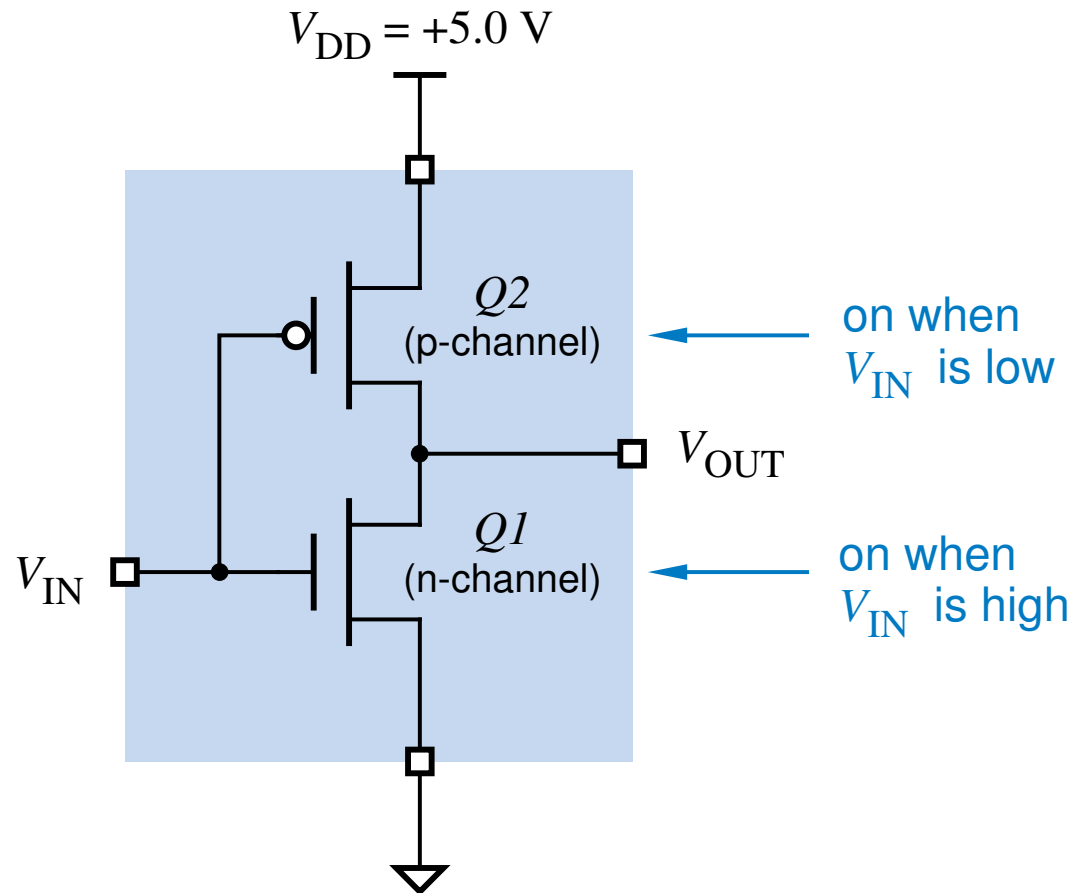

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e


Switch model

  

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

CMOS NAND Gates

Use $2n$ transistors for n -input gate

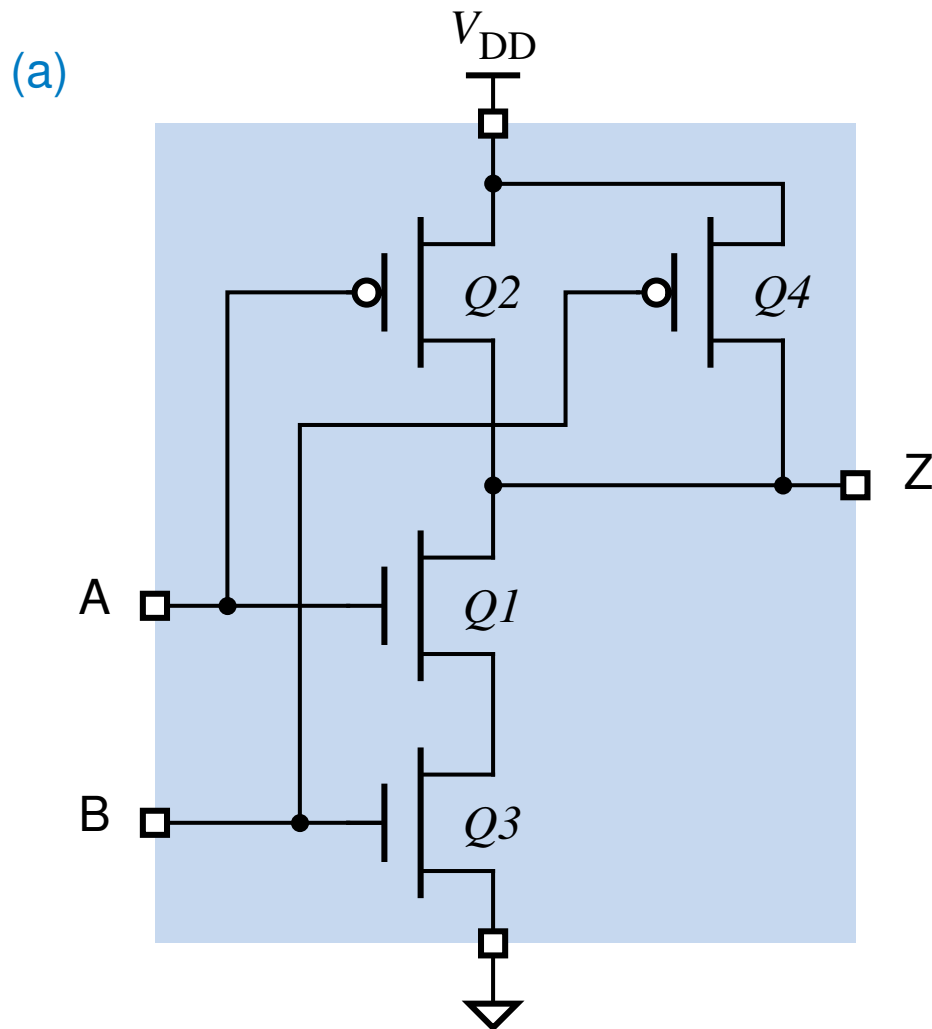

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e




(b)

A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	H
H	L	on	off	off	on	H
H	H	on	off	on	off	L


(c)



CMOS NAND -- switch model

  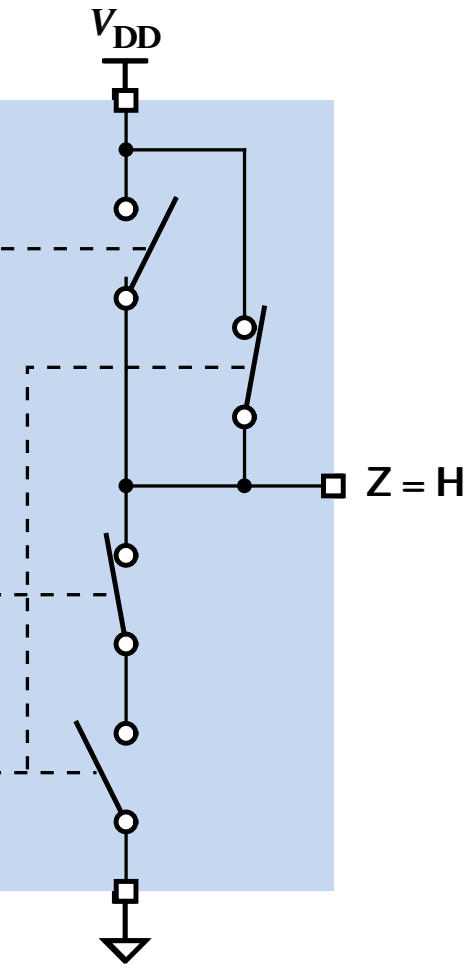


CMOS NAND -- more inputs (3)

 

(b)

A	B	C	Q1	Q2	Q3	Q4	Q5	Q6	Z
L	L	L	off	on	off	on	off	on	H
L	L	H	off	on	off	on	on	off	H
L	H	L	off	on	on	off	off	on	H
L	H	H	off	on	on	off	on	off	H
H	L	L	on	off	off	on	off	on	H
H	L	H	on	off	off	on	on	off	H
H	H	L	on	off	on	off	off	on	H
H	H	H	on	off	on	off	on	off	L


(c)

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

CMOS NOR Gates

 
Like NAND -- $2n$ transistors for n -input gate



(b)

A	B	$Q1$	$Q2$	$Q3$	$Q4$	Z
L	L	off	on	off	on	H
L	H	off	on	on	off	L
H	L	on	off	off	on	L
H	H	on	off	on	off	L

(c)

 


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

NAND vs. NOR

PMOS transistors have higher “on” resistance than NMOS transistors.

NAND

(a)

 


NOR

(a) Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

(b)

(c)

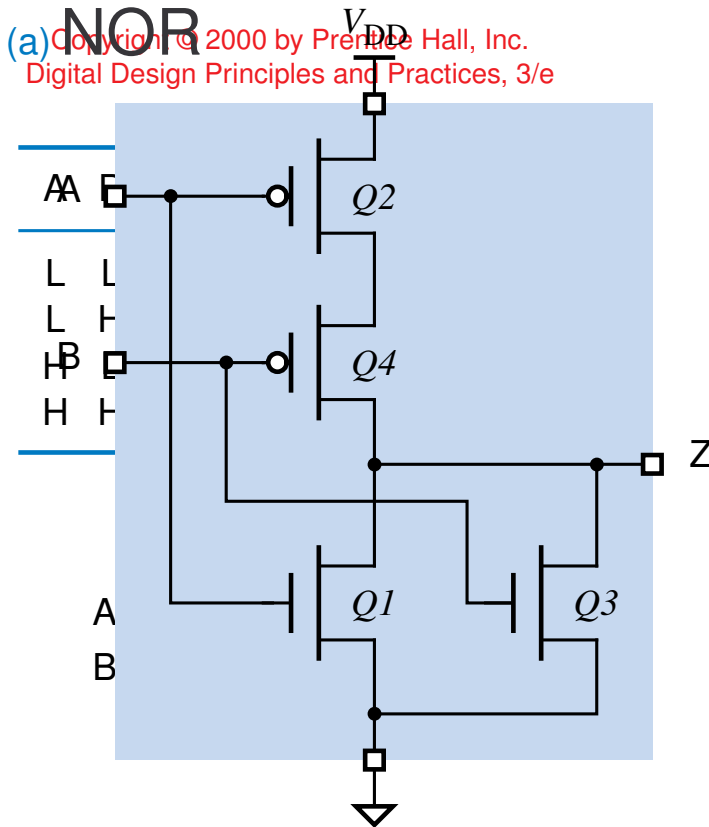


(b)

(c)

Result: NAND gates are preferred in CMOS.

Additional Terms

- **Sinking/Sourcing Current** – (sect. 3.5.2, p. 106) current entering/leaving the output of a device.
- **Fanout** – (sect. 3.5.4) how many gate inputs can a particular device drive and still maintain digital logic characteristics.
- **Unused Inputs** – (sect. 3.5.6) always connect unused inputs to either power supply rail (V_{CC} or Gnd.)
 - Static conditions – may appear to be stable,
 - Dynamic conditions – could be unstable
 - Makes circuit behavior unpredictable.
- **ESD** – Electro-Static Discharge. (sect. 3.5.7) ESD involves the discharge of static electricity and is the deadly enemy of electronic circuits, especially, CMOS devices. ESD damage can be avoided with the use of ESD straps and rubber mats.
- **Transition Time** – (sect. 3.6.1) time required for signal to transit the abnormal region. The time to transit the abnormal region may be different for traversing the region in different directions.

 

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

More Terms ...

- **Propagation Delay** – (sect. 3.6.2) time required for a change on the input to produce a change on the output.
- **Current Spikes** – (sect. 3.6.4) typically seen on the power rails. Produced when many outputs change at the same time. Switching Power Supplies often produce these effects. {t/s note: check frequency to help find source}
- **Decoupling Capacitors** – (sect. 3.6.4) distributes the filtering on the board and aids in the reduction of noise on the power rails.
- **Ground Bounce** – (sect. 3.6.6) read the text. {describe how it looks on an o'scope}
- **Three-state Outputs** – (sect. 3.7.3) devices whose outputs are one of three states, high, low and high impedance. Used to drive an output from multiple, mutually exclusive sources (or devices.)
- Different types of Logic Families:
 - TTL – Transistor-Transistor Logic
 - CMOS – Complementary Metal Oxide Semiconductor
 - ECL – Emitter-Coupled Logic
- Take extreme care when interfacing TTL and CMOS logic devices