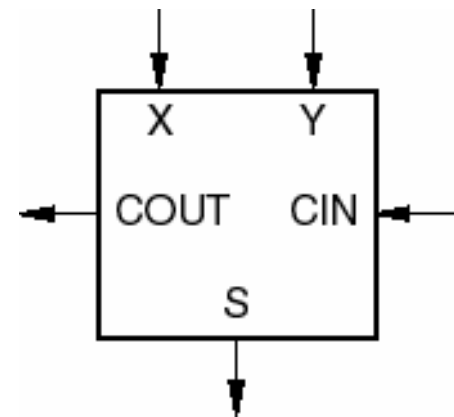


# Combinatorial Logic Design Practices

ECGR2181

*Reading:* Chapter 6



# Documentation Standards

---

Block diagrams

- first step in hierarchical design


Schematic diagrams

HDL programs (ABEL, Verilog, VHDL)

Timing diagrams


Circuit descriptions

# SHIFT-AND-ADD MULTIPLIER






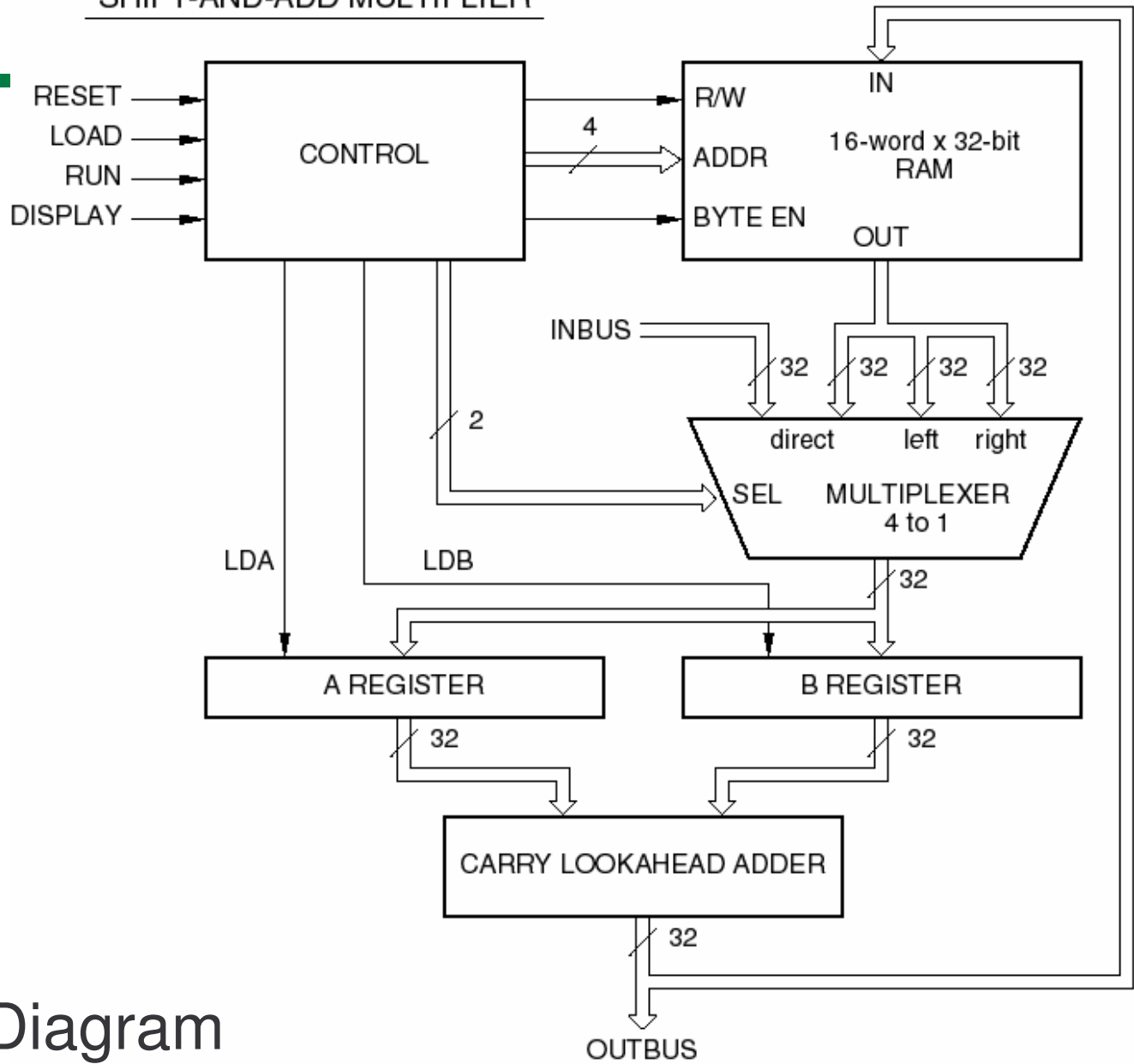


Block Diagram

# Flat schematic structure

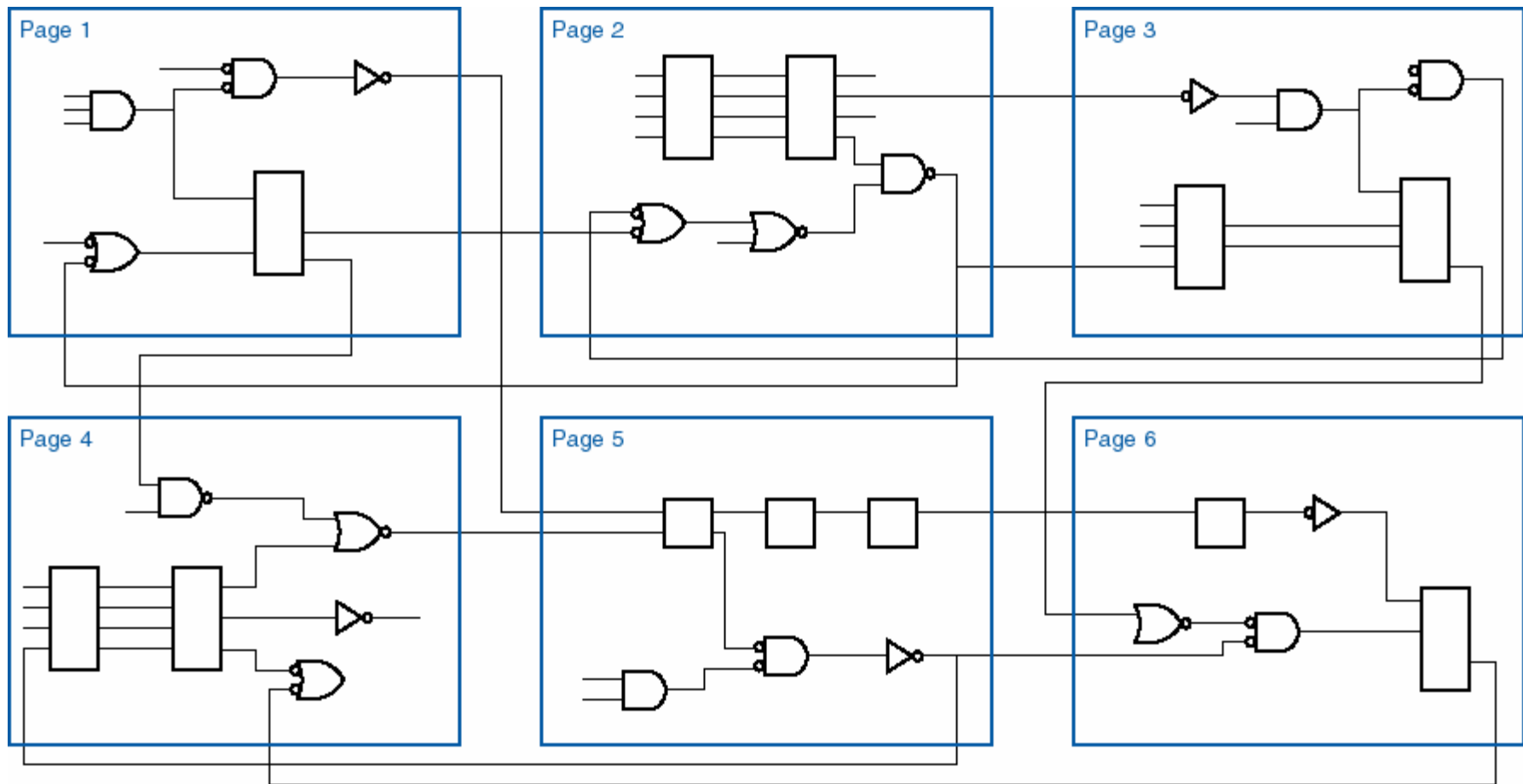

# Hierarchical schematic structure

 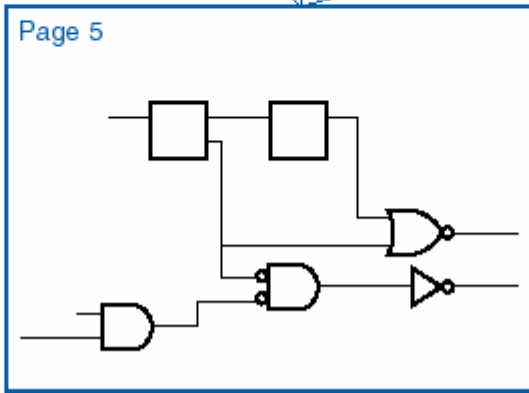  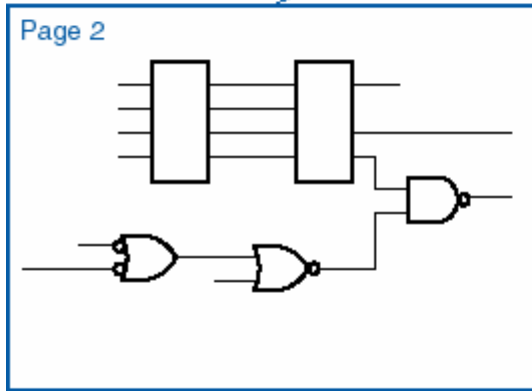 

# Other Documentation

---

## Timing diagrams

- Output from simulator
- Specialized timing-diagram drawing tools

## Circuit descriptions

- Text (word processing)
- Can be as big as a book
- Typically incorporate other elements (block diagrams, timing diagrams, etc.)

# Signal names and active levels


Signal names are chosen to be descriptive.

Active levels -- HIGH or LOW


- named condition or action occurs in either the HIGH or the LOW state, according to the active-level designation in the name.

<i>Active Low</i>	<i>Active High</i>
READY-	READY+
ERROR.L	ERROR.H
ADDR15(L)	ADDR15(H)
RESET*	RESET
ENABLE~	ENABLE
-GO	GO
/RECEIVE	RECEIVE
TRANSMIT_L	TRANSMIT


# Example

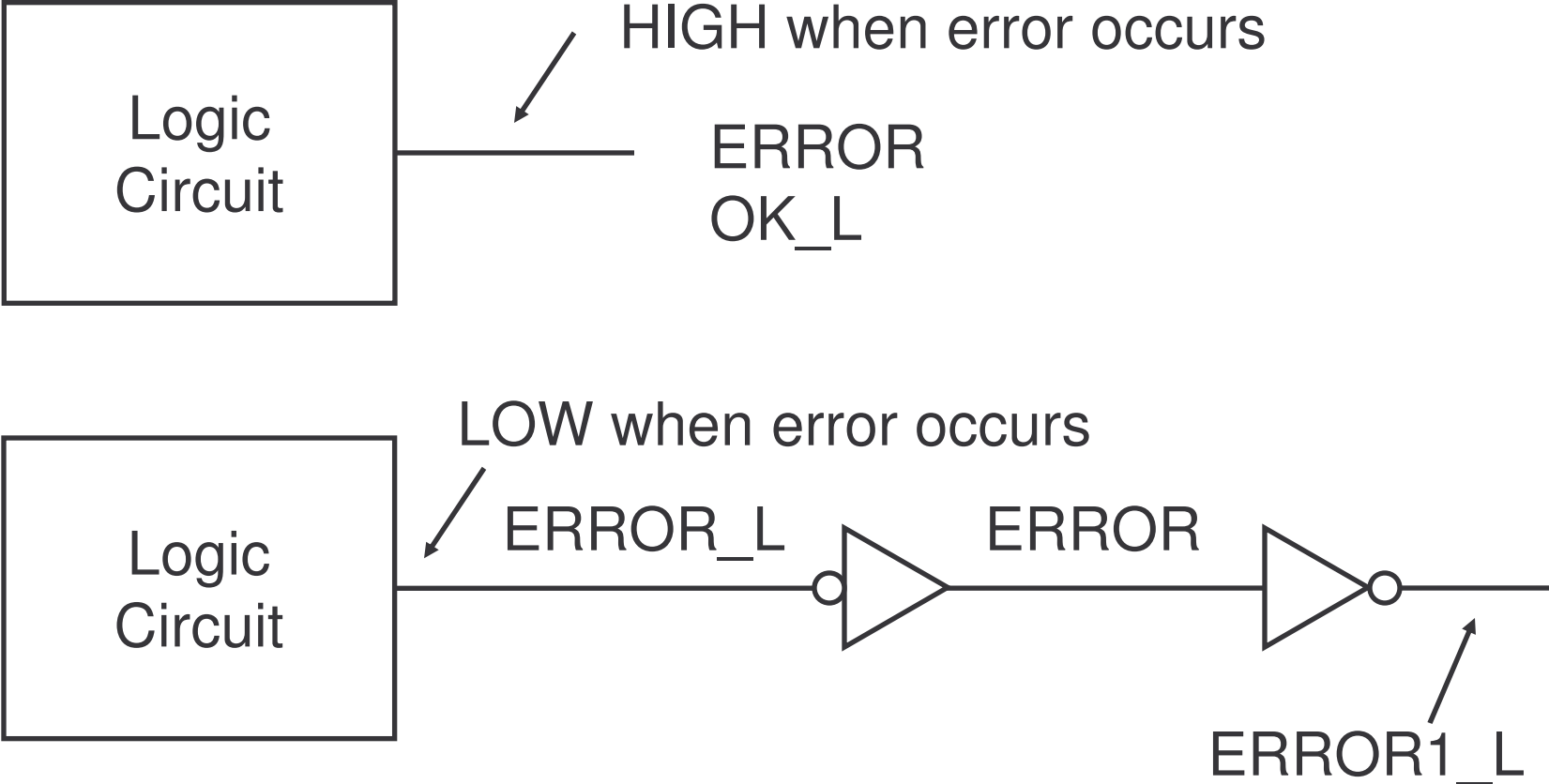



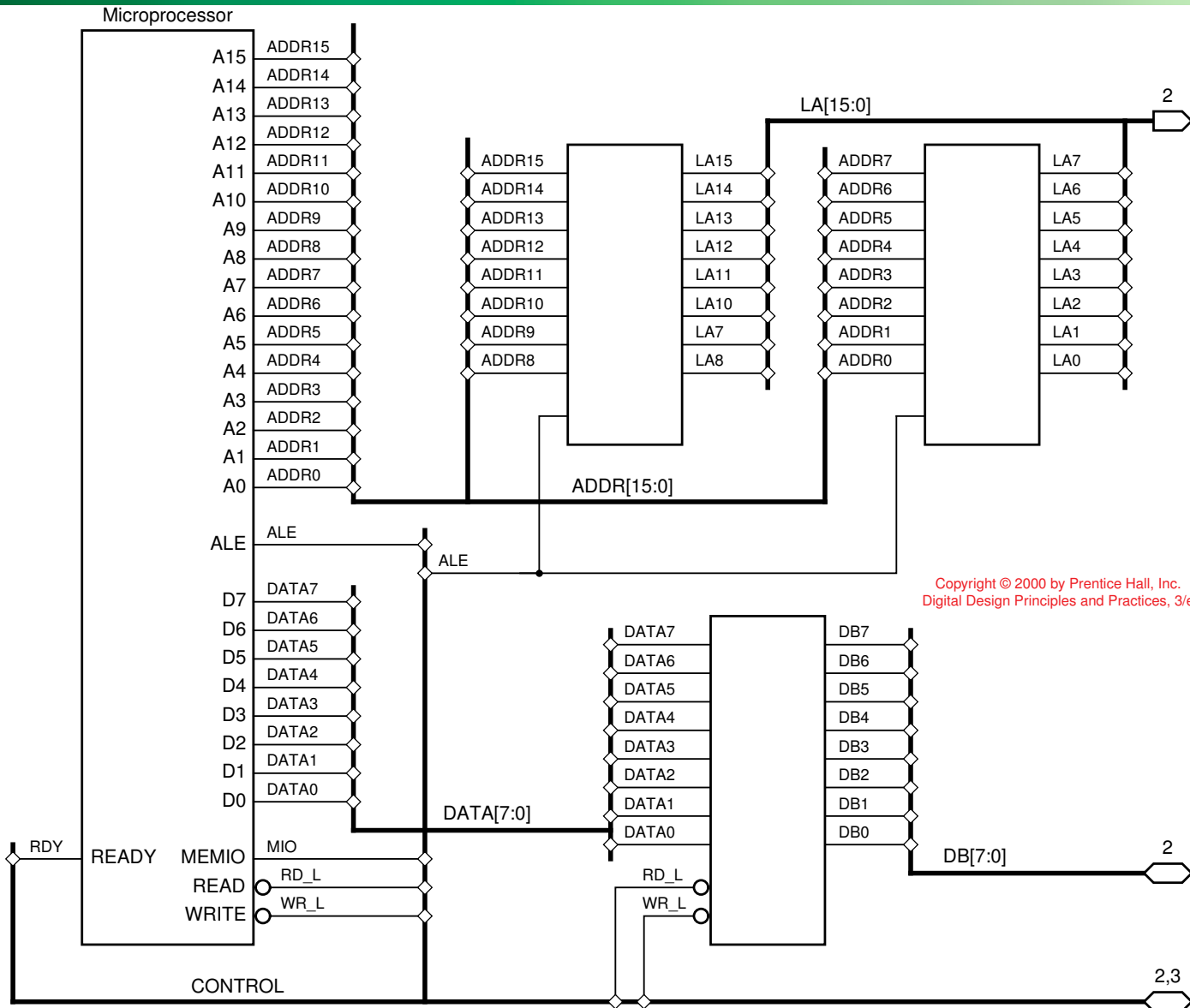


(a)

 



Copyright © 2000 by Prentice Hall, Inc.  
Digital Design Principles and Practices, 3/e

(b)

 


(c)

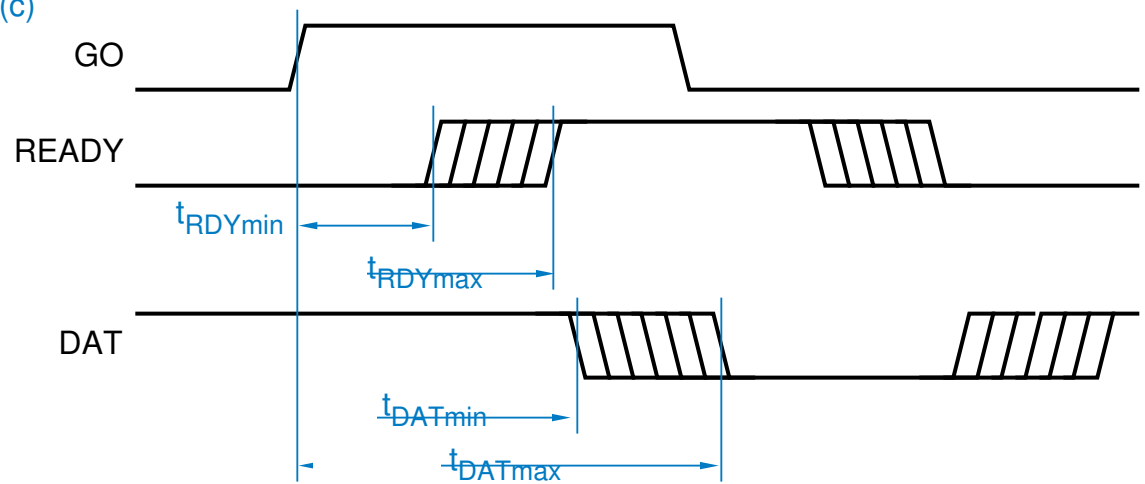

 

 Copyright © 2000 by Prentice Hall, Inc.  
 Digital Design Principles and Practices, 3/e



# Example – Timing Diagram

---


# Programmable Logic Arrays (PLAs)

Any combinational logic function can be realized as a sum of products.

Idea: Build a large AND-OR array with lots of inputs and product terms, and programmable connections.

- $n$  inputs
  - AND gates have  $2n$  inputs -- true and complement of each variable.
- $m$  outputs, driven by large OR gates
  - Each AND gate is programmably connected to each output's OR gate.
- $p$  AND gates ( $p \ll 2^n$ )

# Example: 4x3 PLA, 6 product terms

 

# Programmable Array Logic (PALs)


How beneficial is product sharing?


- Not enough to justify the extra AND array

PALs ==> *fixed* OR array

- Each AND gate is permanently connected to a certain OR gate.

Example: PAL16L8

 

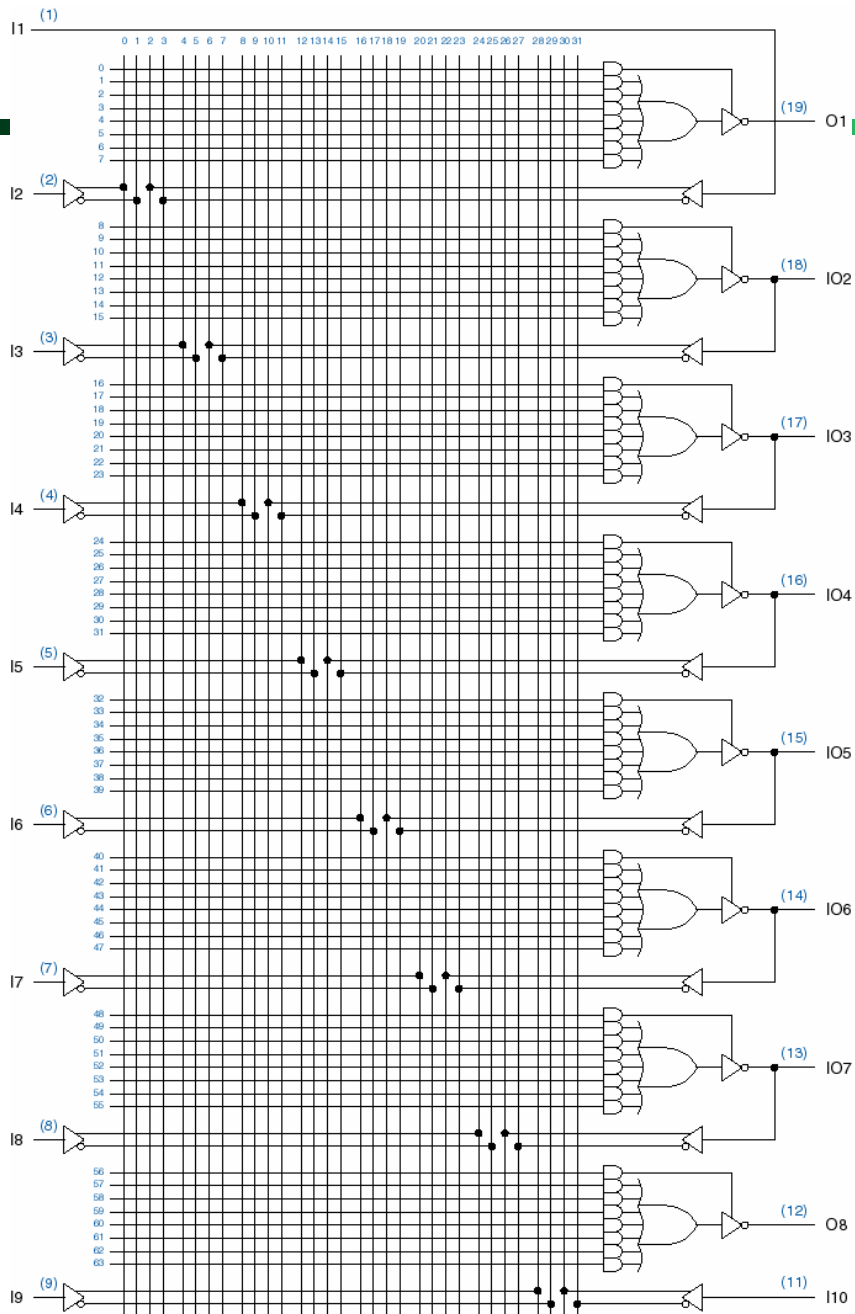

10 primary inputs

8 outputs, with 7 ANDs per output

1 AND for 3-state enable

6 outputs available as inputs

- more inputs, at expense of outputs
- two-pass logic, helper terms

Note inversion on outputs

- output is complement of sum-of-products
- newer PALs have selectable inversion



# Designing with PALs

---

Compare number of inputs and outputs of the problem with available resources in the PAL.


Write equations for each output using HDL.

Compile the HDL program, determine whether minimized equations fit in the available AND terms.

If no fit, try modifying equations.

# Decoders


## General decoder structure

 

Typically  $n$  inputs,  $2^n$  outputs

- 2-to-4, 3-to-8, 4-to-16, etc.


# Binary 2-to-4 decoder

 

<i>Inputs</i>			<i>Outputs</i>			
EN	I1	I0	Y3	Y2	Y1	Y0
0	x	x	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

Note “x” (don’t care) notation.

# 2-to-4-decoder logic diagram

 


# Example: 2-to-4 decoder

## Architecture


```
architecture V2to4dec_s of V2to4dec is
  signal NOTI0, NOTI1: STD_LOGIC;
  component inv port (I: in STD_LOGIC; O: out STD_LOGIC ); end component;
  component and3 port (I0, I1, I2: in STD_LOGIC; O: out STD_LOGIC ); end component;
begin
  U1: inv port map (I0,NOTI0);
  U2: inv port map (I1,NOTI1);
  U3: and3 port map (NOTI0,NOTI1,EN,Y0);
  U4: and3 port map ( I0,NOTI1,EN,Y1);
  U5: and3 port map (NOTI0,  I1,EN,Y2);
  U6: and3 port map (  I0,  I1,EN,Y3);
end V2to4dec_s;
```

↑  
built-in library  
components

 
↑  
positional  
correspondence  
with entity definition



# Decoder Symbol


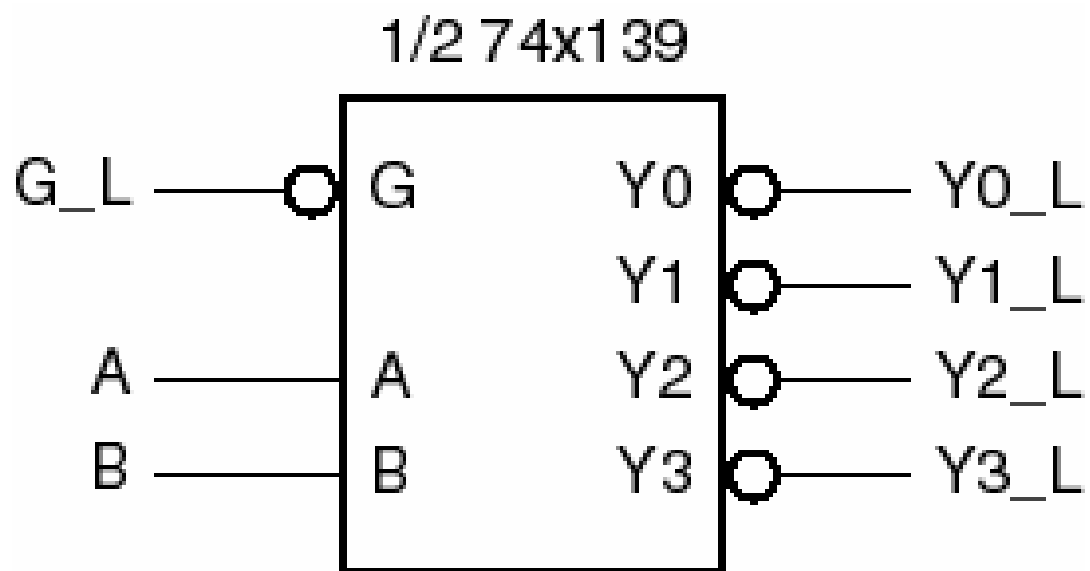


# MSI 2-to-4 decoder

 


Input buffering (less load)  
NAND gates (faster)

# Complete 74x139 Decoder

 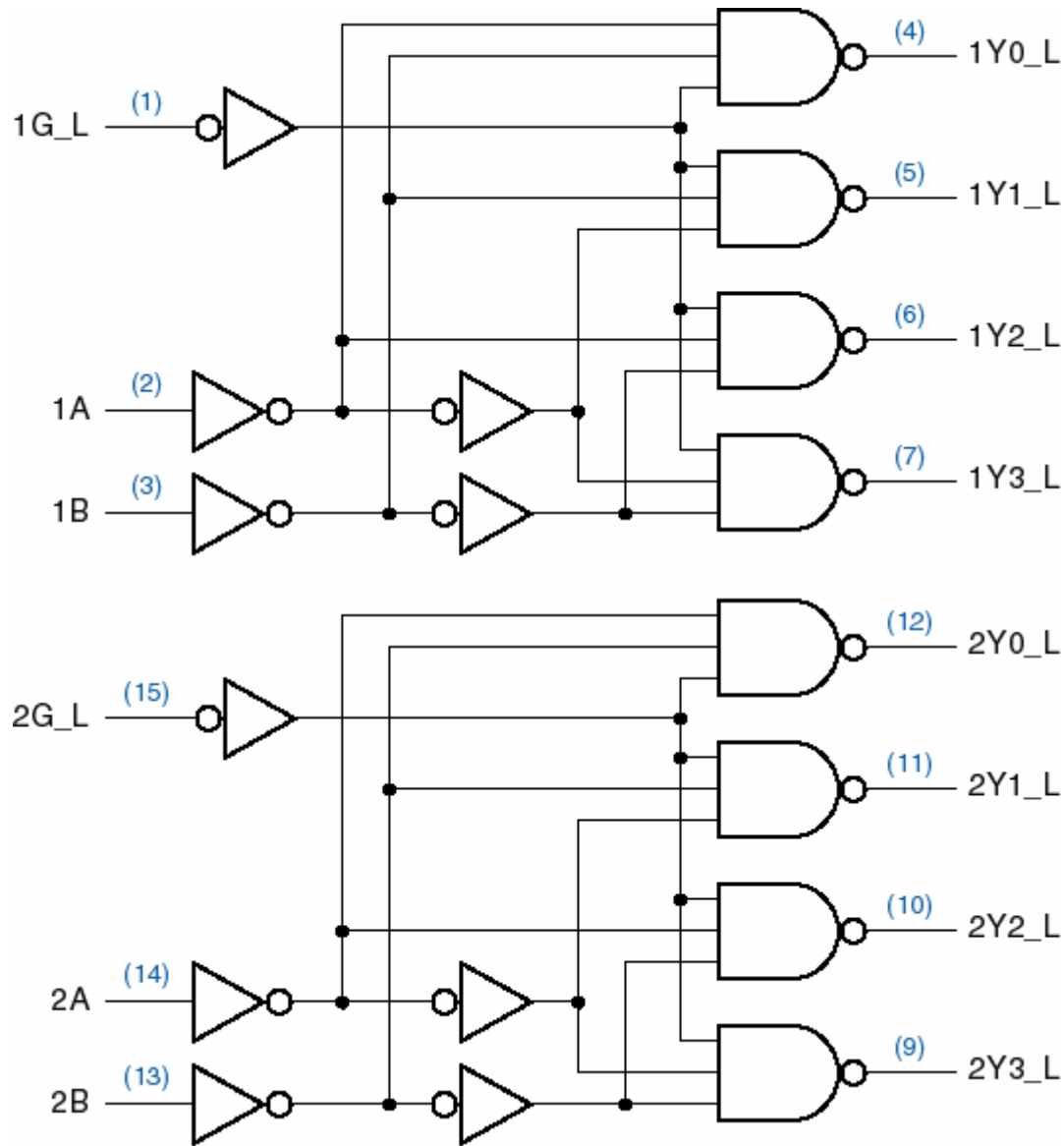




# 3-to-8 decoder

 

# 74x138 3-to-8-decoder symbol

 

# Dataflow-style program for 3-to-8 decoder


```
library IEEE;
use IEEE.std_logic_1164.all;

entity V74x138 is
    port (G1, G2A_L, G2B_L: in STD_LOGIC;           -- enable inputs
          A: in STD_LOGIC_VECTOR (2 downto 0);    -- select inputs
          Y_L: out STD_LOGIC_VECTOR (0 to 7) );   -- decoded outputs
end V74x138;
```

# Dataflow-style program for 3-to-8 decoder


```
architecture V74x138_b of V74x138 is
    signal G2A, G2B: STD_LOGIC;           -- active-high version of inputs
    signal Y: STD_LOGIC_VECTOR (0 to 7);  -- active-high version of outputs
    signal Y_s: STD_LOGIC_VECTOR (0 to 7); -- internal signal
begin
    G2A <- not G2A_L; -- convert inputs
    G2B <- not G2B_L; -- convert inputs
    Y_L <- Y;         -- convert outputs
    with A select Y_s <-
        "10000000" when "000",
        "01000000" when "001",
        "00100000" when "010",
        "00010000" when "011",
        "00001000" when "100",
        "00000100" when "101",
        "00000010" when "110",
        "00000001" when "111",
        "00000000" when others;
    Y <- not Y_s when (G1 and G2A and G2B)='1' else "00000000";
end V74x138_b;
```

# Decoder cascading

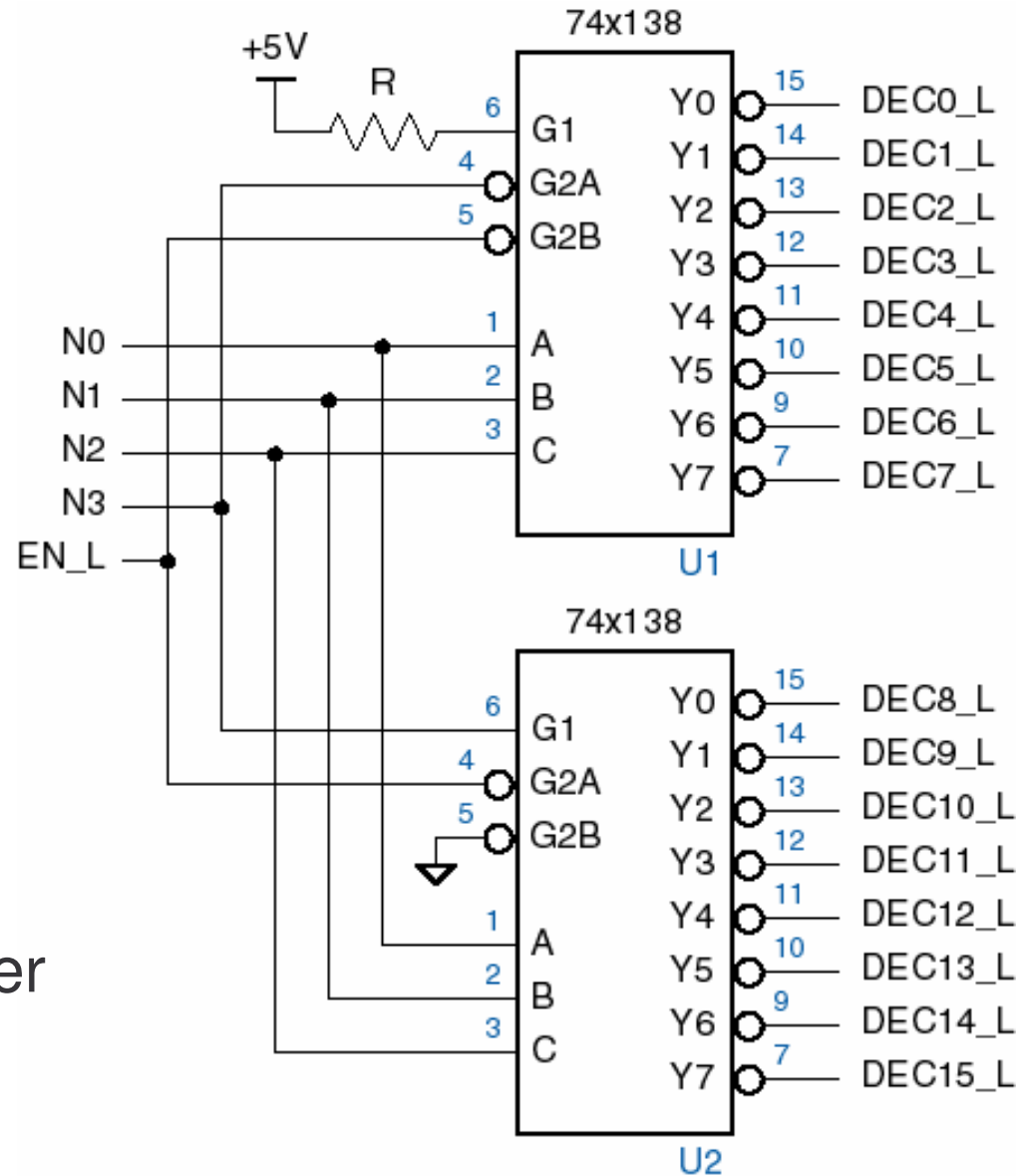

4-to-16 decoder

# More cascading

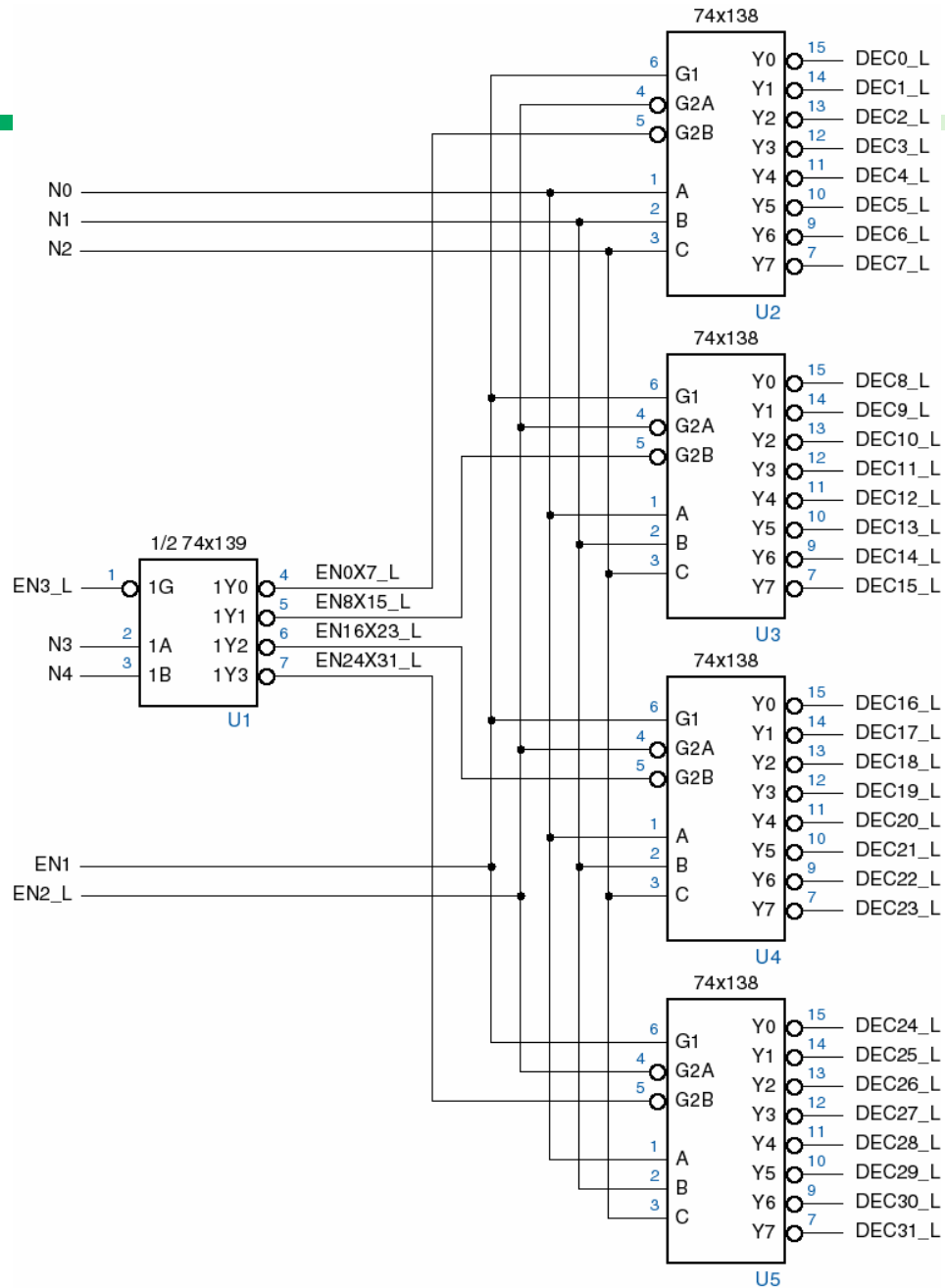

5-to-32 decoder

# Decoder applications

---

## Microprocessor memory systems

- selecting different banks of memory

## Microprocessor input/output systems

- selecting different devices


## Microprocessor instruction decoding

- enabling different functional units

## Memory chips

- enabling different rows of memory depending on address



# Example – Microprocessor Application

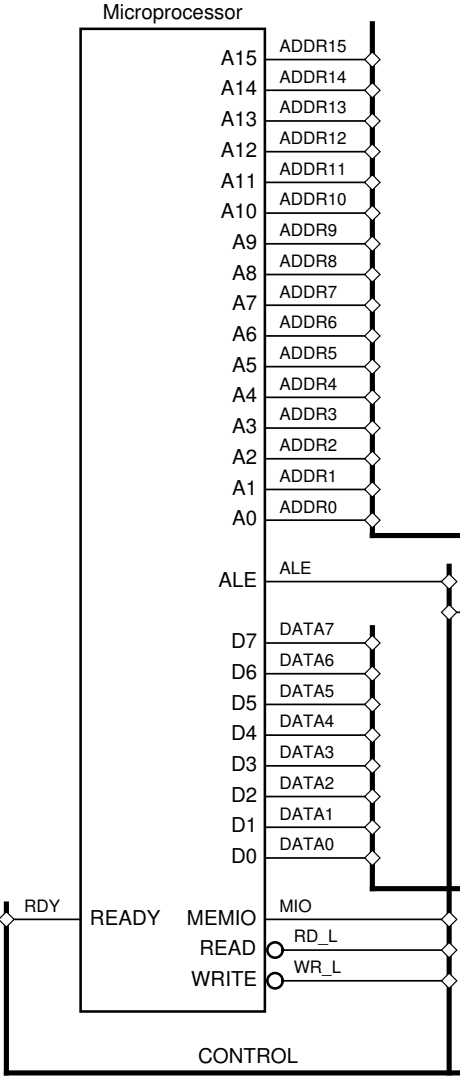





# Encoders vs. Decoders


---

 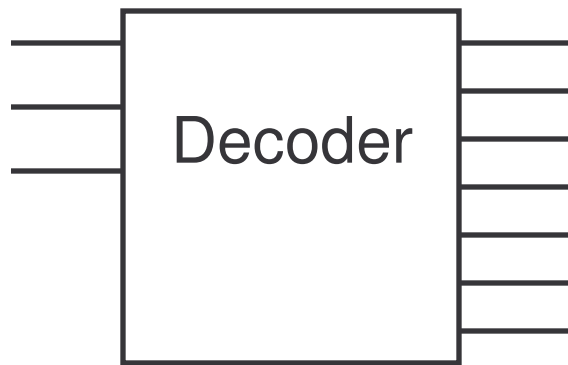


# Binary encoders

 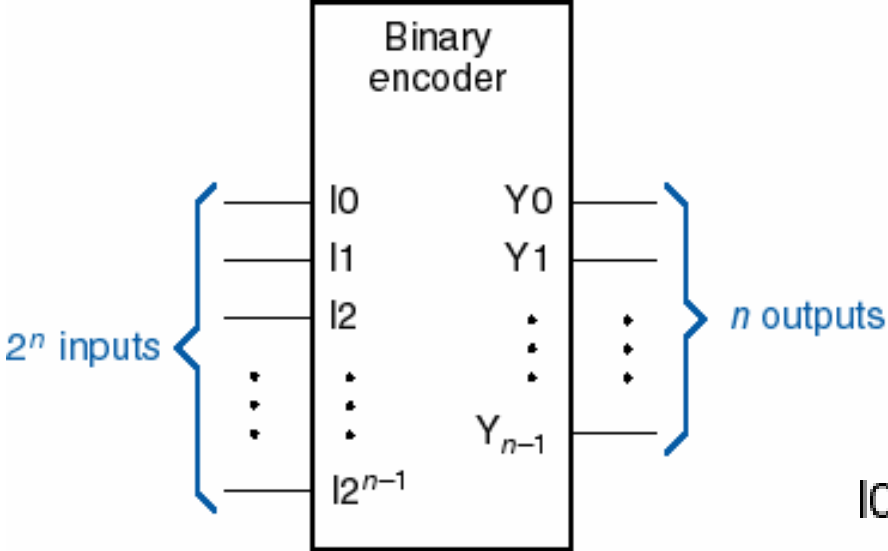

# Need priority in most applications

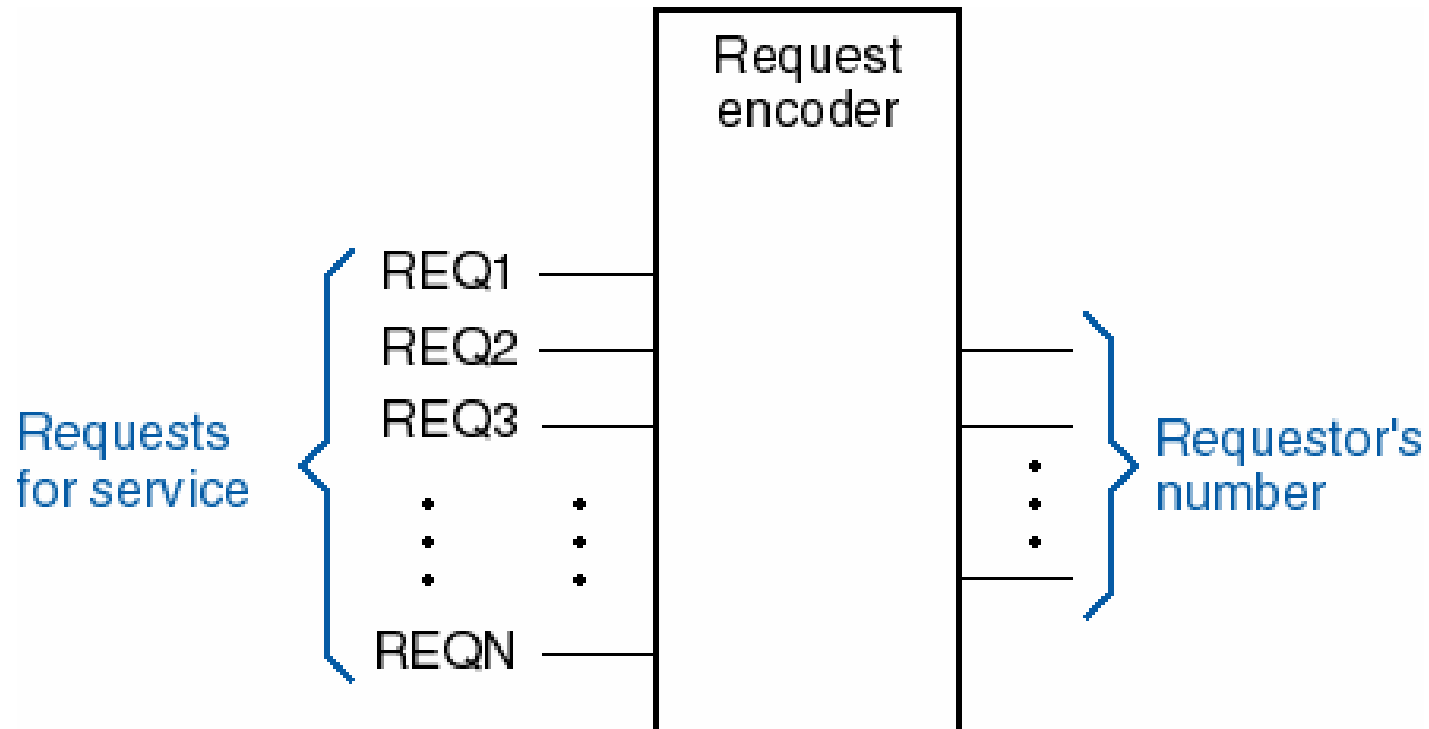

# 8-input priority encoder

 

# Priority-encoder logic equations

$$H7 = I7$$

$$H6 = I6 \cdot I7'$$

$$H5 = I5 \cdot I6' \cdot I7'$$

...

$$H0 = I0 \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$$

$$A2 = H4 + H5 + H6 + H7$$


$$A1 = H2 + H3 + H6 + H7$$

$$A0 = H1 + H3 + H5 + H7$$

$$\text{IDLE} = (I0 + I1 + I2 + I3 + I4 + I5 + I6 + I7)'$$


$$= I0' \cdot I1' \cdot I2' \cdot I3' \cdot I4' \cdot I5' \cdot I6' \cdot I7'$$

# 74x148 8-input priority encoder

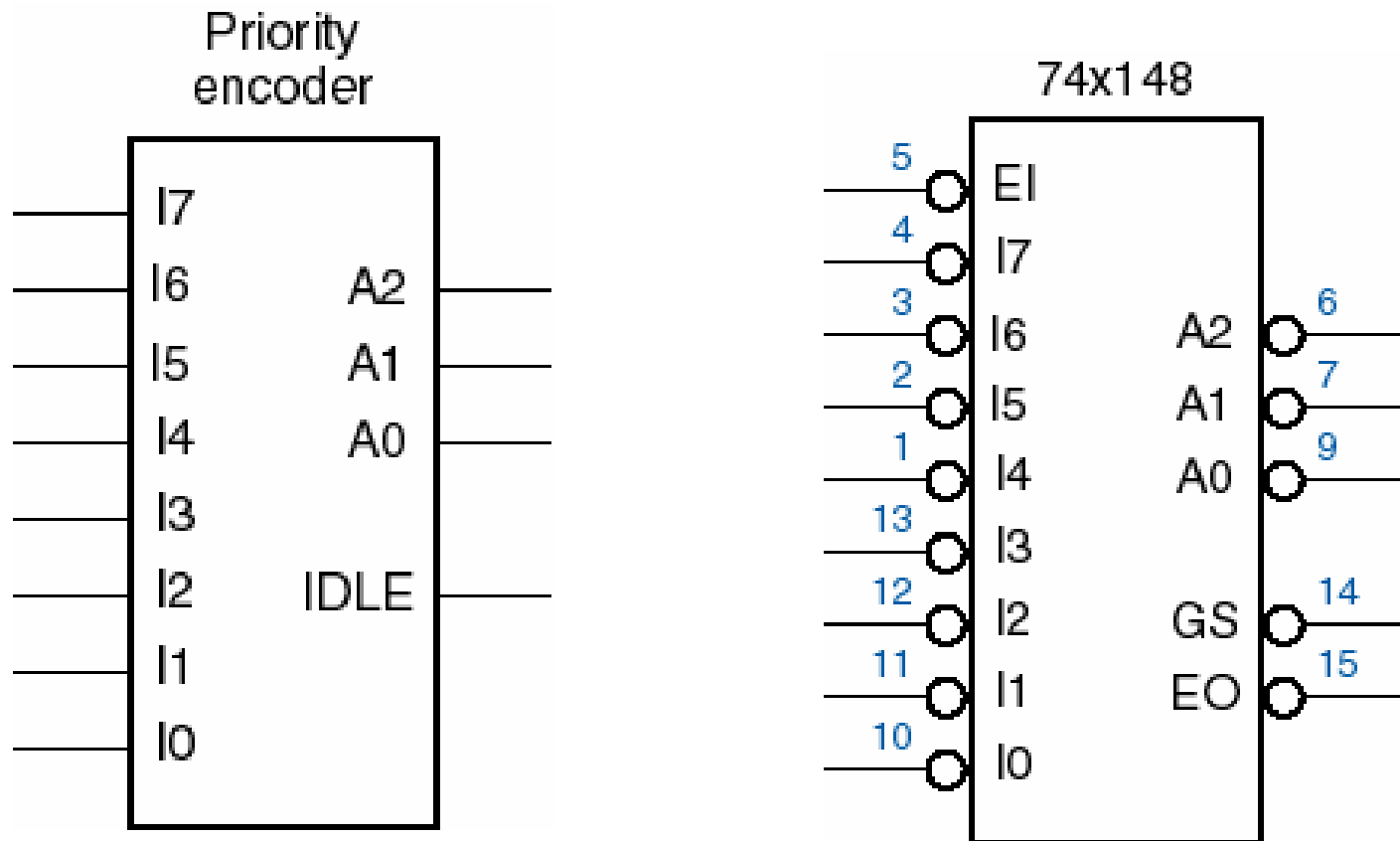

- Active-low I/O
- Enable Input
- “Got Something”
- Enable Output

# 74x148 circuit

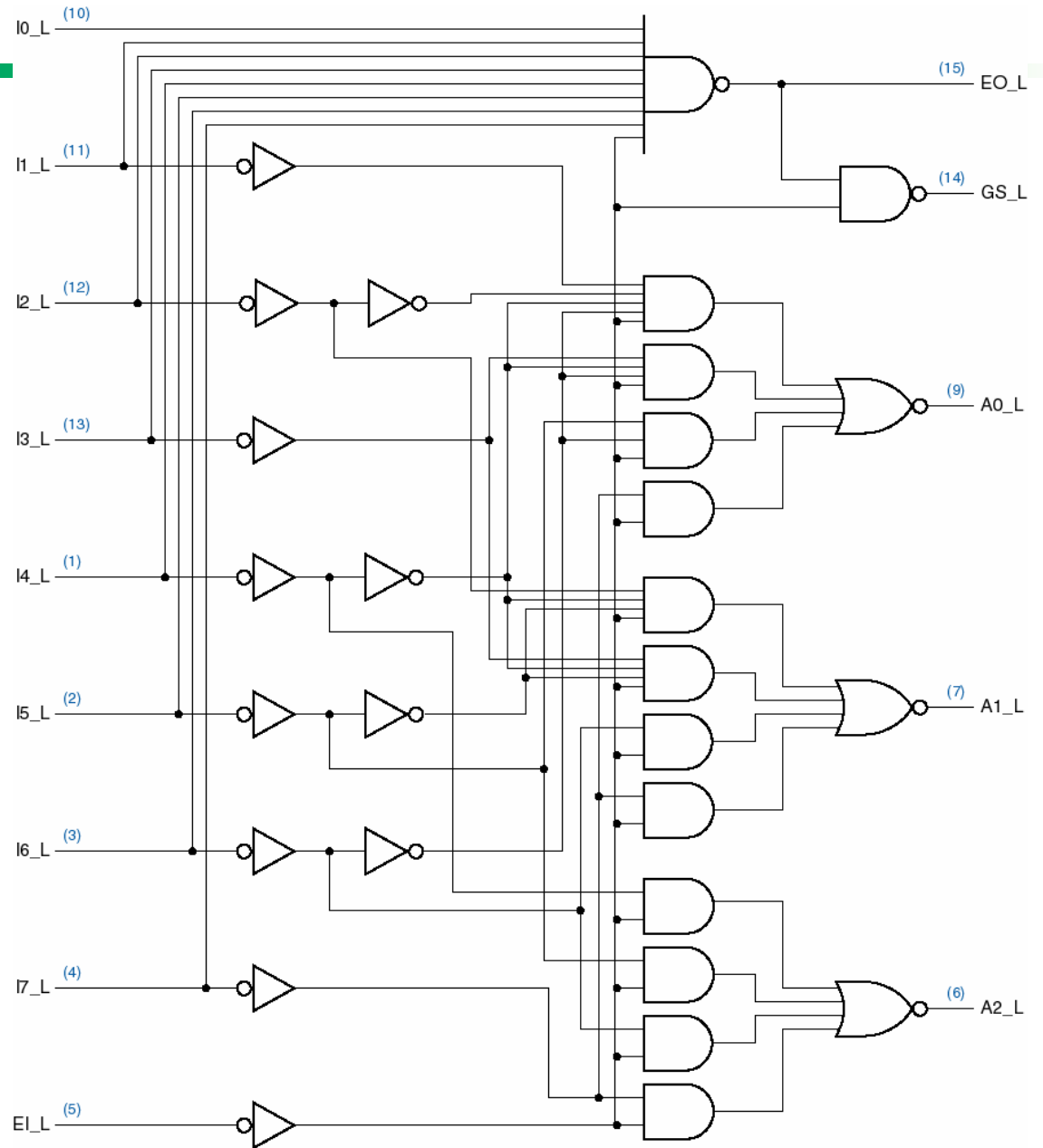


# 74x148 Truth Table

<i>Inputs</i>									<i>Outputs</i>				
E_L	I0_L	I1_L	I2_L	I3_L	I4_L	I5_L	I6_L	I7_L	A2_L	A1_L	A0_L	GS_L	EO_L
1	x	x	x	x	x	x	x	x	1	1	1	1	1
0	x	x	x	x	x	x	x	0	0	0	0	0	1
0	x	x	x	x	x	x	0	1	0	0	1	0	1
0	x	x	x	x	x	0	1	1	0	1	0	0	1
0	x	x	x	x	0	1	1	1	0	1	1	0	1
0	x	x	0	1	1	1	1	1	1	0	1	0	1
0	x	0	1	1	1	1	1	1	1	1	0	0	1
0	0	1	1	1	1	1	1	1	1	1	1	0	1
0	1	1	1	1	1	1	1	1	1	1	1	1	0




# Cascading priority encoders

## 32-input priority encoder

 

# Multiplexers

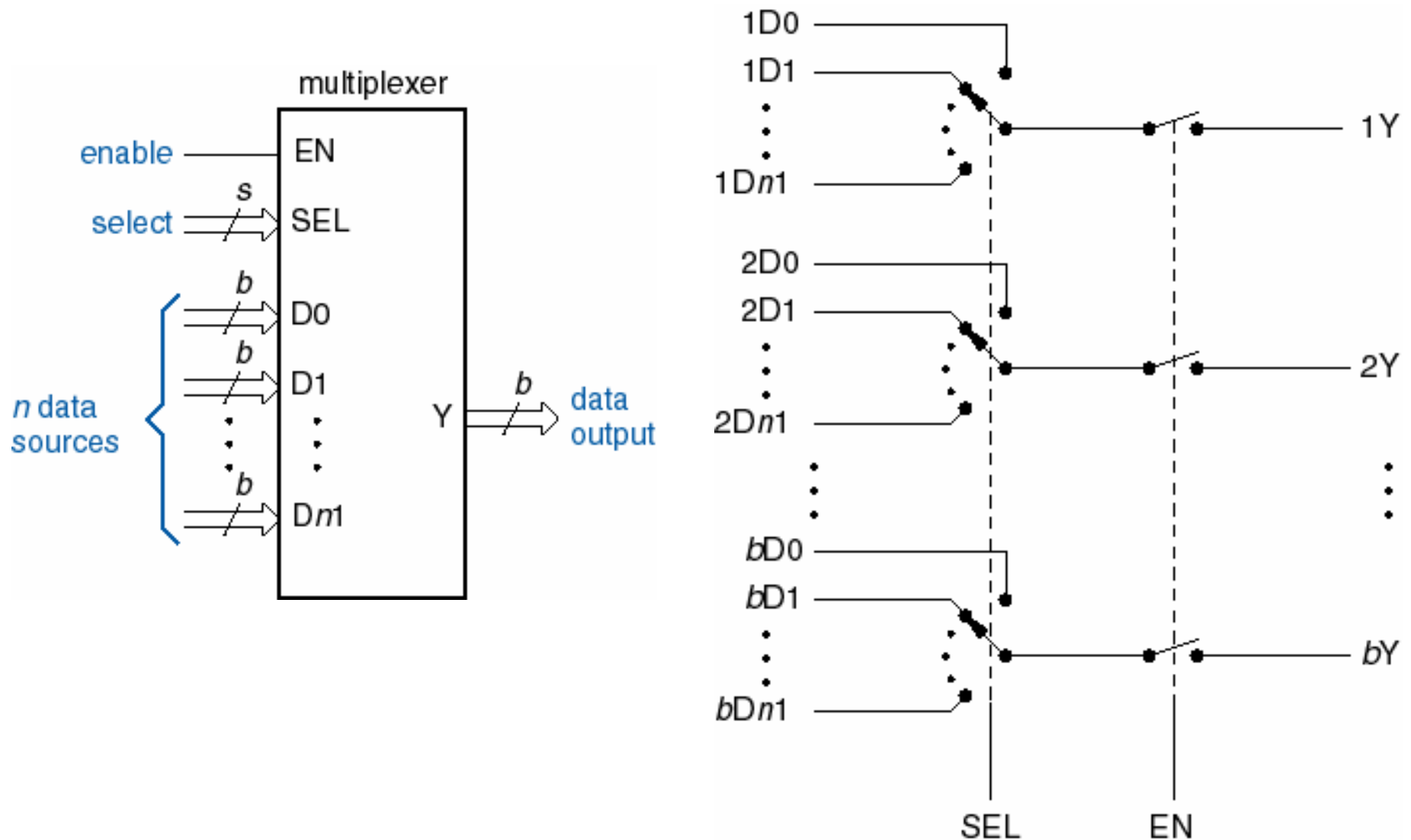

# Multiplexer - Gate-Level Modeling - Verilog

## 2-to-1 Multiplexer

```
// 2-to-1 Multiplexer module
module mux_2 (out, i0, i1, sel);           // header
input i0, i1, sel;                       // input & output ports
output out;
wire x1, x2, x3;                         // internal nets
or (out, x2, x3);                         // form output
and (x2, i0, x1);                         // i0 • sel'
and (x3, i1, sel);                       // i1 • sel
not (x1, sel);                            // invert sel
endmodule
```

# Multiplexer - Dataflow Modeling - Verilog

---

## 4-bit Multiplexer


```
// Four-bit 2-to-1 multiplexer
module mux_4bit (Out, A, B, sel);
input [3:0] A, B;
input sel;
output [3:0] Out;
assign Out = sel ? B, A;
endmodule
```

# Multiplexer - Behavioral Modeling - Verilog

## Conditional Statements

```
module mux4_to_1 (A, B, C, D, OUT, select);
input [7:0] A, B, C, D;
input [1:0] select;
output [7:0] OUT;
reg [7:0] OUT;
always @ (A or B or C or D or select)
case (select)
  2'd0: OUT = A;
  2'd1: OUT = B;
  2'd2: OUT = C;
  2'd3: OUT = D;
endcase
end
```



# 74x151 8-input multiplexer

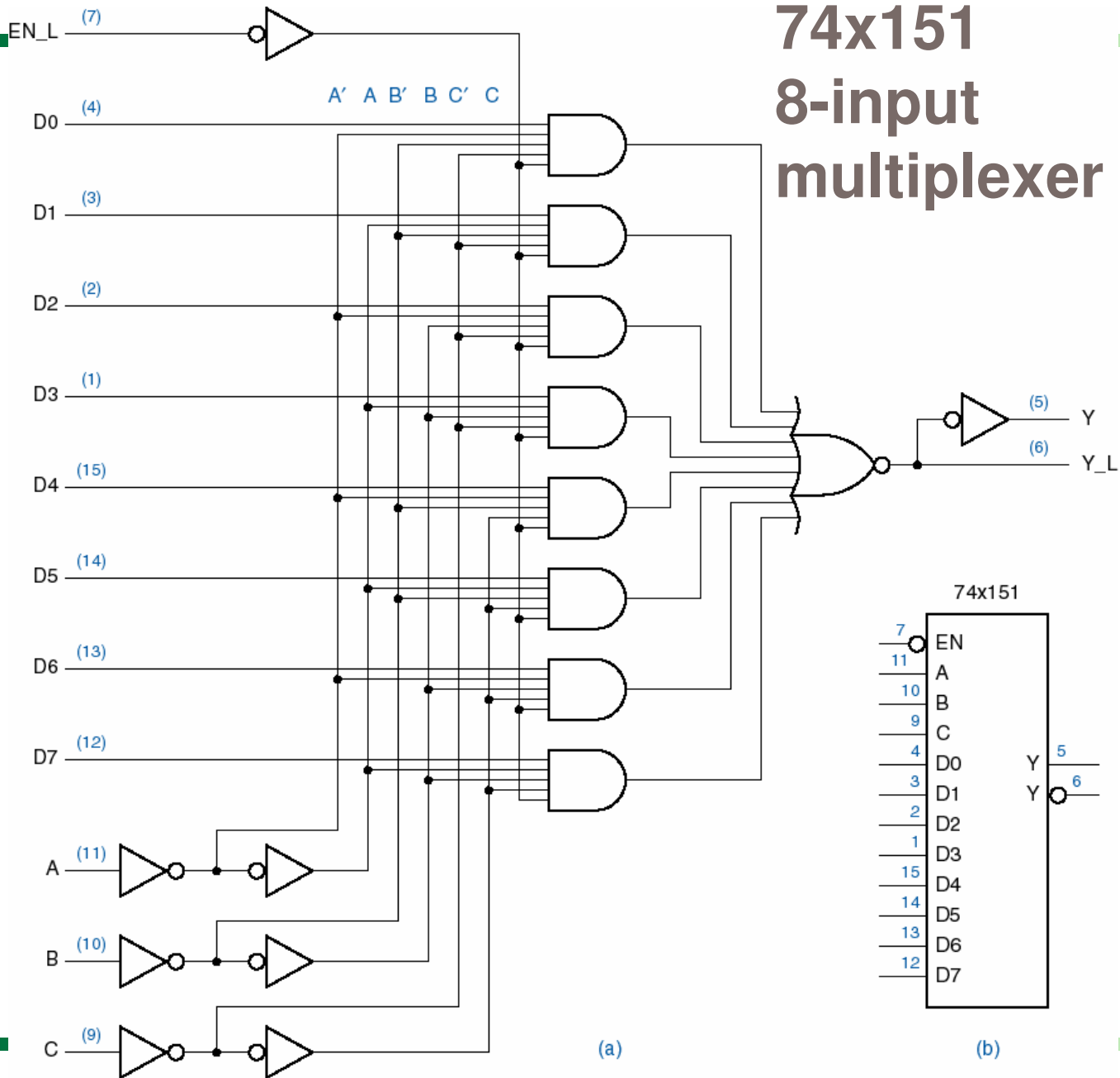

# 74x151 truth table

<i>Inputs</i>				<i>Outputs</i>	
EN_L	C	B	A	Y	Y_L
1	x	x	x	0	1
0	0	0	0	D0	D0'
0	0	0	1	D1	D1'
0	0	1	0	D2	D2'
0	0	1	1	D3	D3'
0	1	0	0	D4	D4'
0	1	0	1	D5	D5'
0	1	1	0	D6	D6'
0	1	1	1	D7	D7'

# CMOS transmission gates

  



## Other multiplexer varieties

2-input, 4-bit-wide  
– 74x157

<i>Inputs</i>		<i>Outputs</i>			
G_L	S	1Y	2Y	3Y	4Y
1	x	0	0	0	0
0	0	1A	2A	3A	4A
0	1	1B	2B	3B	4B

4-input, 2-bit-wide  
– 74x153

# Barrel shifter design example

---

$n$  data inputs,  $n$  data outputs

Control inputs specify number of positions to rotate or shift data inputs


Example:  $n = 16$

- $DIN[15:0]$ ,  $DOUT[15:0]$ ,  $S[3:0]$  (shift amount)


Many possible solutions, all based on multiplexers
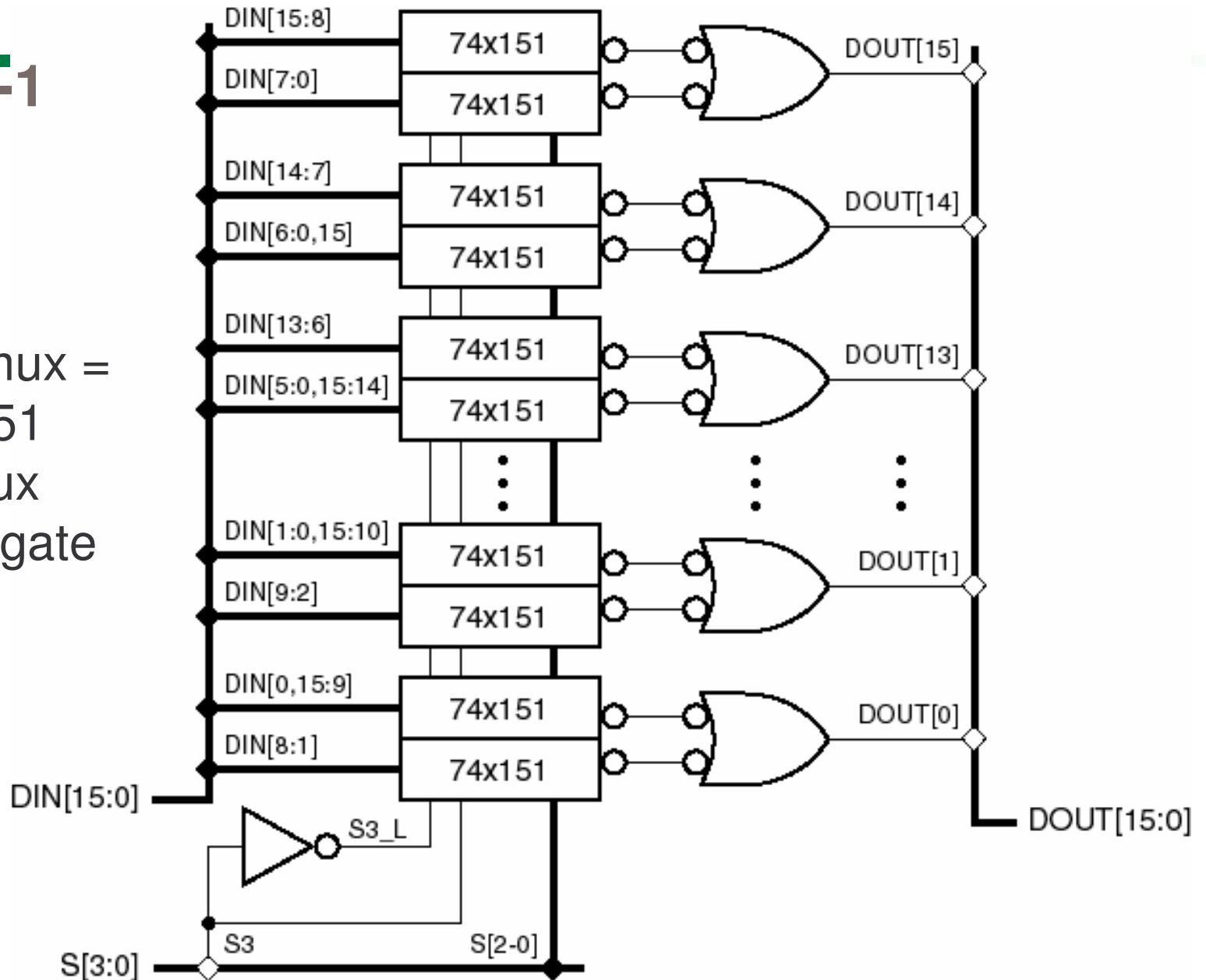
# 16 16-to-1 muxes

16-to-1 mux =  
2 x 74x151  
8-to-1 mux  
+ NAND gate



# 4 16-bit 2-to-1 muxes

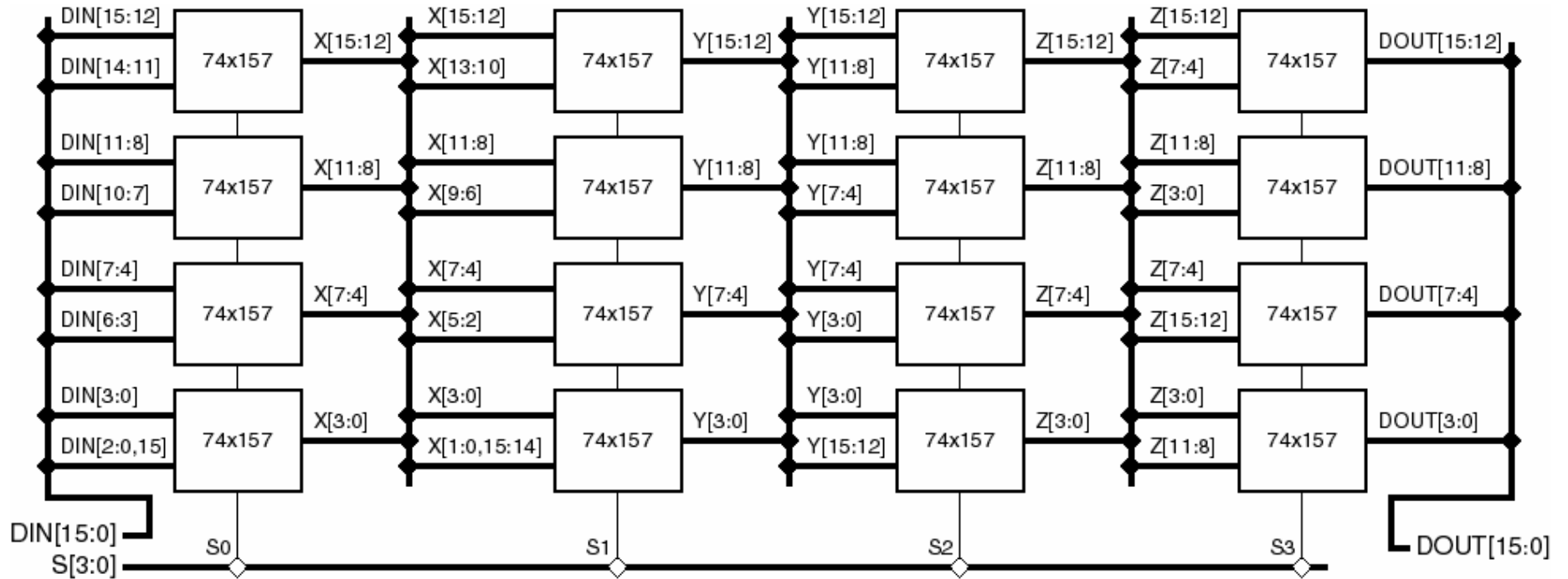

16-bit 2-to-1 mux = 4 x 74x157 4-bit 2-to-1 mux

# Properties of different approaches

<i><b>Multiplexer Component</b></i>	<i><b>Data Loading</b></i>	<i><b>Data Delay</b></i>	<i><b>Control Loading</b></i>	<i><b>Total ICs</b></i>
74x151	16	2	32	36
74x251	16	1	32	32
74x153	4	2	8	16
74x157	2	4	4	16


## 2-input XOR gates

Like an OR gate, but ***excludes*** the case where both inputs are 1.

$X$	$Y$	$X \oplus Y$ (XOR)	$(X \oplus Y)'$ (XNOR)
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1



XNOR: complement of XOR

# XOR and XNOR symbols

 
  
# Gate-level XOR circuits


No direct realization with just a few transistors.






# Equality Comparators



1-bit comparator

 


4-bit comparator

 

# 8-bit Magnitude Comparator

 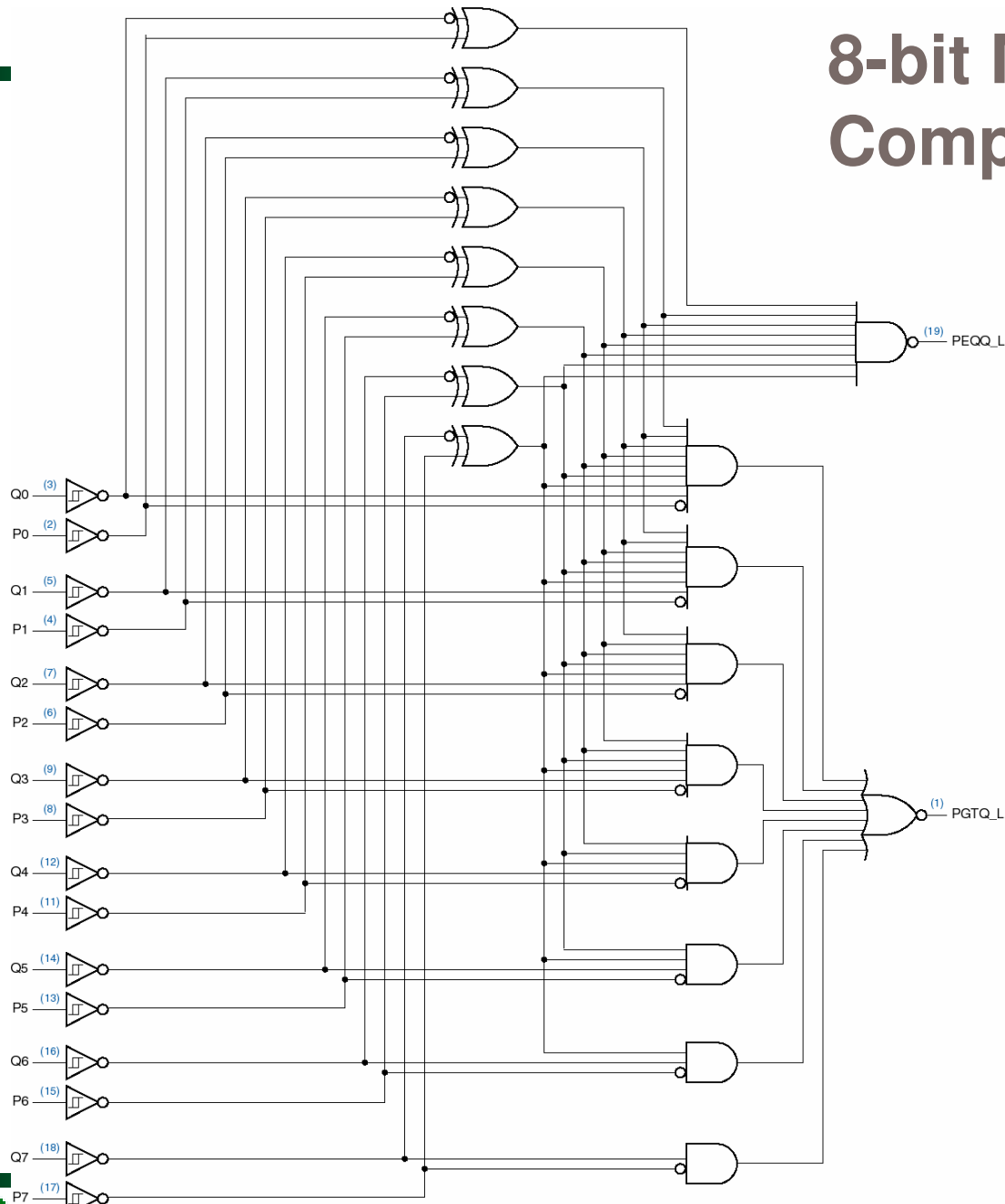

# Other conditions

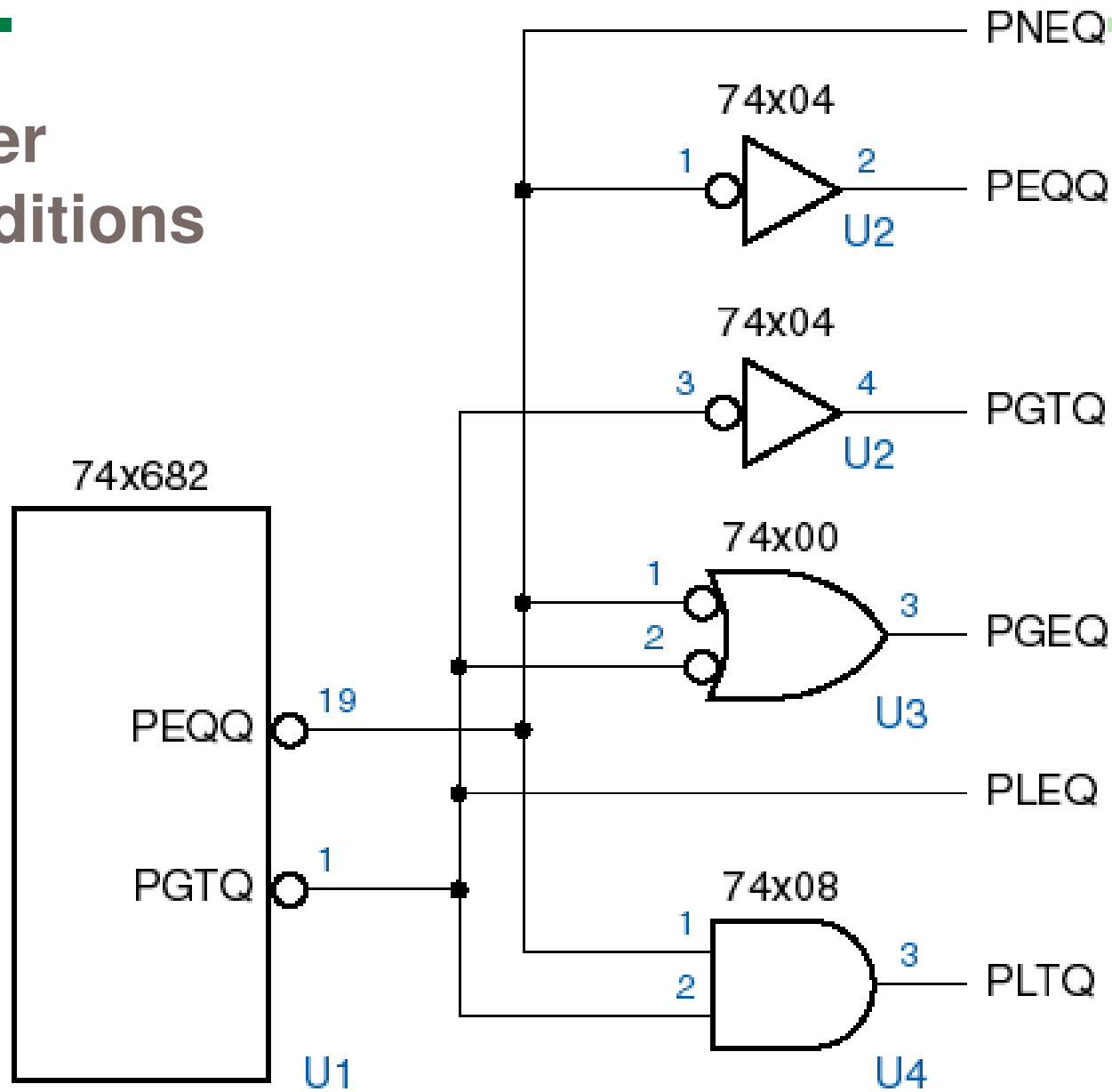

# Adders


Basic building block is “full adder”

- 1-bit-wide adder, produces sum and carry outputs


Truth table:

X	Y	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

# Full-adder circuit

 

# Ripple adder

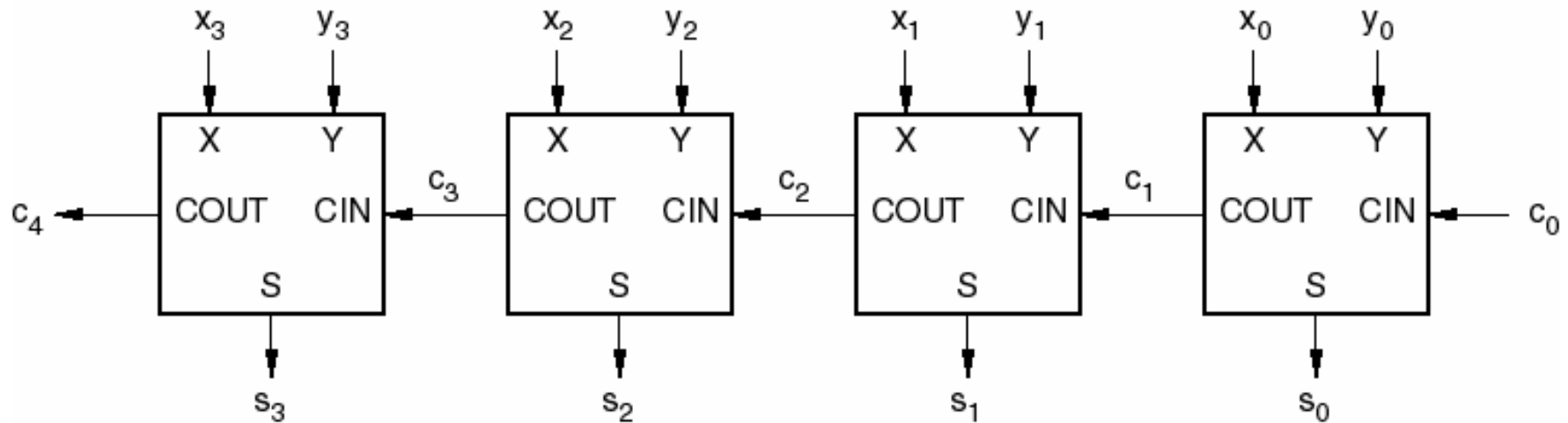


Faster adders eliminate or limit carry chain


- 2-level AND-OR logic ==>  $2^n$  product terms
- 3 or 4 levels of logic, carry lookahead

# 74x283

## 4-bit adder


Uses carry  
lookahead  
internally

 


 




# Ripple carry between groups

 

# Lookahead carry between groups

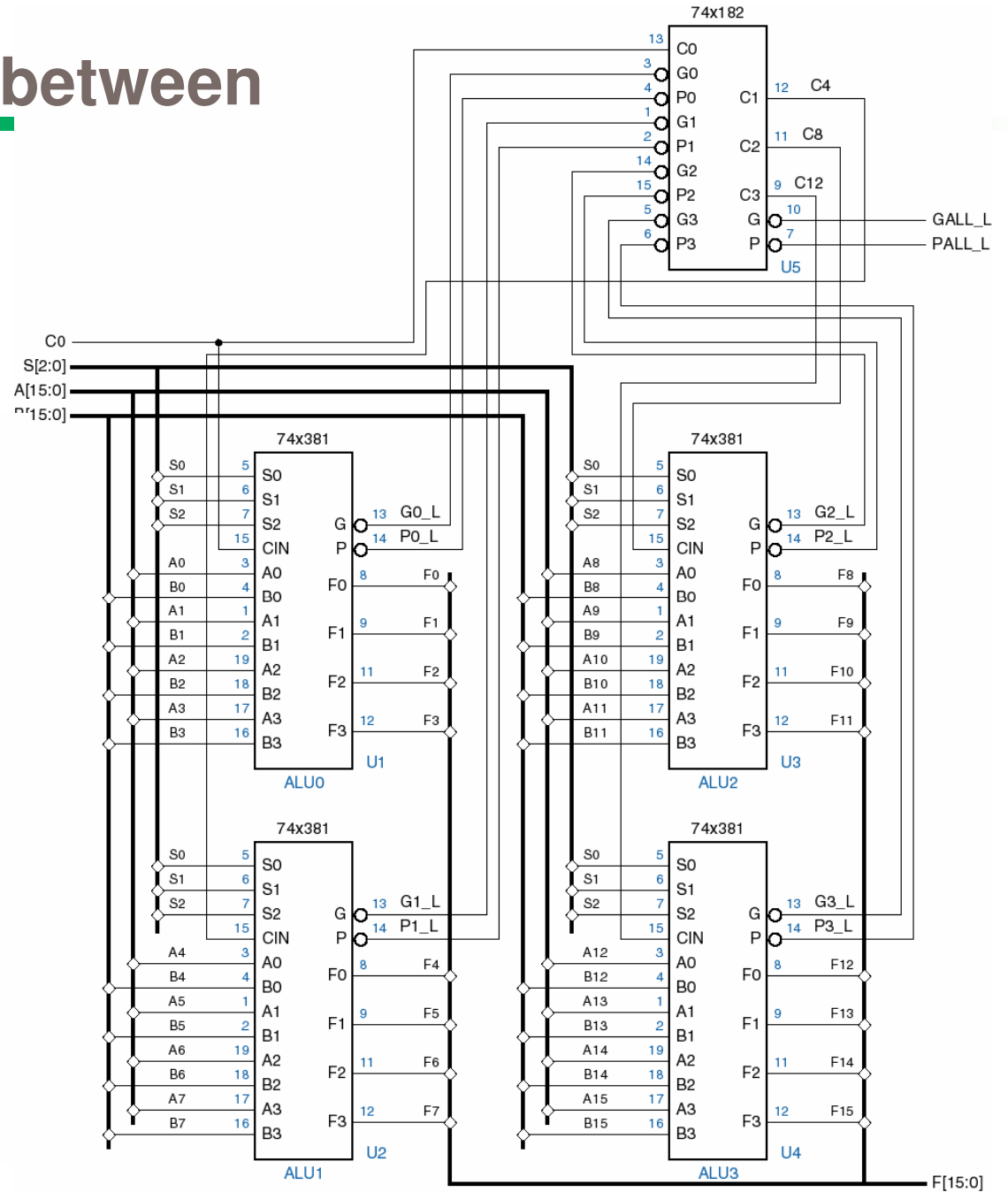 

# Subtraction

---

Subtraction is the same as addition of the two's complement.



The two's complement is the bit-by-bit complement plus 1.

Therefore,  $X - Y = X + Y + 1$  .

- Complement Y inputs to adder, set  $C_{in}$  to 1.
- For a borrow, set  $C_{in}$  to 0.


—

# Full subtractor = full adder, almost

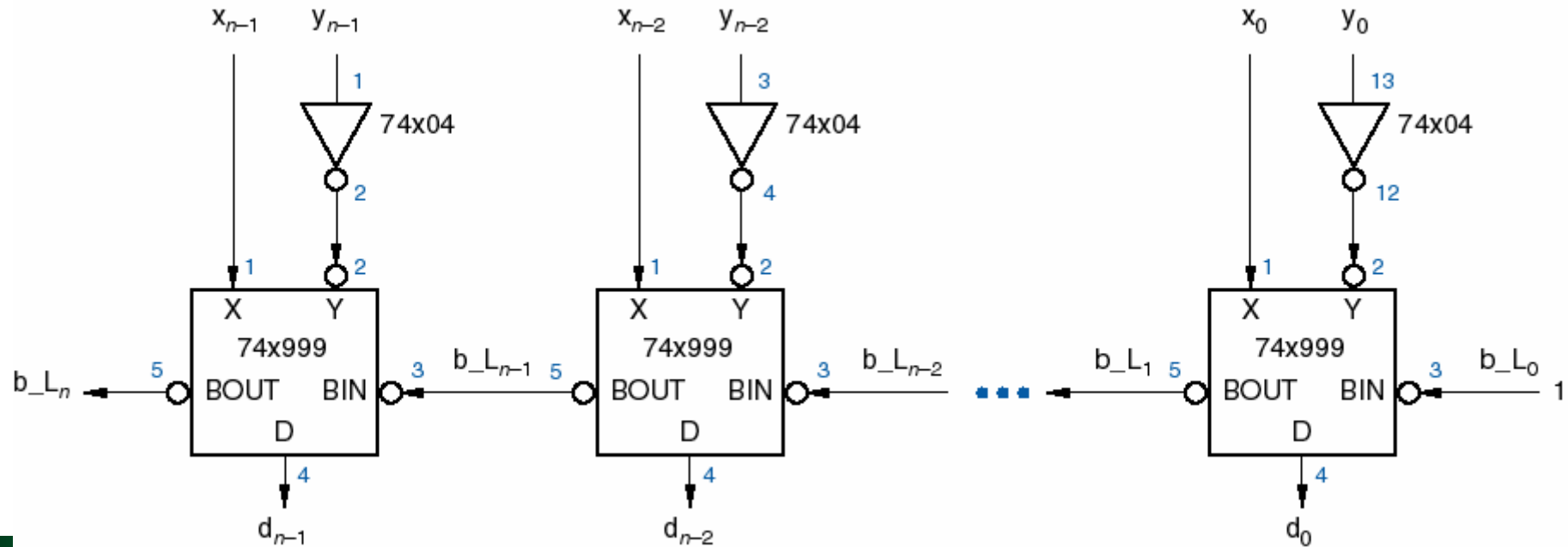 


# Multipliers

## 8x8 multiplier

 

# Full-adder array

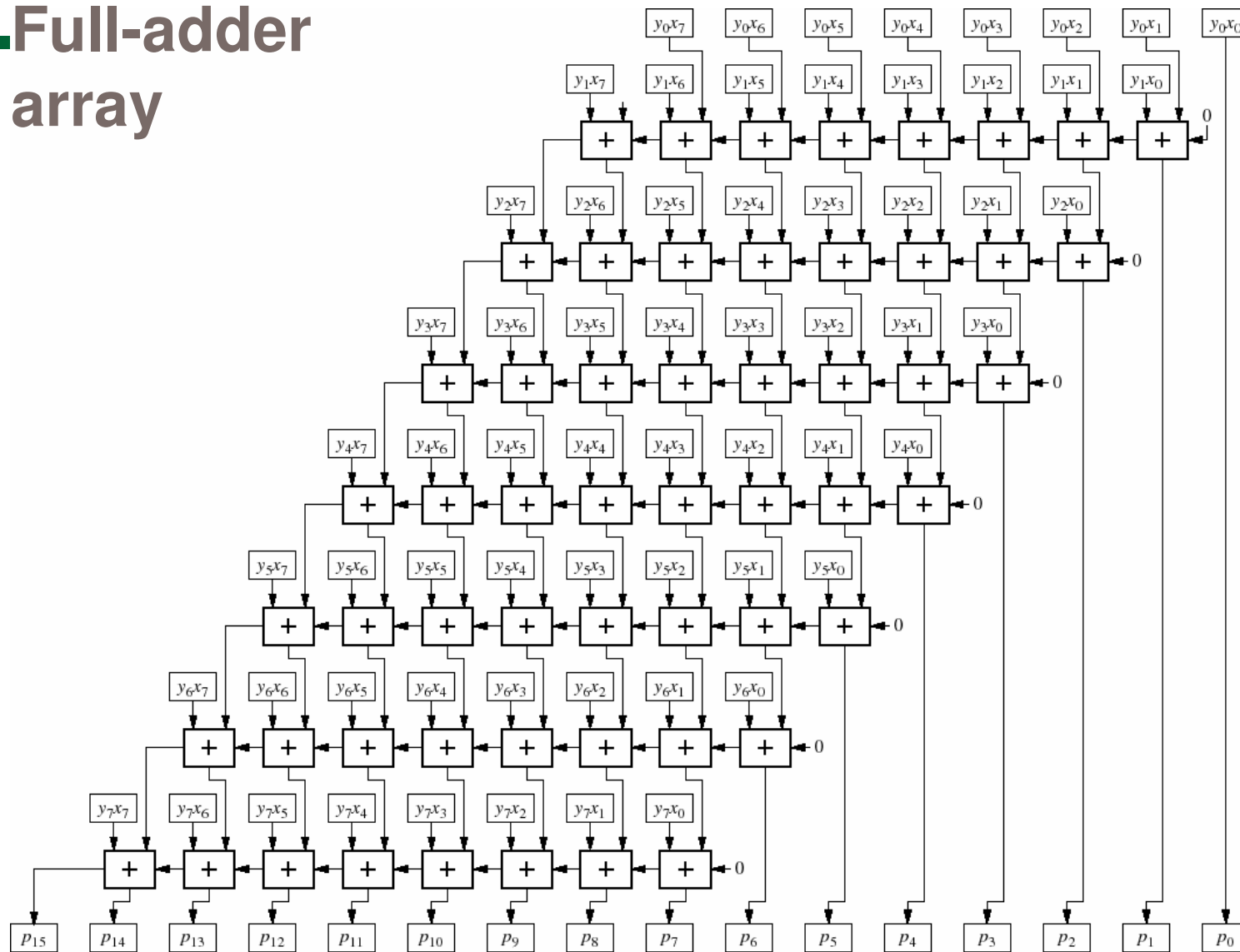

# Faster carry chain

