 





# More Digital Design

ECGR2181




*Reading:* Chapter 9.1

# Memory Hierarchy

 

# View of Computer System

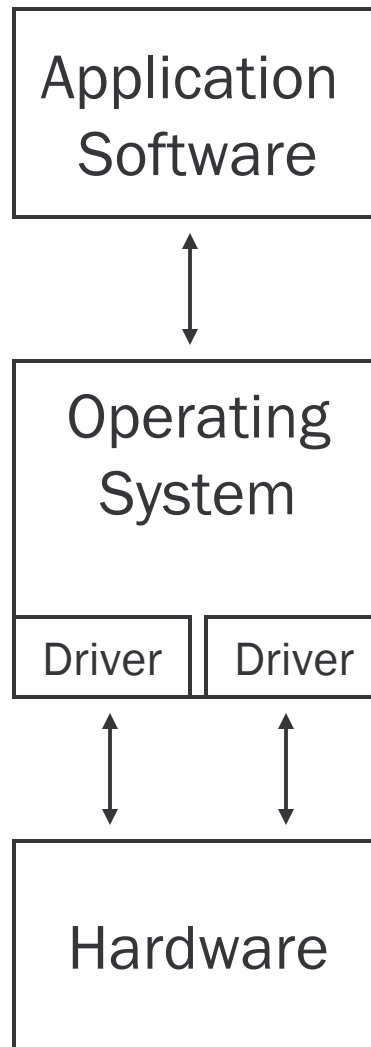


# Memory

To build a memory -- a logical  $k \times m$  array of stored bits.

**Address Space:**  
number of locations  
(usually a power of 2)


$k = 2^n$   
locations

 

**Addressability:**  
number of bits per location  
(e.g., byte-addressable)

$m$  bits

# 2<sup>2</sup> x 3 Memory

 

# More Memory Details

---

This is not the way actual memory is implemented.

- fewer transistors, much more dense, relies on electrical properties

But the logical structure is very similar.

- address decoder
- word select line
- word write enable

Two basic kinds of memory (RAM = Random Access Memory)

Static RAM (SRAM)

- fast, maintains data without power refresh

Dynamic RAM (DRAM)

- slower but denser, bit storage must be periodically refreshed

# Even More Memory Details

---

There are other types of “non-volatile” memory devices:

- ROM
- PROM
- EPROM
- EEPROM
- Flash

Can you think of other memory devices?

# Electronics Packaging


---

- There are several packaging technologies available that an engineer can use to create electronic devices.
- Some are suitable for inexpensive toys but not miniature consumer products, and some are suitable for miniature consumer products but not inexpensive toys.
- These packages have metal leads that are the conductive wire that connect electricity from the outside world to the silicon inside the package.
- Leads between packages are connected with small copper traces on a printed circuit board (PCB), and the package leads are soldered to the PCB.



 
# Examples of Electronics Packages

Dual In-line Package (DIP) Older technology, requires the metal leads to go through a hole in the printed circuit board.




 Dual Flat Pack (DFP) - A fairly recent technology, metal leads solder to the surface of the printed circuit board.



 
# Examples of Electronics Packages


Quad Flat Pack (QFP) - like the Dual Flat Pack, except here are metal leads are on four sides.



 Ball Grid Array (BGA) - The connections to the component are on the bottom of the chip, and have balls of solder on these connections.


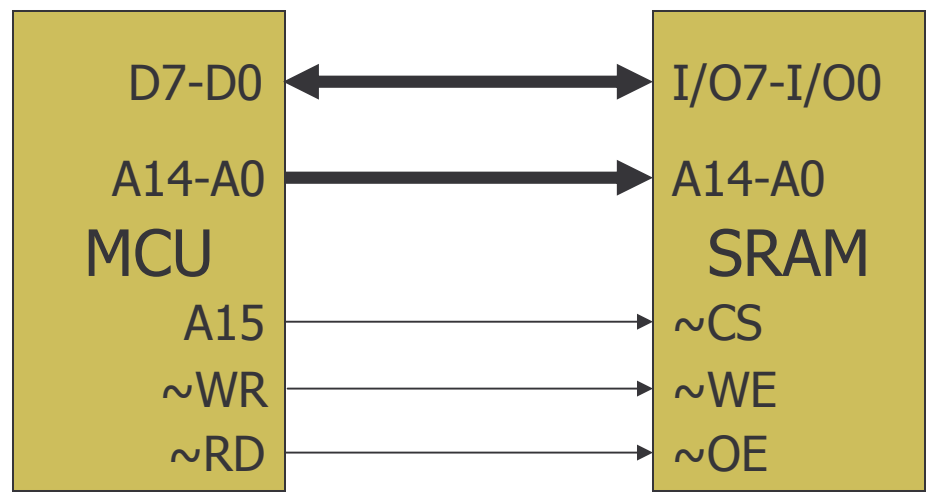
# External Memory Access – Separate Buses




## Chip Select


- Partial vs. Full Decoding
- Power Consumption

*Read*


*Write*

 

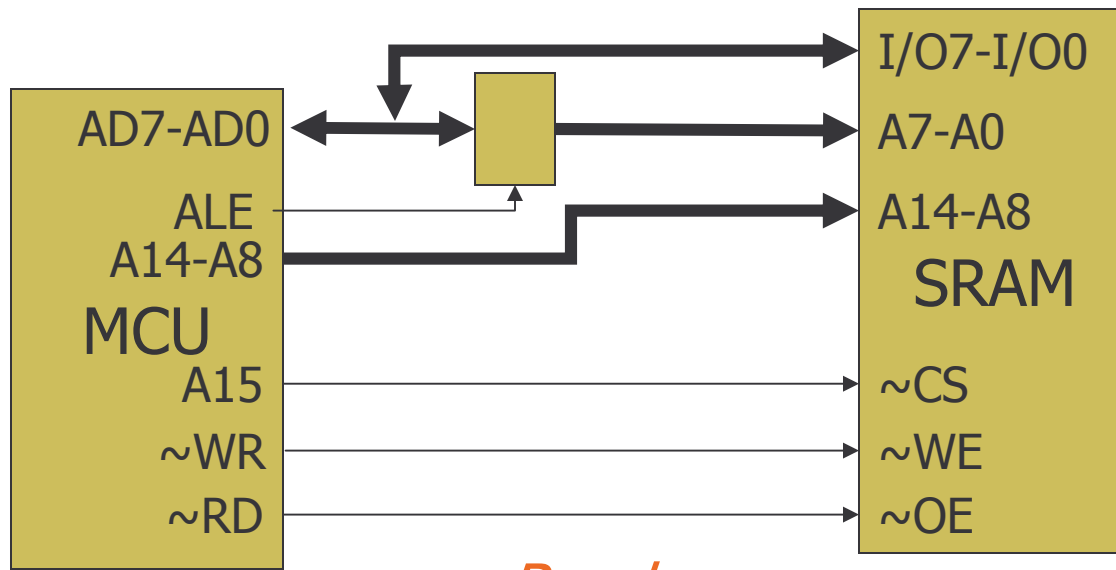
# External Memory Access – Multiplexed Buses



 Use a latch to hold the low byte of the address  
Saves pins



# Multiple External Memories

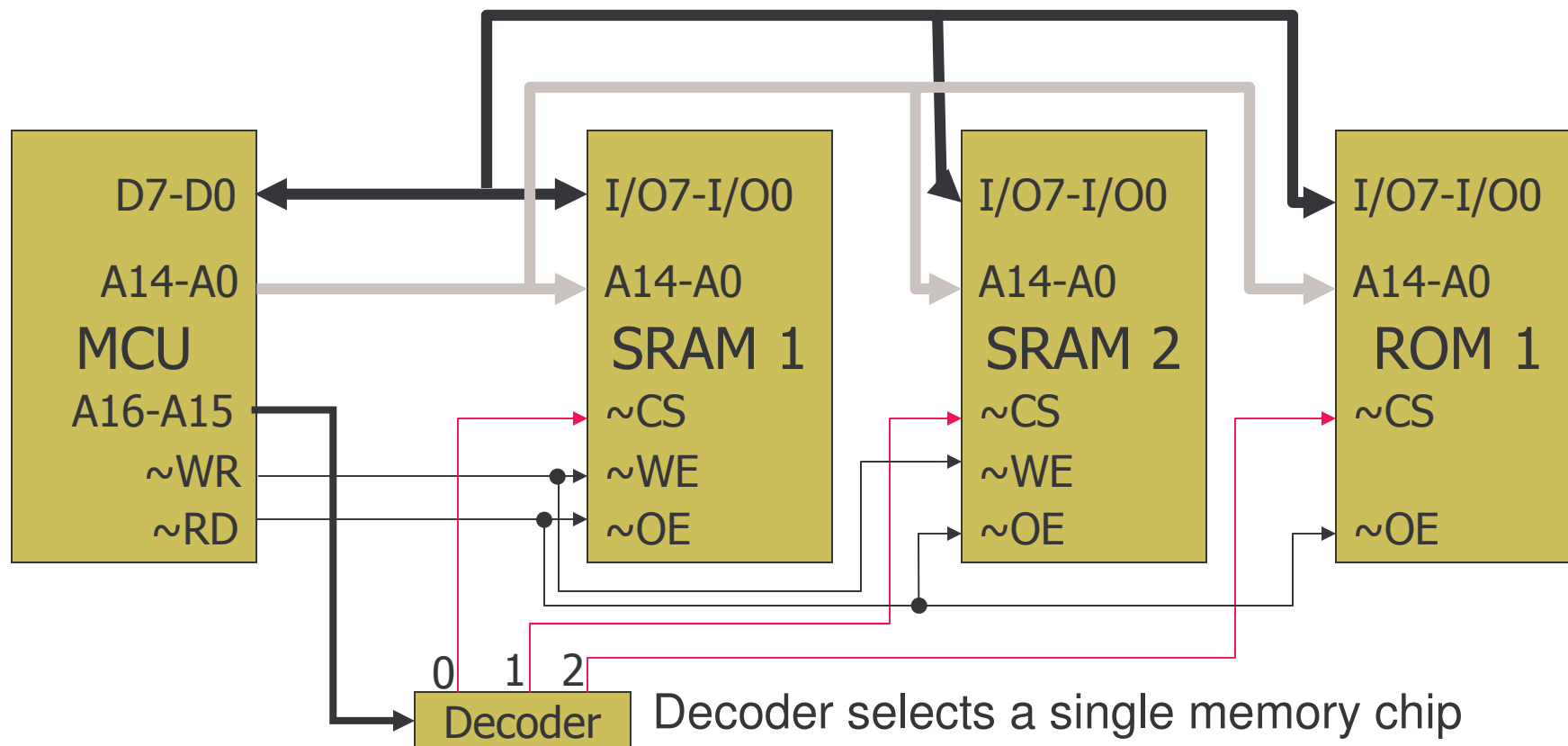


Decoder selects a single memory chip

- Output 0 active when A16:A15 = 00. Address = 0 0xxx xxxx xxxx xxxx = 00000h to 07FFFh
- Output 1 active when A16:A15 = 01. Address = 0 1xxx xxxx xxxx xxxx = 08000h to 0FFFFh
- Output 2 active when A16:A15 = 10. Address = 1 0xxx xxxx xxxx xxxx = 10000h to 17FFFh

# IDT71256L Read Timing

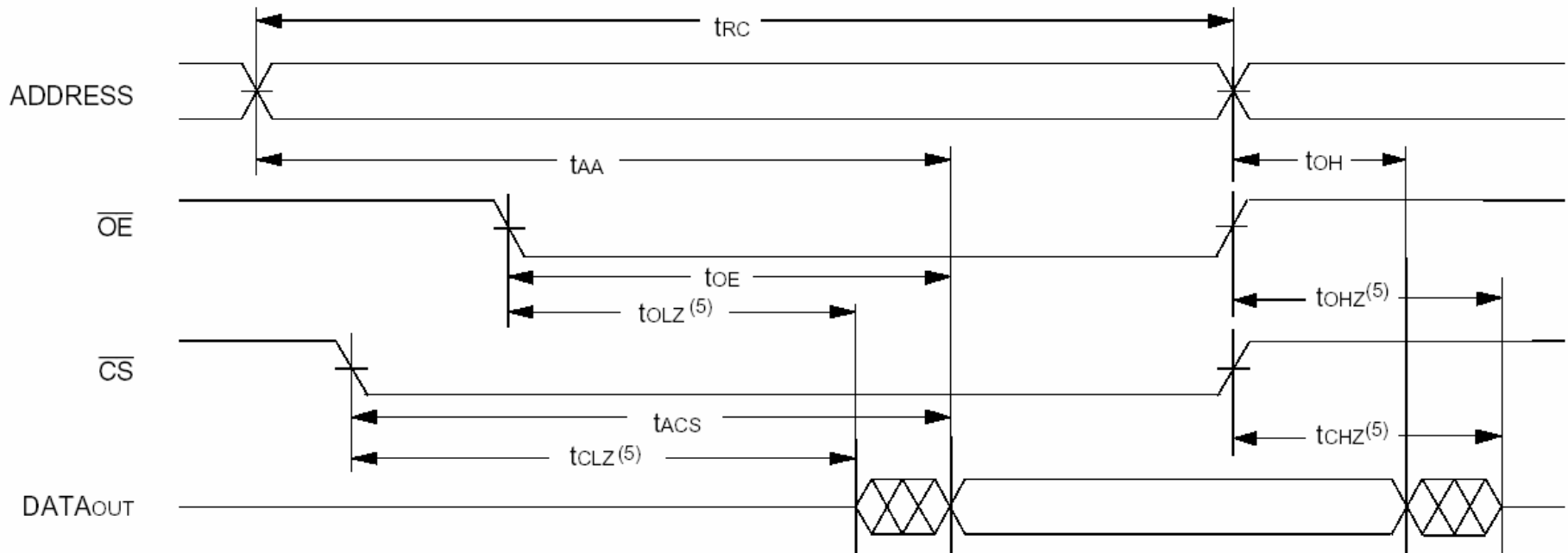
## Timing Waveform of Read Cycle No. 1<sup>(1)</sup>



Symbol	Parameter	Minimum (ns)	Maximum (ns)
$t_{RC}$	Read Cycle Time	20	-
$t_{AA}$	Address Access time	-	20
$t_{OLZ}$	Output Enable to Output in Low-Z	2	-
$t_{OE}$	Output Enable to Output Valid	-	10
$t_{OHZ}$	Output Disable to Output in Hi-Z	2	8

# IDT71256L Write Timing

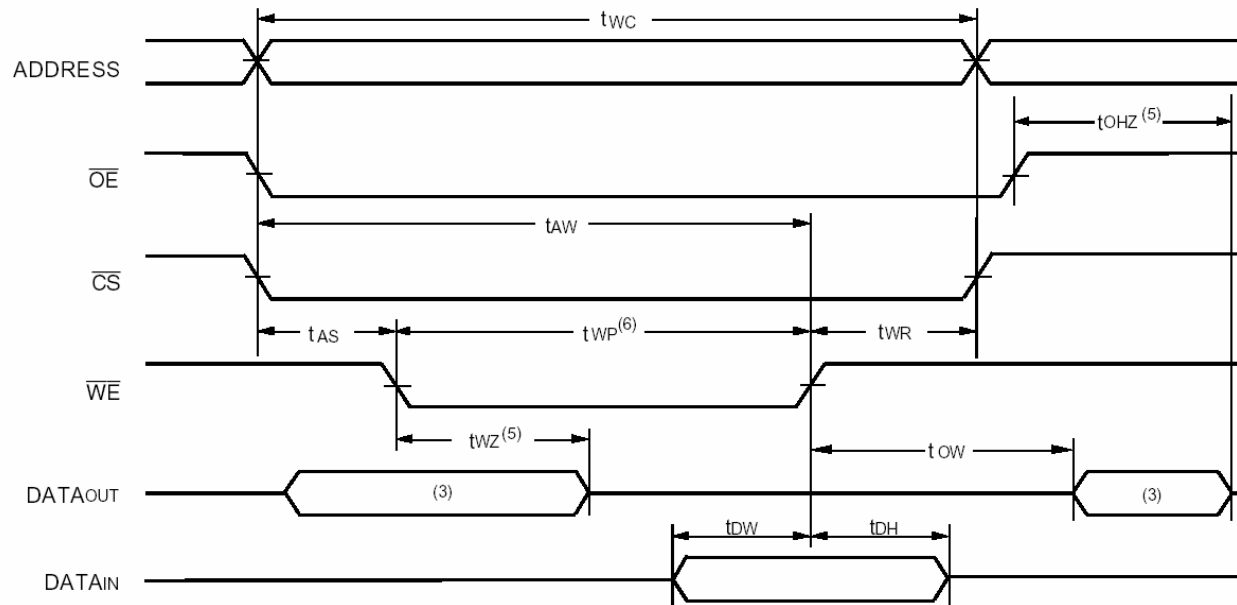**Timing Waveform of Write Cycle No. 1 ( $\overline{WE}$  Controlled Timing)<sup>(1,2,4,6)</sup>**



Symbol	Parameter	Minimum (ns)	Maximum (ns)
$t_{WC}$	Write Cycle Time	20	-
$t_{AW}$	Address Valid to End-of-Write	15	-
$t_{WP}$	Write Pulse Width	15	-
$t_{AS}$	Address Set-Up Time	0	-
$t_{DW}$	Data to Write Time Overlap	11	-
$t_{DH}$	Data Hold from Write Time	0	-


# Driving Force: The Clock

The clock is a signal that keeps the control unit moving.

- At each clock “tick,” control unit moves to the next machine cycle -- may be next instruction or next phase of current instruction.


Clock generator circuit:

 - Based on crystal oscillator
- Generates regular sequence of “0” and “1” logic levels
- Clock cycle (or machine cycle) -- rising edge to rising edge





# Read-Only Memories

 

# Why “ROM”?


---

## Program storage


- Boot ROM for personal computers
- Complete application storage for embedded systems.

Actually, a ROM is a combinational circuit, basically a truth-table lookup.

 - Can perform any combinational logic function
- Address inputs = function inputs
- Data outputs = function outputs




## Logic-in-ROM example

 


<i>Inputs</i>			<i>Outputs</i>			
<i>A2</i>	<i>A1</i>	<i>A0</i>	<i>D3</i>	<i>D2</i>	<i>D1</i>	<i>D0</i>
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

# 4x4 multiplier example

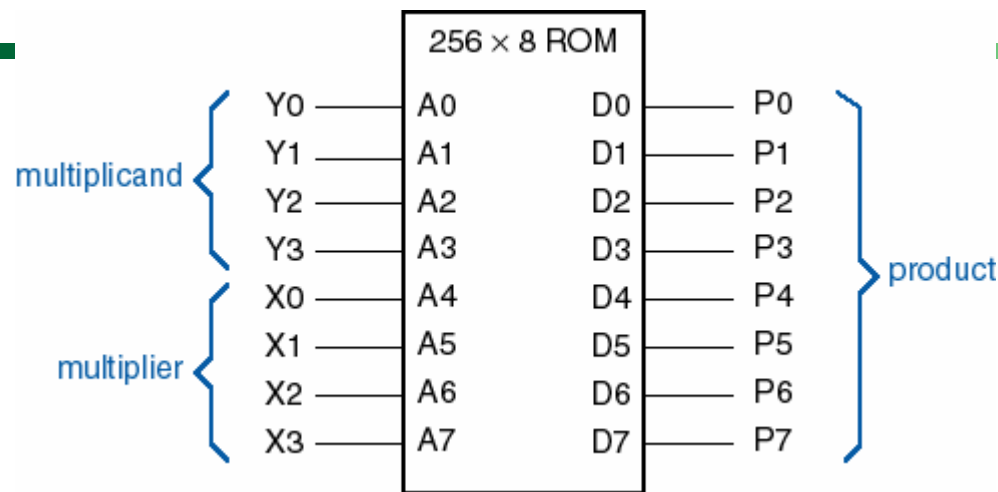


00:	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00	00
10:	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
20:	00	02	04	06	08	0A	0C	0E	10	12	14	16	18	1A	1C	1E
30:	00	03	06	09	0C	0F	12	15	18	1B	1E	21	24	27	2A	2D
40:	00	04	08	0C	10	14	18	1C	20	24	28	2C	30	34	38	3C
50:	00	05	0A	0F	14	19	1E	23	28	2D	32	37	3C	41	46	4B
60:	00	06	0C	12	18	1E	24	2A	30	36	3C	42	48	4E	54	5A
70:	00	07	0E	15	1C	23	2A	31	38	3F	46	4D	54	5B	62	69
80:	00	08	10	18	20	28	30	38	40	48	50	58	60	68	70	78
90:	00	09	12	1B	24	2D	36	3F	48	51	5A	63	6C	75	7E	87
A0:	00	0A	14	1E	28	32	3C	46	50	5A	64	6E	78	82	8C	96
B0:	00	0B	16	21	2C	37	42	4D	58	63	6E	79	84	8F	9A	A5
C0:	00	0C	18	24	30	3C	48	54	60	6C	78	84	90	9C	A8	B4
D0:	00	0D	1A	27	34	41	4E	5B	68	75	82	8F	9C	A9	B6	C3
E0:	00	0E	1C	2A	38	46	54	62	70	7E	8C	9A	A8	B6	C4	D2
F0:	00	0F	1E	2D	3C	4B	5A	69	78	87	96	A5	B4	C3	D2	E1

 


PDP-11 boot ROM  
(64 words, 1024 diodes)

Internal  
ROM  
structure

# Two-dimensional decoding

 


# Larger example, 32Kx8 ROM

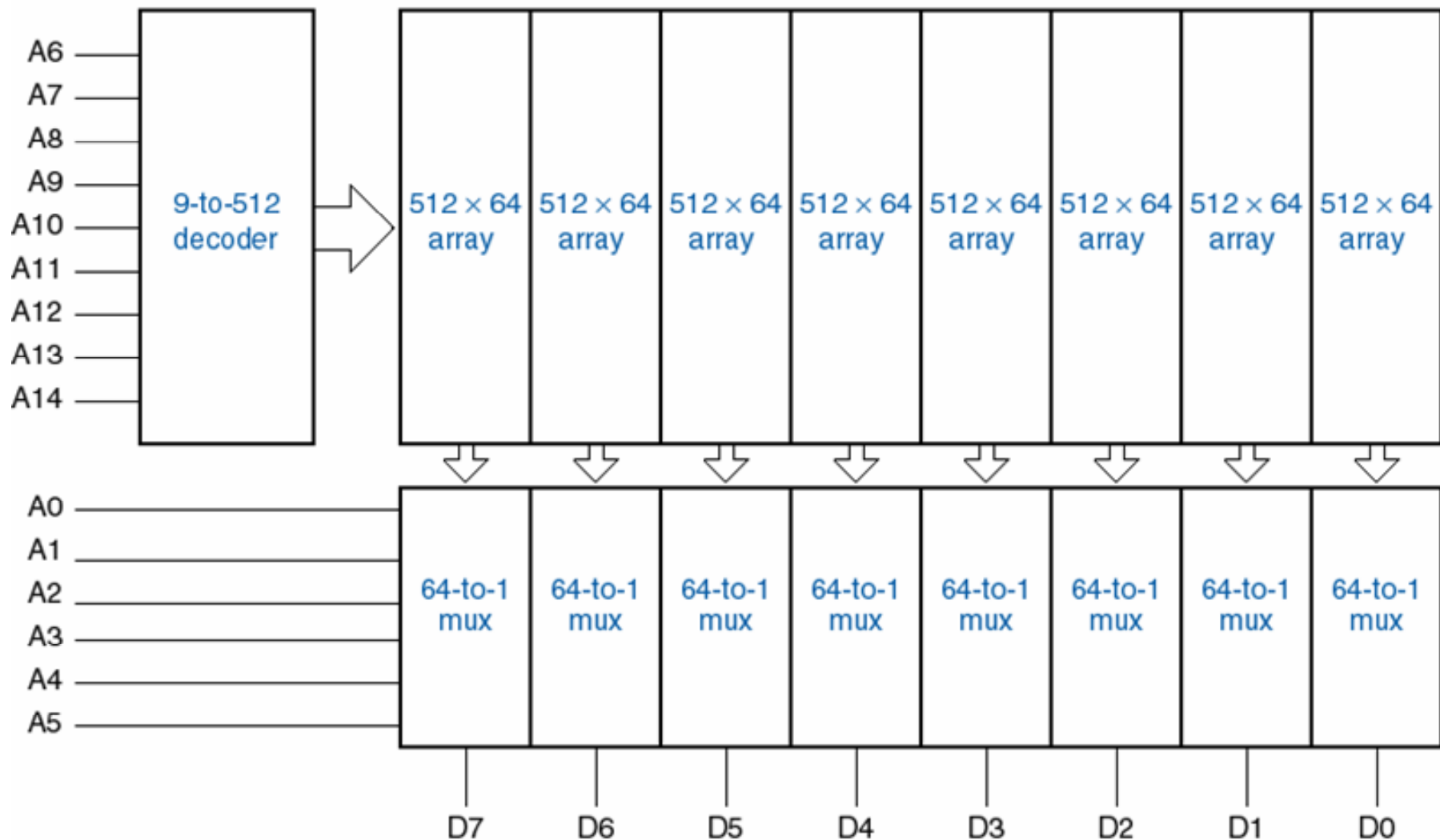

# Today's ROMs


256K bytes, 1M byte, or larger

Use MOS transistors

 




# EEPROMs, Flash PROMs

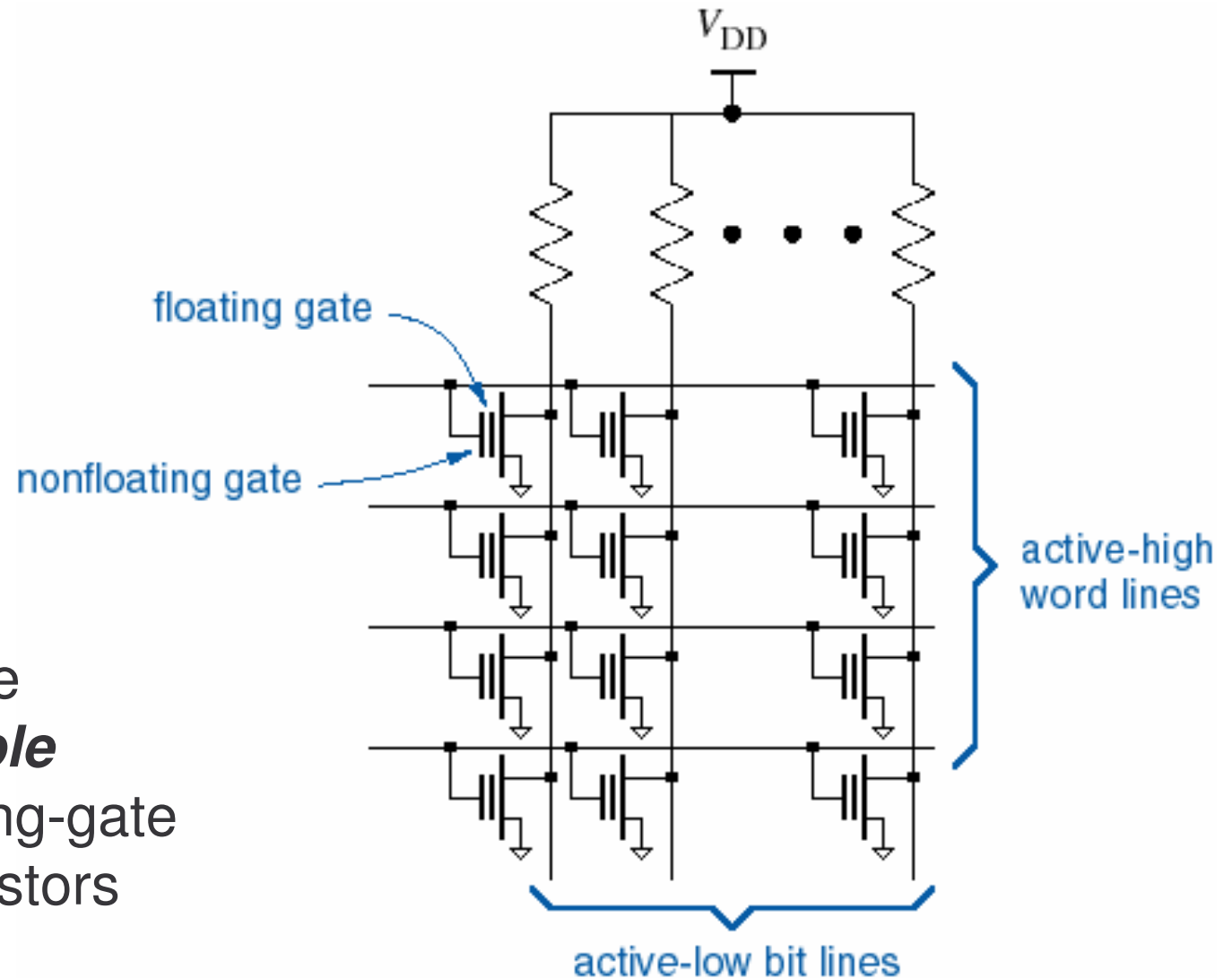

Programmable  
and ***erasable***  
using floating-gate  
MOS transistors

# Typical commercial EEPROMs

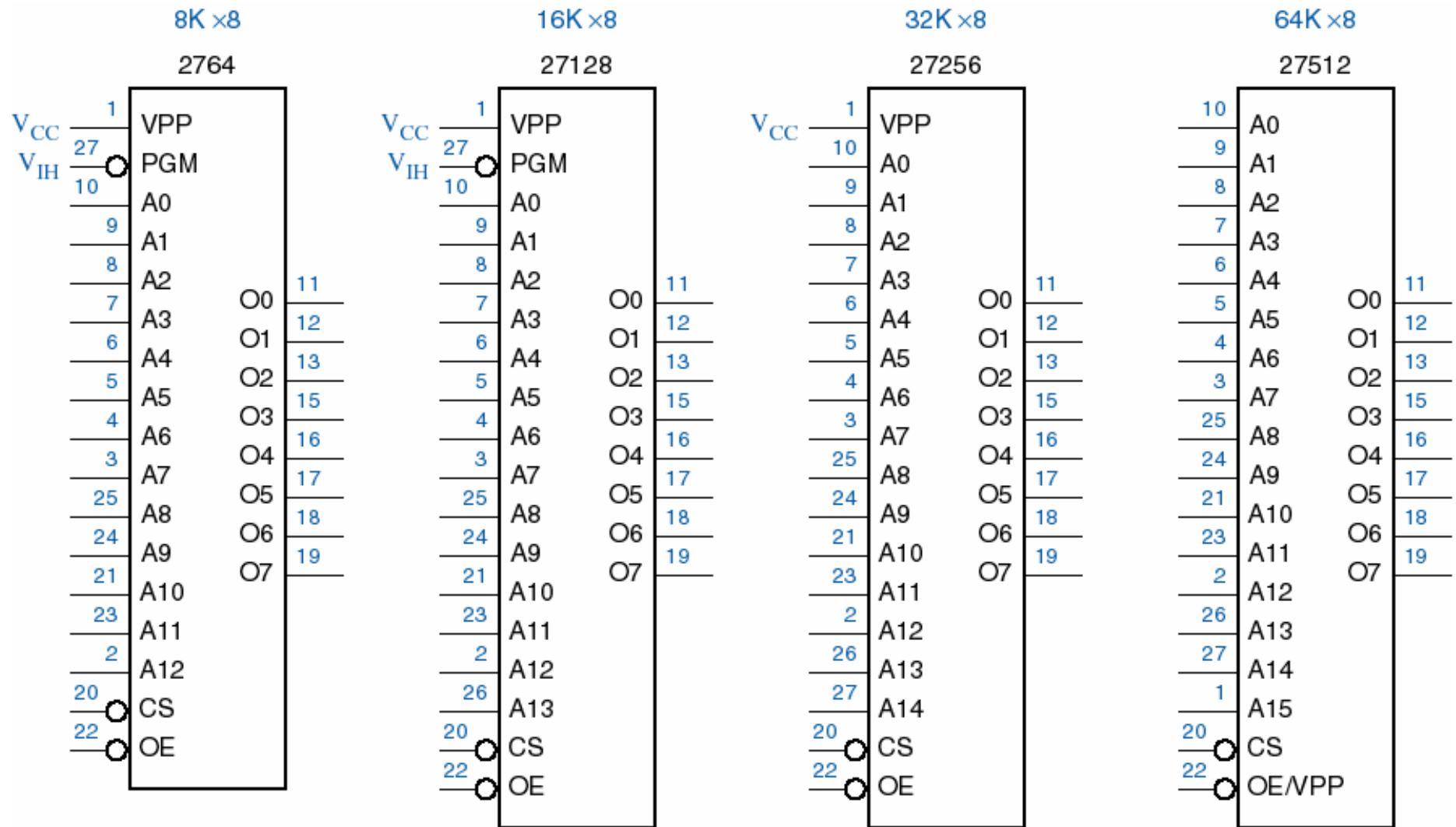

# EEPROM programming

---

Apply a higher voltage to force bit change


- E.g.,  $V_{PP} = 12\text{ V}$
- On-chip high-voltage “charge pump” in newer chips

Erase bits


- Byte-byte
- Entire chip (“flash”)
- One block (typically 32K - 66K bytes) at a time

Programming and erasing are a lot slower than reading  
(milliseconds vs. 10's of nanoseconds)

# Microprocessor EPROM application

 

# ROM control and I/O signals

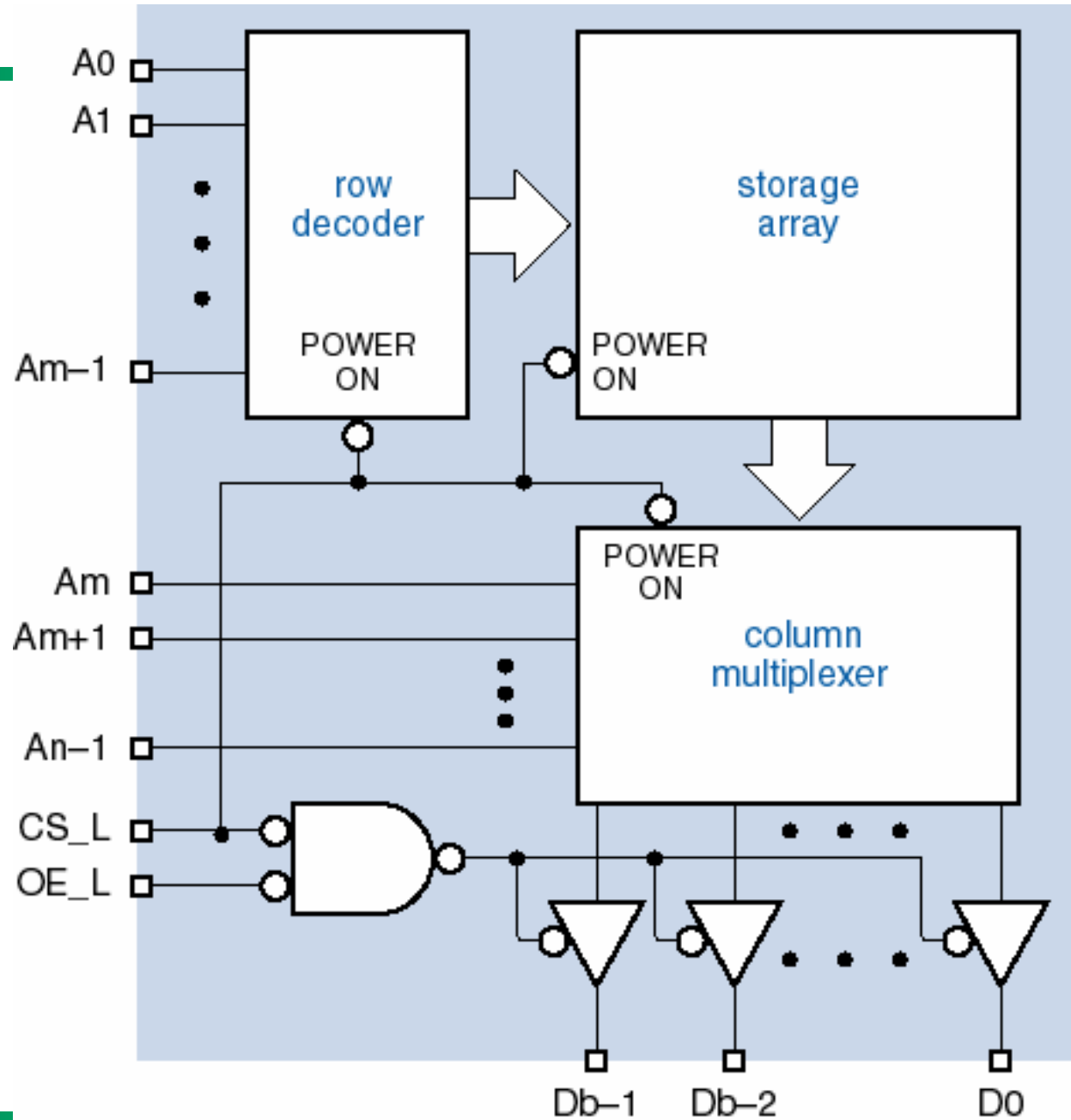

# ROM timing

