


Quiz 8 – ECGR2181 – Fall 2008 – 10/21/08

Your Name: _____

1. Attendance on 10/20/08 (10 points.) Yes No

2. What is the name of the combinational item at the right? (10 points).

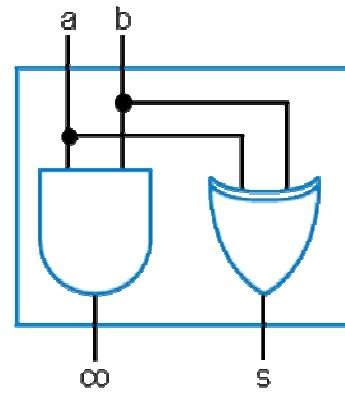- a. Full Adder
- b. Half adder
- c. Carry ripple adder
- d. Cascading adder
- e. Comparator



3. Design a circuit that will compare two 4-bit numbers and give you a “1” if they are identical or a “0” if they are not identical. For example, if a=“0010” and b=“0010”, the result of the circuit would be “1”. (80 points)