

Quiz – ECGR2181 – Fall 2008

Your Name: \_\_\_\_\_

1. Design a full-adder using half-adders and additional logic using the following half-adder.

