

**UNC Charlotte, Department of Electrical and Computer Engineering**  
**ECGR 2181, Fall 2009, Homework #5**  
**Due: 9/30/09 or 10/01/09, at the beginning of class (100 points)**

**Show all of your work!!!!**

1. How long did this assignment take you? (Answer truthfully!) (5 points)
2. Express each as a truth table then minimize: (Show Work! List Properties. **No KMAPS!**):
  - a)  $F(a,b,c) = \sum m(1,2,5,6,7)$  (15 points)
  - b)  $F(a,b,c) = \sum m(0,4,7)$  (15 points)
3. Minimize using KMAPS:
  - a)  $F(a,b,c) = \sum m(1,2,5,6,7)$  (10 points)
  - b)  $F(a,b,c) = \sum m(0,4,7)$  (10 points)
  - c)  $F(a,b,c,d) = \sum m(0,3,6,7,12,13,15)$  (10 points)
  - d)  $F(a,b,c,d) = \sum m(0,1,2,3,4,5,6,7,8,9,10,11,12,14)$  (10 points)
4. Draw the following circuit using **only NAND** Gates:  $f(a,b,c,d) = (ab)' + (b+c'd)' + bc$  (25 points)

**(NOTE: Problem 4 corrected - now is a function of (a, b, c, d) )**