



Digital Design


Chapter 2: Combinational Logic Design

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>

Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may not be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.


Introduction

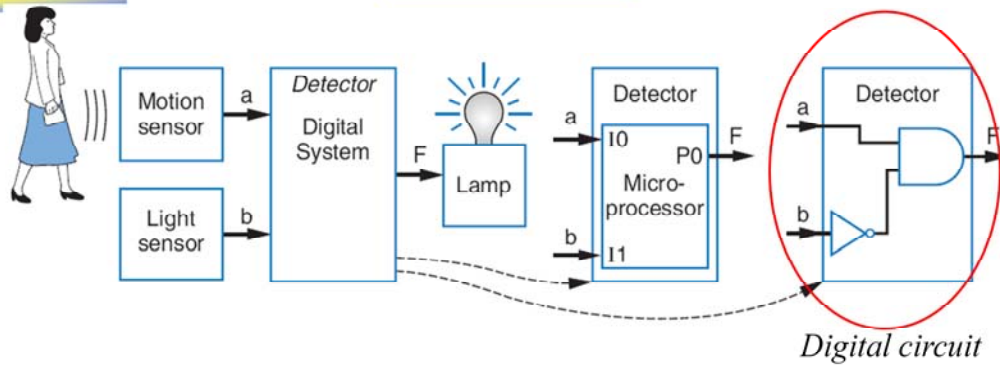

- Let's learn to design digital circuits
- We'll start with a simple form of circuit:

- **Combinational circuit**

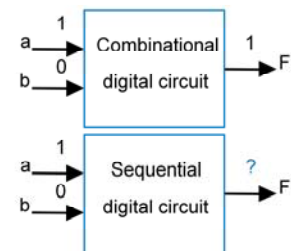- A digital circuit whose outputs depend solely on the present combination of the circuit inputs' values




Digital Design
Copyright © 2006
Frank Vahid

Note: Slides with animation are denoted with a small red "a" near the animated items



Switches

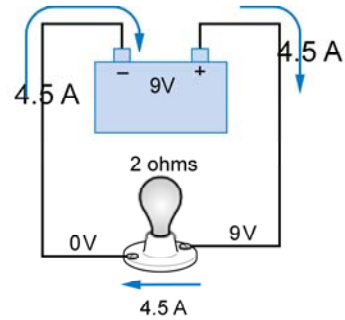- Electronic switches are the basis of binary digital circuits
 - Electrical terminology
 - **Voltage:** Difference in electric potential between two points
 - Analogous to water pressure
 - **Current:** Flow of charged particles
 - Analogous to water flow
 - **Resistance:** Tendency of wire to resist current flow
 - Analogous to water pipe diameter
 - $V = I * R$ (Ohm's Law)



Switches

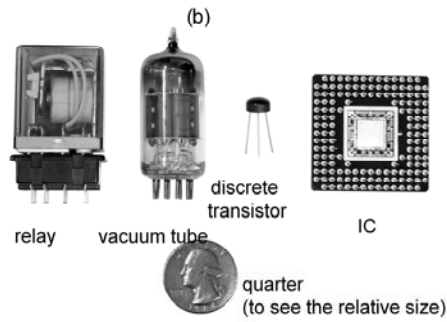
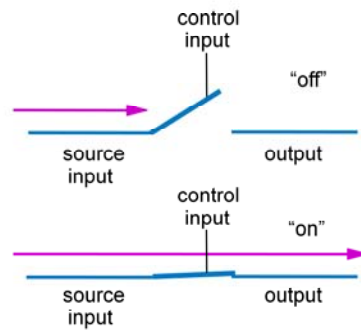
- A switch has three parts
 - Source input, and output
 - Current wants to flow from source input to output
 - Control input
 - Voltage that controls whether that current can flow
- The amazing shrinking switch
 - 1930s: Relays
 - 1940s: Vacuum tubes
 - 1950s: Discrete transistor
 - 1960s: Integrated circuits (ICs)
 - Initially just a few transistors on IC
 - Then tens, hundreds, thousands...



Digital Design
Copyright © 2006
Frank Vahid

Moore's Law

- IC capacity doubling about every 18 months for several decades
 - Known as “Moore’s Law” after Gordon Moore, co-founder of Intel
 - In 1965 predicted that components per IC would double roughly every year or so
 - Book cover depicts related phenomena
 - For a particular number of transistors, the IC shrinks by half every 18 months
 - Notice how much shrinking occurs in just about 10 years
 - Enables incredibly powerful computation in incredibly tiny devices
 - Today’s ICs hold *billions* of transistors
 - The first Pentium processor (early 1990s) needed only 3 million

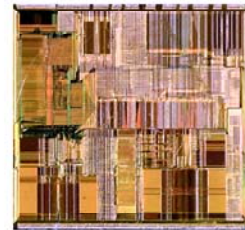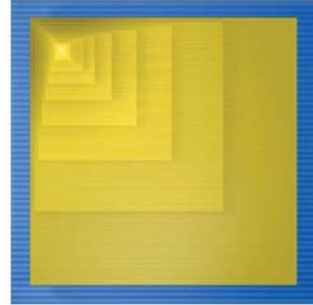


An Intel Pentium processor IC having millions of transistors



Digital Design
Copyright © 2006
Frank Vahid

The CMOS Transistor

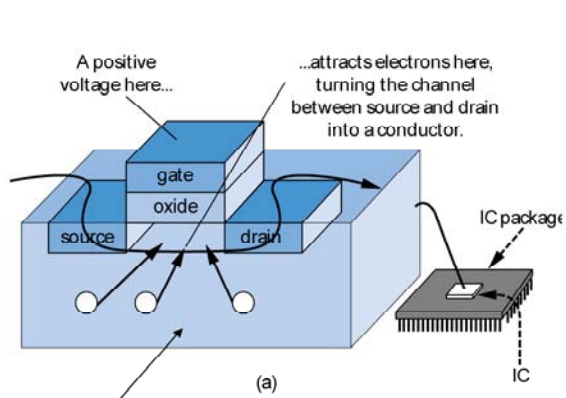- CMOS transistor
 - Basic switch in modern ICs



Silicon -- not quite a conductor or insulator:

Semiconductor



Digital Design
Copyright © 2006
Frank Vahid

nMOS



conducts




does not
conduct

pMOS



does not
conduct

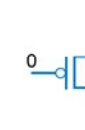

conducts

Boolean Logic Gates

Building Blocks for Digital Circuits

(Because Switches are Hard to Work With)

2.4

These blocks...

...are hard to work with.

Transistors are hard to work with

The right building blocks...

...enable greater designs.

The logic gates that we'll soon introduce enable greater designs

- "Logic gates" are better digital circuit building blocks than switches (transistors)
 - Why?...



Digital Design
Copyright © 2006
Frank Vahid

Boolean Algebra and its Relation to Digital Circuits

- To understand the benefits of “logic gates” vs. switches, we should first understand Boolean algebra
- “Traditional” algebra
 - Variable represent real numbers
 - Operators operate on variables, return real numbers
- **Boolean Algebra**
 - Variables represent 0 or 1 only
 - Operators return 0 or 1 only
 - Basic operators
 - AND: a AND b returns 1 only when both $a=1$ and $b=1$
 - OR: a OR b returns 1 if either (or both) $a=1$ or $b=1$
 - NOT: NOT a returns the opposite of a (1 if $a=0$, 0 if $a=1$)

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Digital Design
Copyright © 2006
Frank Vahid

Boolean Algebra and its Relation to Digital Circuits

- Developed mid-1800's by George Boole to formalize human thought

– Ex: "I'll go to lunch if Mary goes OR John goes, AND Sally does not go."

- Let F represent my going to lunch (1 means I go, 0 I don't go)
- Likewise, m for Mary going, j for John, and s for Sally
- Then **F = (m OR j) AND NOT(s)**

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

– Nice features

- Formally evaluate

– $m=1, j=0, s=1 \rightarrow F = (1 \text{ OR } 0) \text{ AND NOT}(1) = 1 \text{ AND } 0 = \underline{0}$

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

- Formally transform

– $F = (m \text{ and NOT}(s)) \text{ OR } (j \text{ and NOT}(s))$

» Looks different, but same function

» We'll show transformation techniques soon

a	NOT
0	1
1	0



Evaluating Boolean Equations

- Evaluate the Boolean equation

$$F = (a \text{ AND } b) \text{ OR } (c \text{ AND } d)$$

for the given values of variables a, b, c, and d:

– Q1: a=1, b=1, c=1, d=0.

- Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 0) = 1 \text{ OR } 0 = 1$.

– Q2: a=0, b=1, c=0, d=1.

- Answer: $F = (0 \text{ AND } 1) \text{ OR } (0 \text{ AND } 1) = 0 \text{ OR } 0 = 0$.

– Q3: a=1, b=1, c=1, d=1.

- Answer: $F = (1 \text{ AND } 1) \text{ OR } (1 \text{ AND } 1) = 1 \text{ OR } 1 = 1$.

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



Converting to Boolean Equations

- Convert the following English statements to a Boolean equation
 - Q1. a is 1 and b is 1.
 - Answer: $F = a \text{ AND } b$
 - Q2. either of a or b is 1.
 - Answer: $F = a \text{ OR } b$
 - Q3. both a and b are not 0.
 - Answer:
 - (a) Option 1: $F = \text{NOT}(\text{NOT}(a) \text{ AND } \text{NOT}(b))$
 - (b) Option 2: $F = a \text{ OR } b$
 - Q4. a is 1 and b is 0.
 - Answer: $F = a \text{ AND } \text{NOT}(b)$





Converting to Boolean Equations

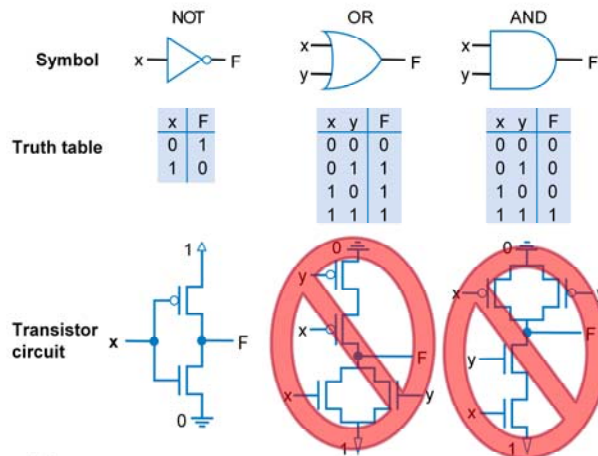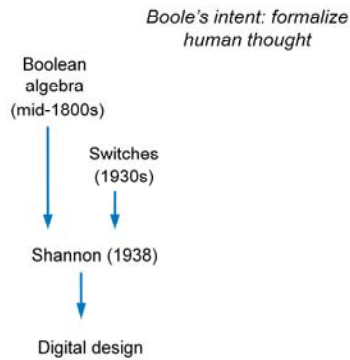- **Q1. A fire sprinkler system should spray water if high heat is sensed and the system is set to enabled.**
 - Answer: Let Boolean variable h represent “high heat is sensed,” e represent “enabled,” and F represent “spraying water.” Then an equation is: $F = h \text{ AND } e$.
- **Q2. A car alarm should sound if the alarm is enabled, and either the car is shaken or the door is opened.**
 - Answer: Let a represent “alarm is enabled,” s represent “car is shaken,” d represent “door is opened,” and F represent “alarm sounds.” Then an equation is: $F = a \text{ AND } (s \text{ OR } d)$.
 - (a) Alternatively, assuming that our door sensor d represents “door is closed” instead of open (meaning $d=1$ when the door is closed, 0 when open), we obtain the following equation: $F = a \text{ AND } (s \text{ OR } \text{NOT}(d))$.



Relating Boolean Algebra to Digital Design






- Implement Boolean operators using transistors
 - Call those implementations **logic gates**.
 - **Let's us build circuits by doing math** -- powerful concept

Note: These OR/AND implementations are inefficient; -per Vahid


not just inefficient ... these circuits do not work. We'll examine how to produce AND and OR gates with CMOS transistors later

NOT/OR/AND Logic Gate Timing Diagrams

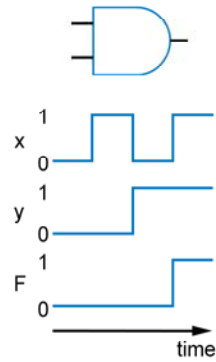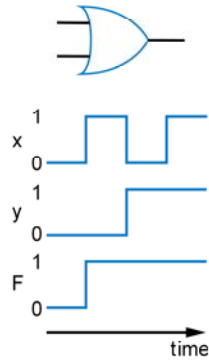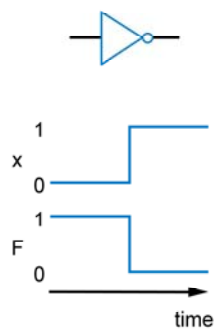

Digital Design
Copyright © 2006
Frank Vahid

Building Circuits Using Gates


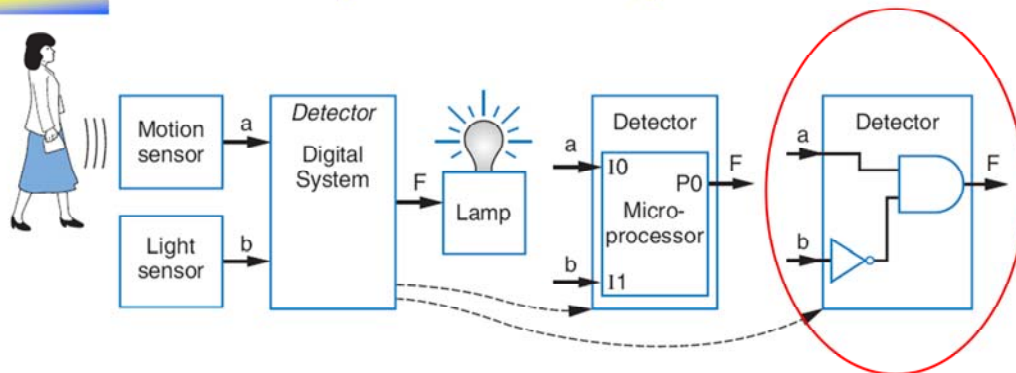


- Recall Chapter 1 motion-in-dark example
 - Turn on lamp ($F=1$) when motion sensed ($a=1$) and no light ($b=0$)
 - $F = a \text{ AND NOT}(b)$
 - Build using logic gates, AND and NOT, as shown
 - We just built our first digital circuit!



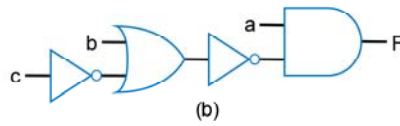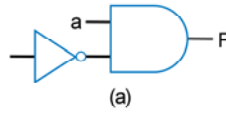Example: Converting a Boolean Equation to a Circuit of Logic Gates

- Q: Convert the following equation to logic gates:
 $F = a \text{ AND NOT}(b \text{ OR NOT}(c))$




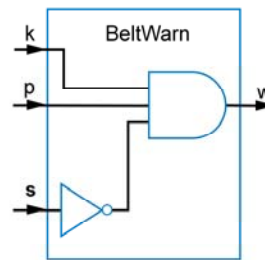Example: Seat Belt Warning Light System

- Design circuit for warning light
- Sensors
 - s=1: seat belt fastened
 - k=1: key inserted
 - p=1: person in seat
- Capture Boolean equation
 - person in seat, and seat belt not fastened, and key inserted
- Convert equation to circuit
- Notice
 - Boolean algebra enables easy capture as equation and conversion to circuit
 - How design with switches?
 - Of course, logic gates are built from switches, but we think at level of logic gates, not switches




$$w = p \text{ AND NOT}(s) \text{ AND } k$$



Digital Design
Copyright © 2006
Frank Vahid

Some Circuit Drawing Conventions

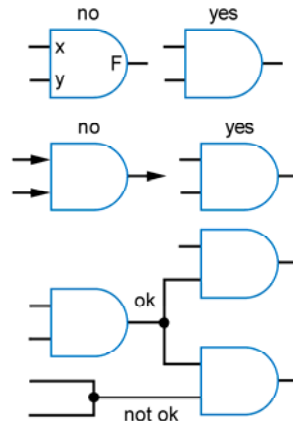

Boolean Algebra

- By defining logic gates based on Boolean algebra, we can use algebraic methods to manipulate circuits
 - So let's learn some Boolean algebraic methods
- Start with notation: Writing a AND b, a OR b, and NOT(a) is cumbersome
 - Use symbols: $a * b$, $a + b$, and a' (in fact, $a * b$ can be just ab).
 - Original: $w = (p \text{ AND NOT}(s) \text{ AND } k) \text{ OR } t$
 - New: $w = ps'k + t$
 - Spoken as "w equals p and s prime and k, or t"
 - Or even just "w equals p s prime k, or t"
 - s' known as "complement of s"
 - While symbols come from regular algebra, *don't* say "times" or "plus"

Boolean algebra precedence, highest precedence first.

Symbol	Name	Description
()	Parentheses	Evaluate expressions nested in parentheses first
'	NOT	Evaluate from left to right
*	AND	Evaluate from left to right
+	OR	Evaluate from left to right



Boolean Algebra Operator Precedence

- Evaluate the following Boolean equations, assuming $a=1$, $b=1$, $c=0$, $d=1$.
 - Q1. $F = a * b + c$.
 - Answer: $*$ has precedence over $+$, so we evaluate the equation as $F = (1 * 1) + 0 = (1) + 0 = 1 + 0 = 1$.
 - Q2. $F = ab + c$.
 - Answer: the problem is identical to the previous problem, using the shorthand notation for $*$.
 - Q3. $F = ab'$.
 - Answer: we first evaluate b' because NOT has precedence over AND, resulting in $F = 1 * (1') = 1 * (0) = 1 * 0 = 0$.
 - Q4. $F = (ac)'$.
 - Answer: we first evaluate what is inside the parentheses, then we NOT the result, yielding $(1*0)' = (0)' = 0' = 1$.
 - Q5. $F = (a + b') * c + d'$.
 - Answer: Inside left parentheses: $(1 + (1')) = (1 + (0)) = (1 + 0) = 1$. Next, $*$ has precedence over $+$, yielding $(1 * 0) + 1' = (0) + 1'$. The NOT has precedence over the OR, giving $(0) + (1') = (0) + (0) = 0 + 0 = 0$.



Boolean Algebra Terminology

- Example equation: $F(a,b,c) = a'bc + abc' + ab + c$
- **Variable**
 - Represents a value (0 or 1)
 - Three variables: a, b, and c
- **Literal**
 - Appearance of a variable, in true or complemented form
 - Nine literals: a', b, c, a, b, c', a, b, and c
- **Product term**
 - Product of literals
 - Four product terms: a'bc, abc', ab, c
- **Sum-of-products**
 - Equation written as OR of product terms only
 - Above equation is in sum-of-products form. "F = (a+b)c + d" is not.



Boolean Algebra Properties

- Commutative
 - $a + b = b + a$
 - $a * b = b * a$
- Distributive
 - $a * (b + c) = a * b + a * c$
 - $a + (b * c) = (a + b) * (a + c)$
 - (this one is tricky!)
- Associative
 - $(a + b) + c = a + (b + c)$
 - $(a * b) * c = a * (b * c)$
- Identity
 - $0 + a = a + 0 = a$
 - $1 * a = a * 1 = a$
- Complement
 - $a + a' = 1$
 - $a * a' = 0$
- *To prove, just evaluate all possibilities*

Example uses of the properties

- Show abc' equivalent to $c'ba$.
 - Use commutative property:
 - $a*b*c' = a*c'*b = c'*a*b = c'*b*a = c'ba$.
- Show $abc + abc' = ab$.
 - Use first distributive property
 - $abc + abc' = ab(c+c')$.
 - Complement property
 - Replace $c+c'$ by 1: $ab(c+c') = ab(1)$.
 - Identity property
 - $ab(1) = ab*1 = ab$.
- Show $x + x'z$ equivalent to $x + z$.
 - Second distributive property
 - Replace $x+x'z$ by $(x+x')*(x+z)$.
 - Complement property
 - Replace $(x+x')$ by 1,
 - Identity property
 - replace $1*(x+z)$ by $x+z$.




Example that Applies Boolean Algebra Properties

- Want automatic door opener circuit (e.g., for grocery store)

- Output: $f=1$ opens door
- Inputs:
 - $p=1$: person detected
 - $h=1$: switch forcing hold open
 - $c=1$: key forcing closed
- Want open door when
 - $h=1$ and $c=0$, or
 - $h=0$ and $p=1$ and $c=0$

- Equation: $f = hc' + h'pc'$

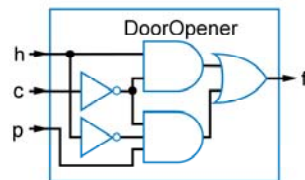

Digital Design
Copyright © 2006
Frank Vahid

- Found inexpensive chip that computes:

- $f = c'hp + c'hp' + c'h'p$

- Can we use it?

- Is it the same as $f = hc' + h'pc'$?

- Use Boolean algebra:

$$f = c'hp + c'hp' + c'h'p$$

$$f = c'h(p + p') + c'h'p \text{ (by the distributive property)}$$

$$f = c'h(1) + c'h'p \text{ (by the complement property)}$$

$$f = c'h + c'h'p \text{ (by the identity property)}$$

$$f = hc' + h'pc' \text{ (by the commutative property)}$$

Same!


Boolean Algebra: Additional Properties

Aircraft lavatory sign example


- Null elements
 - $a + 1 = 1$
 - $a * 0 = 0$
- Idempotent Law
 - $a + a = a$
 - $a * a = a$
- Involution Law
 - $(a')' = a$
- DeMorgan's Law
 - $(a + b)' = a'b'$
 - $(ab)' = a' + b'$
 - Very useful!
- To prove, just evaluate all possibilities

- Behavior
 - Three lavatories, each with sensor (a, b, c), equals 1 if door locked
 - Light "Available" sign (S) if any lavatory available
- Equation and circuit
 - $S = a' + b' + c'$
- Transform
 - $(abc)' = a' + b' + c'$ (by DeMorgan's Law)
 - $S = (abc)'$
- New equation and circuit

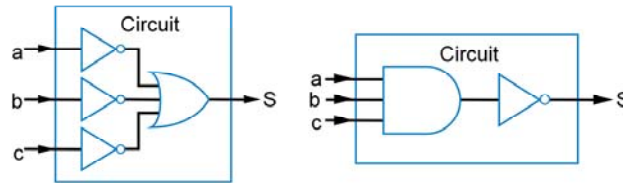- Alternative: Instead of lighting "Available," light "Occupied"
 - Opposite of "Available" function $S = a' + b' + c'$
 - So $S' = (a' + b' + c)'$
 - $S' = (a')' * (b')' * (c)'$ (by DeMorgan's Law)
 - $S' = a * b * c$ (by Involution Law)
 - Makes intuitive sense
 - Occupied if all doors are locked



Representations of Boolean Functions

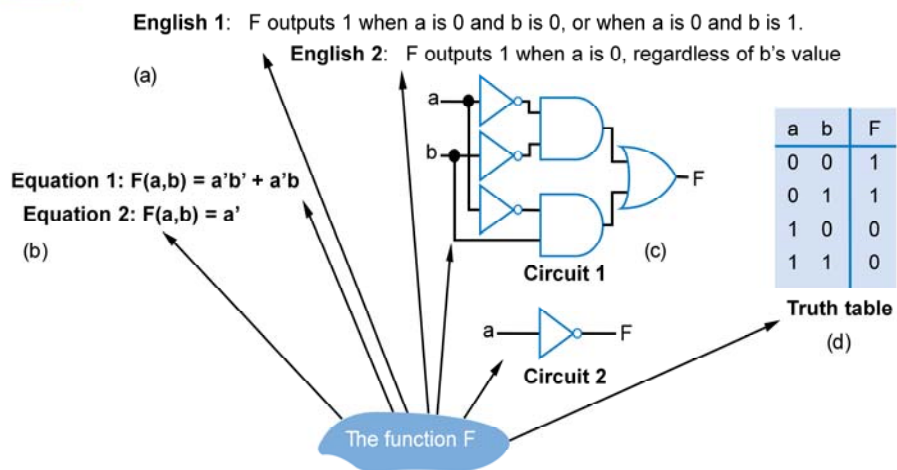

- A function can be represented in different ways
 - Above shows seven representations of the same functions $F(a,b)$, using four different methods: English, Equation, Circuit, and Truth Table



Truth Table Representation of Boolean Functions

- Define value of F for each possible combination of input values
 - 2-input function: 4 rows
 - 3-input function: 8 rows
 - 4-input function: 16 rows

a	b	F
0	0	
0	1	
1	0	
1	1	

(a)

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

(b)

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

(c)

- Q: Use truth table to define function $F(a,b,c)$ that is 1 when abc is 5 or greater in binary

a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



Digital Design
Copyright © 2006
Frank Vahid

Converting among Representations

- Can convert from any representation to any other
- Common conversions
 - Equation to circuit (we did this earlier)
 - Truth table to equation (which we can convert to circuit)
 - Easy -- just OR each input term that should output 1
 - Equation to truth table
 - Easy -- just evaluate equation for each input combination (row)
 - Creating intermediate columns helps

Inputs		Outputs	Term
a	b	F	F = sum of
0	0	1	a'b'
0	1	1	a'b
1	0	0	
1	1	0	

$$F = a'b' + a'b$$

Q: Convert to equation

a	b	c	F	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	ab'c
1	1	0	1	abc'
1	1	1	1	abc

$$F = ab'c + abc' + abc$$

Q: Convert to truth table: $F = a'b' + a'b$

Inputs				Output
a	b	a'b'	a'b	F
0	0	1	0	1
0	1	0	1	1
1	0	0	0	0
1	1	0	0	0



Digital Design
Copyright © 2006
Frank Vahid

Standard Representation: Truth Table

- How can we determine if two functions are the same?
 - Recall automatic door example
 - Same as $f = hc' + h'pc'$?
 - Used algebraic methods
 - But if we failed, does that prove *not* equal? No.
- Solution: Convert to truth tables
 - Only ONE truth table representation of a given function
 - **Standard** representation -- for given function, only one version in standard form exists

$$f = c'hp + c'hp' + c'h'$$

$$f = c'h(p + p') + c'h'p$$

$$f = c'h(1) + c'h'p$$

$$f = c'h + c'h'p$$

(what if we stopped here?)

$$f = hc' + h'pc'$$

Q: Determine if $F=ab+a'$ is same function as $F=a'b'+a'b+ab$, by converting each to truth table first

F = ab + a'			F = a'b' + a'b + ab		
a	b	F	a	b	F
0	0	1	0	0	1
0	1	1	0	1	1
1	0	0	1	0	0
1	1	1	1	1	1

Same



Digital Design
Copyright © 2006
Frank Vahid

Canonical Form -- Sum of Minterms

- Truth tables too big for numerous inputs
- Use standard form of equation instead
 - Known as **canonical form**
 - Regular algebra: group terms of polynomial by power
 - $ax^2 + bx + c$ ($3x^2 + 4x + 2x^2 + 3 + 1 \rightarrow 5x^2 + 4x + 4$)
 - Boolean algebra: create sum of minterms
 - **Minterm**: product term with every literal appearing exactly once, in true or complemented form
 - Just multiply-out equation until sum of product terms
 - Then expand each term until all terms are minterms

Q: Determine if $F(a,b)=ab+a'$ is same function as $F(a,b)=a'b'+a'b+ab$, by converting first equation to canonical form (second already in canonical form)

$F = ab+a'$ (already sum of products)

$F = ab + a'(b+b')$ (expanding term)


$F = ab + a'b + a'b'$ (SAME -- same three terms as other equation)



Digital Design
Copyright © 2006
Frank Vahid

Multiple-Output Circuits

- Many circuits have more than one output
- Can give each a separate circuit, or can share gates
- Ex: $F = ab + c'$, $G = ab + bc$

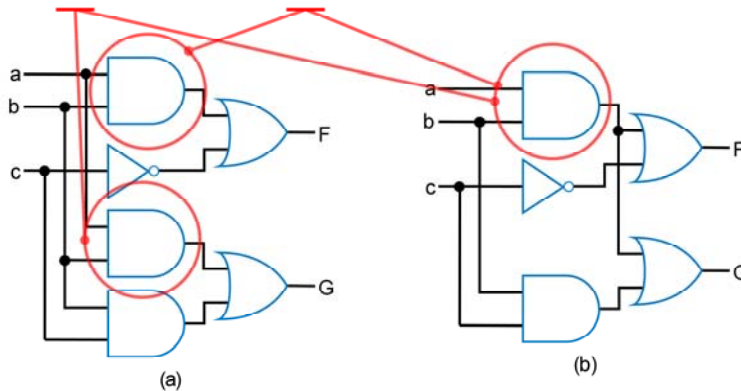

Option 1: Separate circuits

Option 2: Shared gates




Multiple-Output Example: BCD to 7-Segment Converter



TABLE 2-4 4-bit binary number to seven-segment display truth table

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

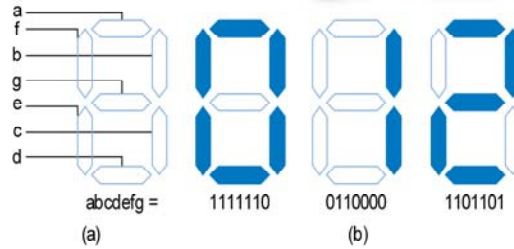

$$a = w'x'y'z' + w'x'yz' + w'x'yz + w'xy'z + w'xyz' + w'xyz + wx'y'z' + wx'y'z$$

$$b = w'x'y'z' + w'x'y'z + w'x'yz' + w'x'yz + w'xy'z' + w'xyz' + wx'y'z' + wx'y'z$$



Practice Problem

TABLE 2-4 4-bit binary number to seven-segment display truth table

w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	1	1	1	0	1	1	1
1	0	1	1	0	0	1	1	1	1	1
1	1	0	0	1	0	0	1	1	1	0
1	1	0	1	0	1	1	1	1	0	1
1	1	1	0	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	1	1	1

- Find the Canonical Sums expression for output f

Practice Problem

Use Boolean Algebra to reduce this equation to smallest S.O.P. expression:

$$\begin{aligned} H(a,b,c,d) &= \Sigma m(0, 1, 5, 10, 11, 14, 15) \\ &= m_0 + m_1 + m_5 + m_{10} + m_{11} + m_{14} + m_{15} \end{aligned}$$

Solution(highlight to see):

Combinational Logic Design Process

	Step	Description
Step 1	Capture the function	Create a truth table or equations, <i>whichever is most natural for the given problem</i> , to describe the desired behavior of the combinational logic.
Step 2	Convert to equations	This step is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.
Step 3	Implement as a gate-based circuit	For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)



Example: Three 1s Detector

- Problem: Detect three consecutive 1s in 8-bit input: abcdefgh


- 00011101 → 1 10101011 → 0
- 11110000 → 1

- **Step 1: Capture** the function

- Truth table or equation?
 - Truth table too big: $2^8=256$ rows
 - Equation: create terms for each possible case of three consecutive 1s
- $y = abc + bcd + cde + def + efg + fgh$

- **Step 2: Convert** to equation -- already done

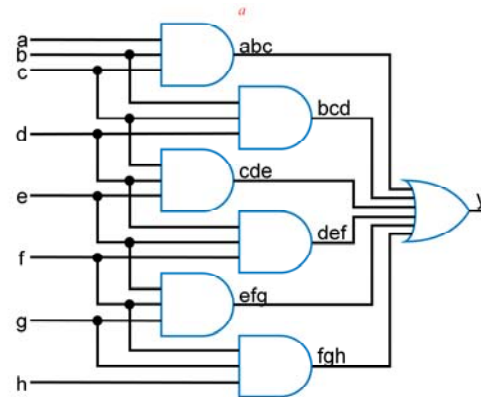- **Step 3: Implement** as a gate-based circuit



Digital Design
Copyright © 2006
Frank Vahid

Example: Number of 1s Count

- Problem: Output in binary on two outputs yz the number of 1s on three inputs


- 010 → 01 101 → 10 000 → 00

- **Step 1: Capture** the function
 - Truth table or equation?
 - Truth table is straightforward

- **Step 2: Convert** to equation
 - $y = a'bc + ab'c + abc' + abc$
 - $z = a'b'c + a'bc' + ab'c' + abc$



- **Step 3: Implement** as a gate-based circuit

Inputs			# of 1s	Outputs	
a	b	c		y	z
0	0	0	(0)	0	0
0	0	1	(1)	0	1
0	1	0	(1)	0	1
0	1	1	(2)	1	0
1	0	0	(1)	0	1
1	0	1	(2)	1	0
1	1	0	(2)	1	0
1	1	1	(3)	1	1

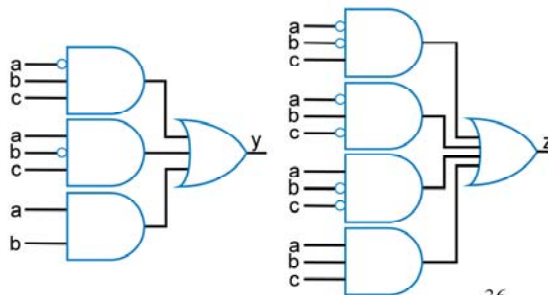

Digital Design
Copyright © 2006
Frank Vahid

More Gates

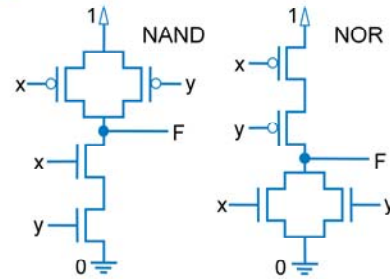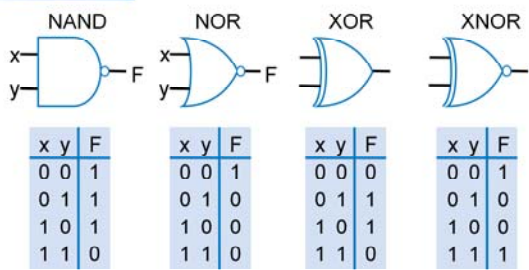


- NAND: Opposite of AND (“NOT AND”)
- NOR: Opposite of OR (“NOT OR”)
- XOR: Exactly 1 input is 1, for 2-input XOR. (For more inputs -- odd number of 1s)
- XNOR: Opposite of XOR (“NOT XOR”)
- NAND and NOR gates are most basic for transistor point-of-view
 - Use controlled-switch model discussed earlier to understand
- AND in CMOS: NAND with NOT
- OR in CMOS: NOR with NOT
- So, NAND/NOR more common



More Gates: Example Uses


- Aircraft lavatory sign example

- $S = (abc)'$

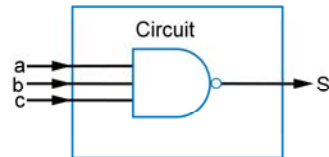


- Detecting all 0s

- Use NOR

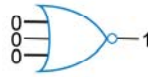

- Detecting equality

- Use XNOR

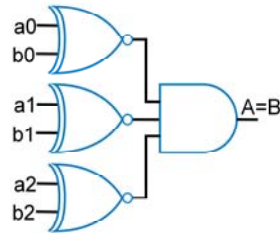




- Detecting odd # of 1s

- Use XOR

- Useful for generating “parity” bit
common for detecting errors



Completeness of NAND

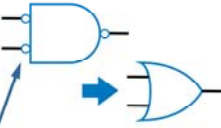- Any Boolean function can be implemented *using just NAND gates*. Why?
 - Need AND, OR, and NOT
 - NOT: 2-input NAND with inputs tied together 
 - AND: NAND followed by NOT 
 - OR: NAND preceded by NOTs on all inputs 
- Likewise for NOR

Bubbles same as inverters.



Number of Possible Boolean Functions

- How many possible functions of 2 variables?
 - 2^2 rows in truth table, 2 choices for each
 - $2^{(2^2)} = 2^4 = 16$ possible functions
- N variables
 - 2^N rows
 - $2^{(2^N)}$ possible functions

a	b	F
0	0	0 or 1 2 choices
0	1	0 or 1 2 choices
1	0	0 or 1 2 choices
1	1	0 or 1 2 choices




$2^4 = 16$
possible functions

a	b	f0	f1	f2	f3	f4	f5	f6	f7	f8	f9	f10	f11	f12	f13	f14	f15
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1
		0	a AND b		a	b	a XOR b		a OR b	a NOR b	a XNOR b		b'	a'	a NAND b		1



Decoders and Muxes


- **Decoder:** Popular combinational logic building block, in addition to logic gates
 - Converts input binary number to one high output
- 2-input decoder: four possible input binary numbers
 - So has four outputs, one for each possible input binary number
- Internal design
 - AND gate for each output to detect input combination
- Decoder with enable e
 - Outputs all 0 if $e=0$
 - Regular behavior if $e=1$
- n -input decoder: 2^n outputs

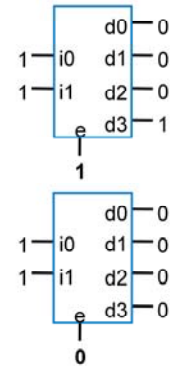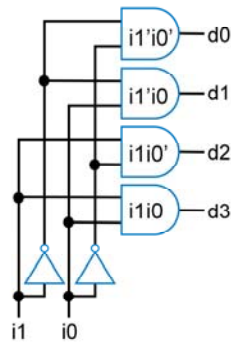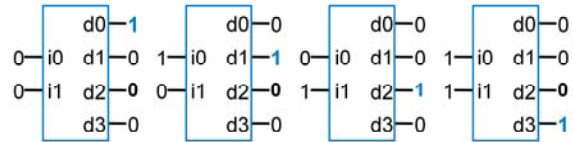

Digital Design
Copyright © 2006
Frank Vahid

Decoder Example

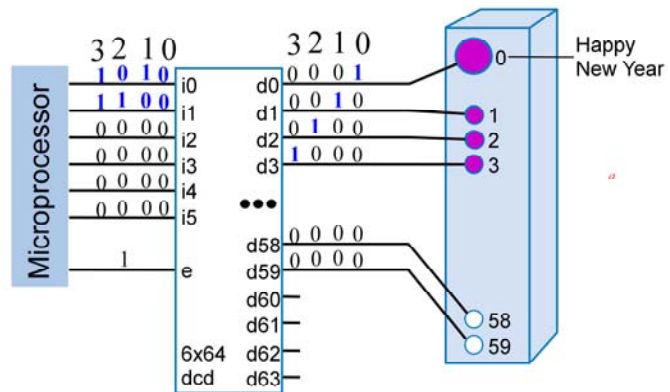
- New Year's Eve Countdown Display
 - Microprocessor counts from 59 down to 0 in binary on 6-bit output
 - Want illuminate one of 60 lights for each binary number
 - Use 6x64 decoder
 - 4 outputs unused



Digital Design
Copyright © 2006
Frank Vahid


Multiplexor (Mux)

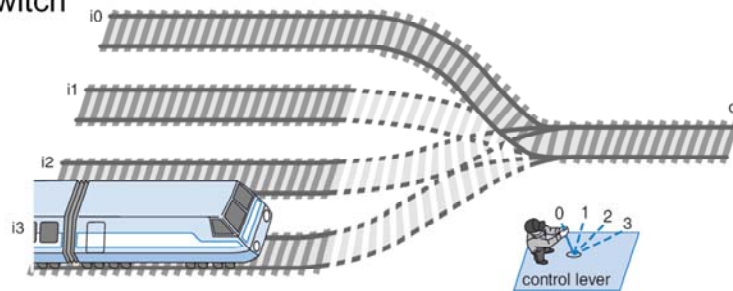- Mux: Another popular combinational building block
 - Routes one of its N data inputs to its one output, based on binary value of select inputs
 - 4 input mux \rightarrow needs 2 select inputs to indicate which input to route through
 - 8 input mux \rightarrow 3 select inputs
 - N inputs $\rightarrow \log_2(N)$ selects
 - Like a railyard switch




Digital Design
Copyright © 2006
Frank Vahid


Mux Internal Design

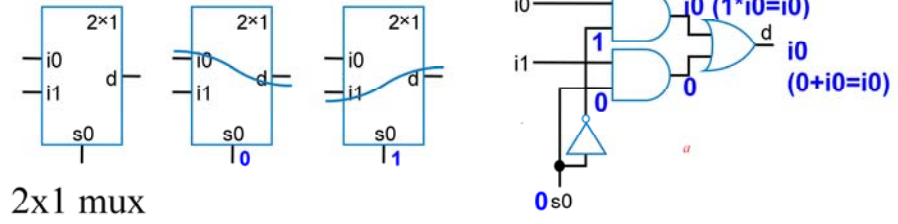

2x1 mux

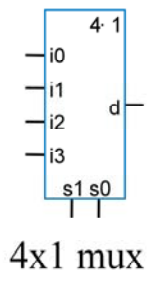


4x1 mux

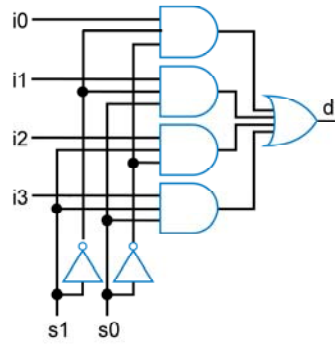


Mux Example

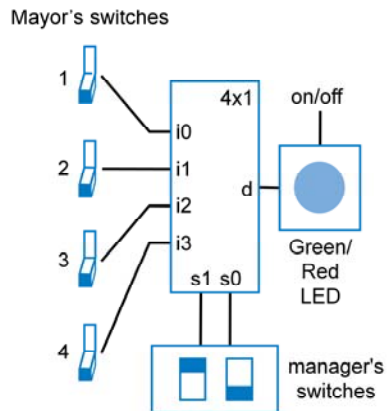- City mayor can set four switches up or down, representing his/her vote on each of four proposals, numbered 0, 1, 2, 3
- City manager can display any such vote on large green/red LED (light) by setting two switches to represent binary 0, 1, 2, or 3
- Use 4x1 mux




Muxes Commonly Together -- N-bit Mux

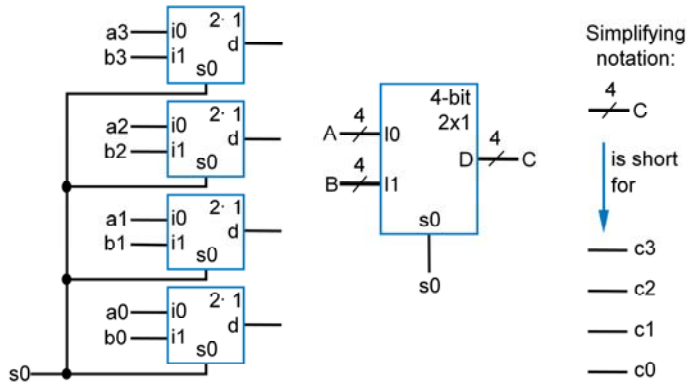

- Ex: Two 4-bit inputs, A (a3 a2 a1 a0), and B (b3 b2 b1 b0)
 - 4-bit 2x1 mux (just four 2x1 muxes sharing a select line) can select between A or B



N-bit Mux Example

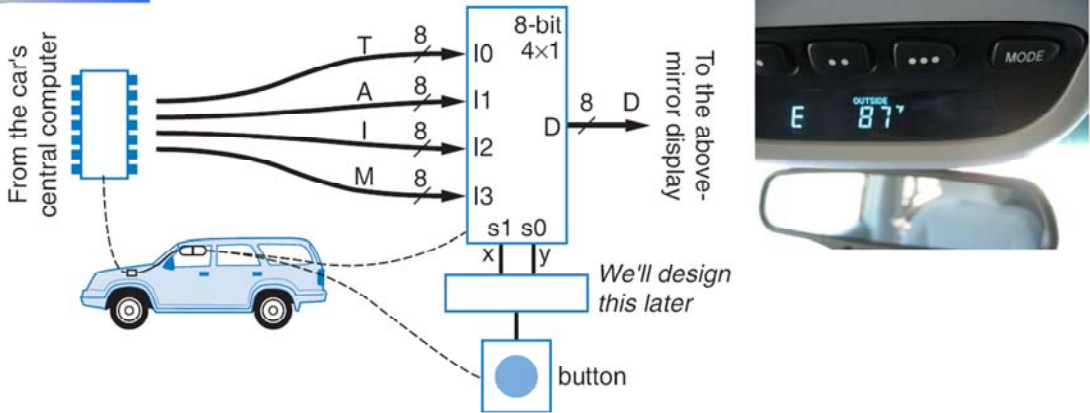


- Four possible display items
 - Temperature (T), Average miles-per-gallon (A), Instantaneous mpg (I), and Miles remaining (M) -- each is 8-bits wide
 - Choose which to display using two inputs x and y
 - Use 8-bit 4x1 mux



Digital Design
 Copyright © 2006
 Frank Vahid

Additional Considerations

Schematic Capture and Simulation

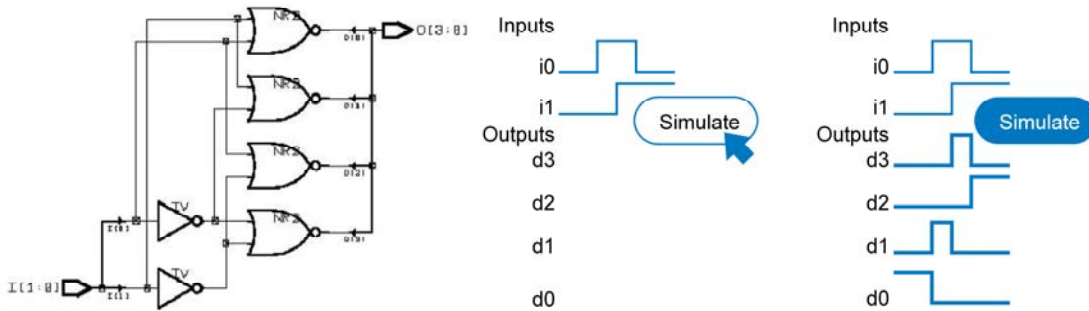


- **Schematic capture**
 - Computer tool for user to capture logic circuit graphically
- **Simulator**
 - Computer tool to show what circuit outputs would be for given inputs
 - Outputs commonly displayed as **waveforms**



Additional Considerations

Non-Ideal Gate Behavior -- Delay

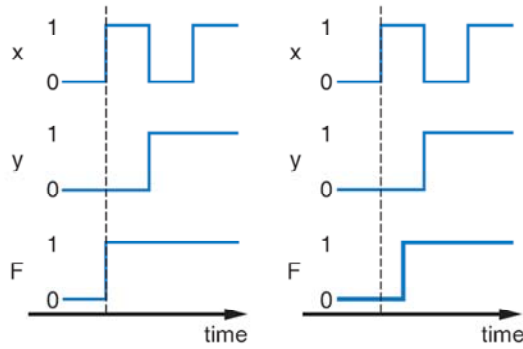

- Real gates have some delay (called *Propagation Delay*)
 - Outputs don't change immediately after inputs change



Digital Design
Copyright © 2006
Frank Vahid

Chapter Summary

- Combinational circuits
 - Circuit whose outputs are function of present inputs
 - No “state”
- Switches: Basic component in digital circuits
- Boolean logic gates: AND, OR, NOT -- Better building block than switches
 - Enables use of Boolean algebra to design circuits
- Boolean algebra: uses true/false variables/operators
- Representations of Boolean functions: Can translate among
- Combinational design process: Translate from equation (or table) to circuit through well-defined steps
- More gates: NAND, NOR, XOR, XNOR also useful
- Muxes and decoders: Additional useful combinational building blocks

