



Digital Design

Chapter 4b: Datapath Components - Sequential

Slides to accompany the textbook *Digital Design*, First Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2007.
<http://www.ddvahid.com>

Copyright © 2007 Frank Vahid

Instructors of courses requiring Vahid's *Digital Design* textbook (published by John Wiley and Sons) have permission to modify and use these slides for auxiliary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites. PowerPoint source (or pdf with animations) may not be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley - see <http://www.ddvahid.com> for information.




Introduction

- Chapters 3: Introduced increasingly complex digital building blocks
 - Basic registers, and controllers
- Controllers good for systems with control inputs/outputs
 - **Control** input: Single bit (or just a few), representing environment event or state
 - e.g., 1 bit representing button pressed
 - **Data** input: Multiple bits collectively representing single entity
 - e.g., 7 bits representing temperature in binary
- Need building blocks for data
 - **Datapath components**, aka register-transfer-level (RTL) components. store/transform data
 - Put datapath components together to form a **datapath**
- This chapter introduces numerous datapath components, and simple datapaths
 - Next chapter will combine controllers and datapaths into “processors”



Registers

   - Can store data, very common in datapaths
- Basic register of Ch 3: Loaded every cycle
 - Useful for implementing FSM – stores encoded state
 - For other uses, may want to load only on certain cycles





Basic register loads on every clock cycle

How extend to only load on certain cycles?



Register with Parallel Load

  
- Add 2x1 mux to front of each flip-flop
- Register's load input selects mux input to pass
 - Either existing flip-flop value, or new value to load




Digital Design
Copyright © 2006
Frank Vahid

Basic Example using Registers

 - This example will show how registers load simultaneously on clock cycles
 - Notice that all load inputs set to 1 in this example -- just for demonstration purposes




Basic Example Using Registers (cont.)

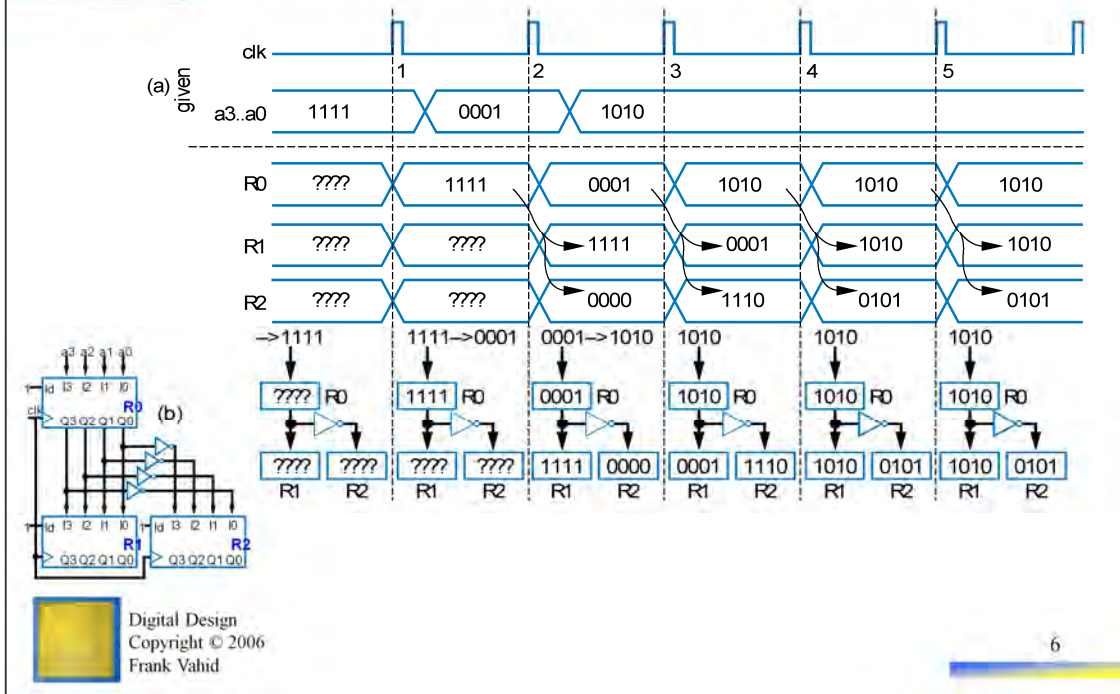


Register Example using the Load Input: Weight Sampler

 - Scale has two displays
 - Present weight
 - Saved weight
 - Useful to compare present item with previous item
- Use register to store weight
 - Pressing button causes present weight to be stored in register
 - Register contents always displayed as "Saved weight," even when new present weight appears




Register Example: Temperature History Display

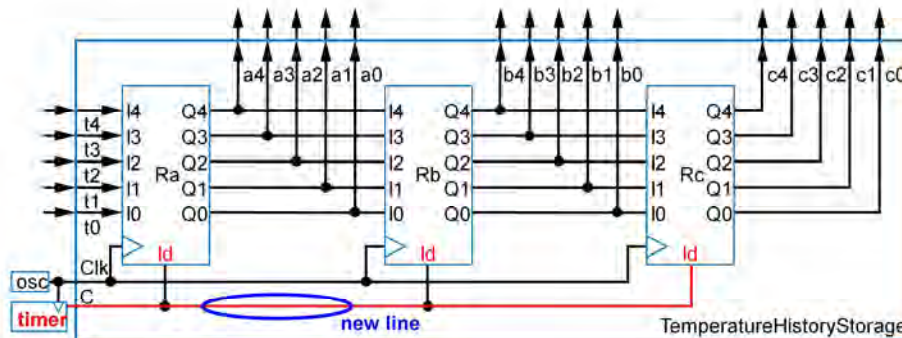
- Recall Chpt 3 example
 - Timer pulse every hour
 - Previously used as clock. Better design only connects oscillator to clock inputs - - use registers with load input, connect to timer pulse.



Register Example: Above-Mirror Display

 


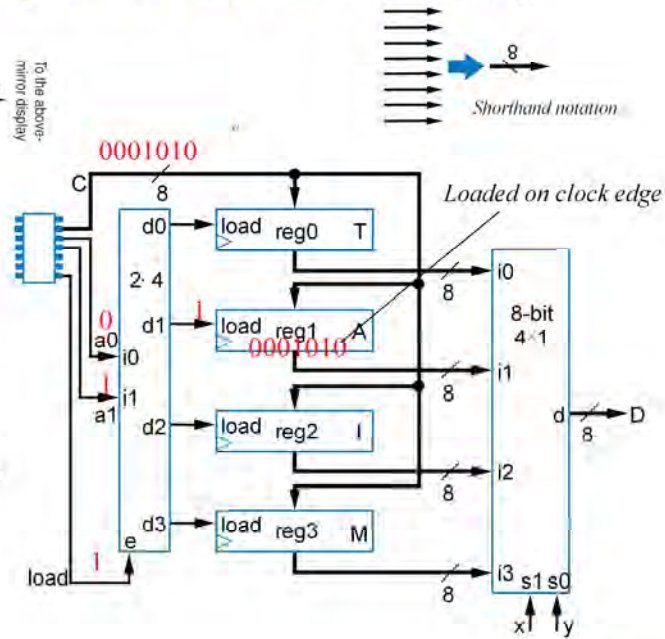- Ch2 example: Four simultaneous values from car's computer
- To reduce wires: Computer writes only 1 value at a time, loads into one of four registers
 - Was: $8+8+8+8 = 32$ wires
 - Now: $8 + 2 + 1 = 11$ wires




Register Example: Computerized Checkerboard

 - Each register holds values for one column of lights
 - 1 lights light
- Microprocessor loads one register at a time
 - Occurs fast enough that user sees entire board change at once




Digital Design
Copyright © 2006
Frank Vahid

 Register Example: Computerized Checkerboard



Shift Register

 - Shift right
 - Move each bit one position right
 - Shift in 0 to leftmost bit



Q: Do four right shifts on 1001, showing value after each shift


A: 1001 (original)
0100
0010
0001
0000

- Implementation: Connect flip-flop output to next flip-flop's input



Shift Register

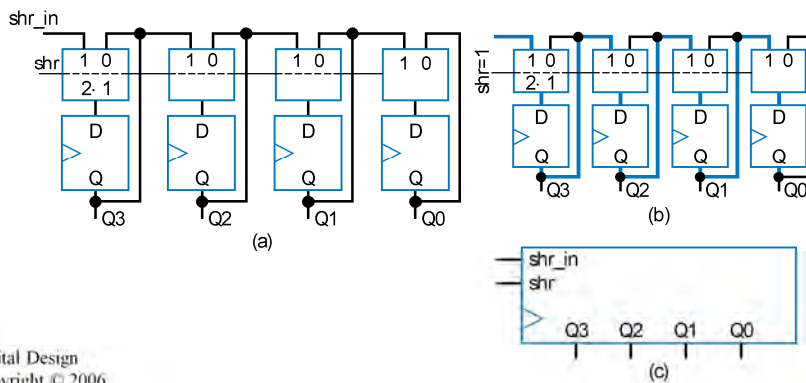
- To allow register to either shift or retain, use 2x1 muxes
 - shr: 0 means retain, 1 shift
 - shr_in: value to shift in
 - May be 0, or 1
- Note: Can easily design shift register that shifts left instead



Digital Design
Copyright © 2006
Frank Vahid

Rotate Register

 - Rotate right: Like shift right, but leftmost bit comes from rightmost bit
- a.k.a. Barrel Shifter



- Shift registers can be made to shift left as well ...




Shift Register Example: Above-Mirror Display

- Earlier example: 8 + 2 + 1 = 11 wires from car's computer to above-mirror display's four registers


- Better than 32 wires, but 11 still a lot -- want fewer for smaller wire bundles



 - Use shift registers
 - Wires: 1 + 2 + 1 = 4
 - Computer sends one value at a time, one bit per clock cycle



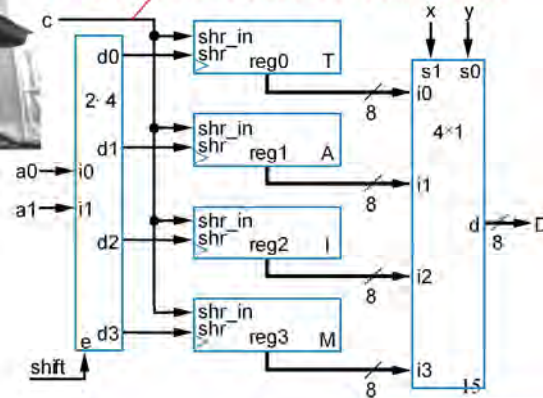Note: this line is 1 bit, rather than 8 bits like before





Digital Design
Copyright © 2006
Frank Vahid

Multifunction Registers

- Many registers have multiple functions
 - Load, shift, clear (load all 0s)
 - And retain present value, of course
- Easily designed using muxes
 - Just connect each mux input to achieve desired function

Functions:


s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	(unused - let's load 0s)

  

Digital Design
Copyright © 2006
Frank Vahid

Multifunction Registers

s1	s0	Operation
0	0	Maintain present value
0	1	Parallel load
1	0	Shift right
1	1	Shift left

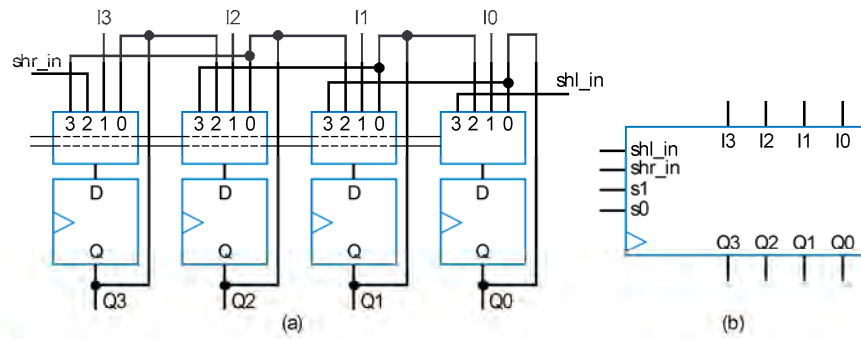


Digital Design
Copyright © 2006
Frank Vahid

Multifunction Registers with Separate Control Inputs

ld	shr	shl	Operation
0	0	0	Maintain present value
0	0	1	Shift left
0	1	0	Shift right
0	1	1	Shift right – shr has priority over shl
1	0	0	Parallel load
1	0	1	Parallel load – ld has priority
1	1	0	Parallel load – ld has priority
1	1	1	Parallel load – ld has priority

Truth table for combinational circuit

Inputs			Outputs		Note Operation
ld	shr	shl	s1	s0	
0	0	0	0	0	Maintain value
0	0	1	1	1	Shift left
0	1	0	1	0	Shift right
0	1	1	1	0	Shift right
1	0	0	0	1	Parallel load
1	0	1	0	1	Parallel load
1	1	0	0	1	Parallel load
1	1	1	0	1	Parallel load

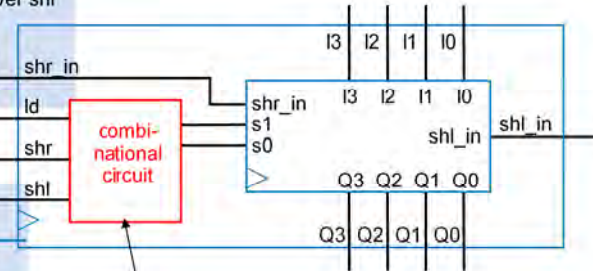

$$s1 = ld' * shr' * shl + ld' * shr * shl' + ld' * shr * shl$$

$$s0 = ld' * shr' * shl + ld$$

Register Operation Table

- Register operations typically shown using compact version of table
 - X means same operation whether value is 0 or 1
 - One X expands to two rows
 - Two Xs expand to four rows
 - Put highest priority control input on left to make reduced table simple

Inputs			Outputs		Note Operation
ld	shr	shl	s1	s0	
0	0	0	0	0	Maintain value
0	0	1	1	1	Shift left
0	1	0	1	0	Shift right
0	1	1	1	0	Shift right
1	0	0	0	1	Parallel load
1	0	1	0	1	Parallel load
1	1	0	0	1	Parallel load
1	1	1	0	1	Parallel load

ld	shr	shl	Operation
0	0	0	Maintain value
0	0	1	Shift left
0	1	X	Shift right
1	X	X	Parallel load



Register Design Process

- Can design register with desired operations using simple four-step process

TABLE 4.1 Four-step process for designing a multifunction register.

	Step	Description
1.	<i>Determine mux size</i>	Count the number of operations (don't forget the maintain present value operation!) and add in front of each flip-flop a mux with at least that number of inputs.
2.	<i>Create mux operation table</i>	Create an operation table defining the desired operation for each possible value of the mux select lines.
3.	<i>Connect mux inputs</i>	For each operation, connect the corresponding mux data input to the appropriate external input or flip-flop output (possibly passing through some logic) to achieve the desired operation.
4.	<i>Map control lines</i>	Create a truth table that maps external control lines to the internal mux select lines, with appropriate priorities, and then design the logic to achieve that mapping.



Register Design Example

- Desired register operations
 - Load, shift left, synchronous clear, synchronous set

s2	s1	s0	Operation
0	0	0	Maintain present value
0	0	1	Parallel load
0	1	0	Shift left
0	1	1	Synchronous clear
1	0	0	Synchronous set
1	0	1	Maintain present value
1	1	0	Maintain present value
1	1	1	Maintain present value

Step 1: Determine mux size

5 operations: above, plus maintain present value (don't forget this one!)
 --> Use 8x1 mux

Step 2: Create mux operation table

Step 3: Connect mux inputs


Step 4: Map control lines

$$s2 = \text{clr} * \text{set}$$


$$s1 = \text{clr} * \text{set} * \text{ld} * \text{shl} + \text{clr}$$

$$s0 = \text{clr} * \text{set} * \text{ld} + \text{clr}$$

Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s

 

Register Design Example

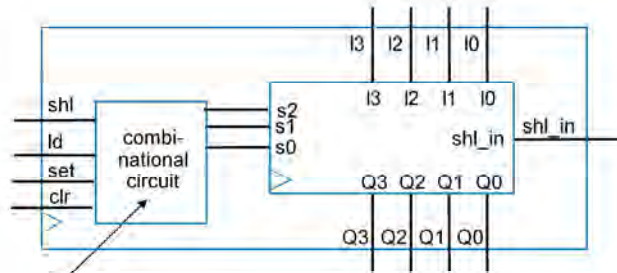

Step 4: Map control lines

$$s2 = \text{clr} * \text{set}$$

$$s1 = \text{clr} * \text{set} * \text{ld} * \text{shl} + \text{clr}$$

$$s0 = \text{clr} * \text{set} * \text{ld} + \text{clr}$$


Inputs				Outputs			Operation
clr	set	ld	shl	s2	s1	s0	
0	0	0	0	0	0	0	Maintain present value
0	0	0	1	0	1	0	Shift left
0	0	1	X	0	0	1	Parallel load
0	1	X	X	1	0	0	Set to all 1s
1	X	X	X	0	1	1	Clear to all 0s



Digital Design
Copyright © 2006
Frank Vahid


Shifters

- Shifting (e.g., left shifting 0011 yields 0110) useful for:
 - Manipulating bits
 - Converting serial data to parallel (remember earlier above-mirror display example with shift registers)
 - Shift left once is same as multiplying by 2 (0011 (3) becomes 0110 (6))
 - Why? Essentially appending a 0 – Note that multiplying decimal number by 10 accomplished just by appending 0, i.e., by shifting left (55 becomes 550)
 - Shift right once same as dividing by 2

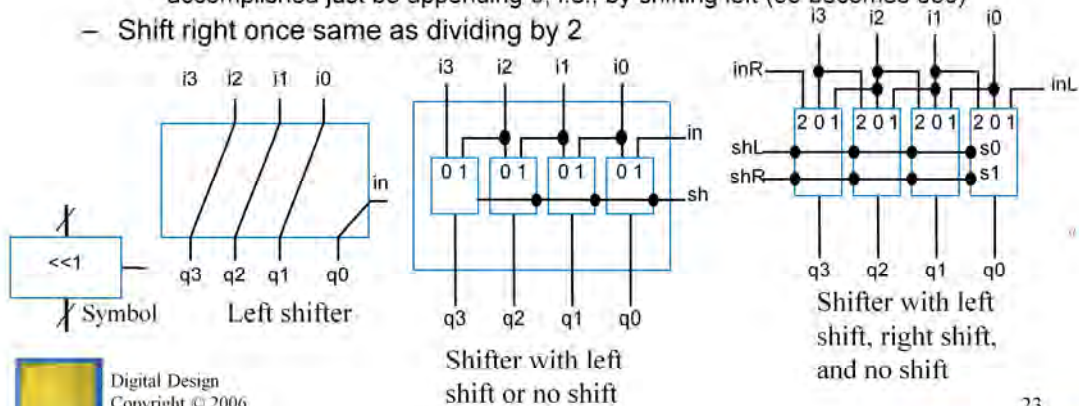


Shifter Example: Approximate Celsius to Fahrenheit Converter

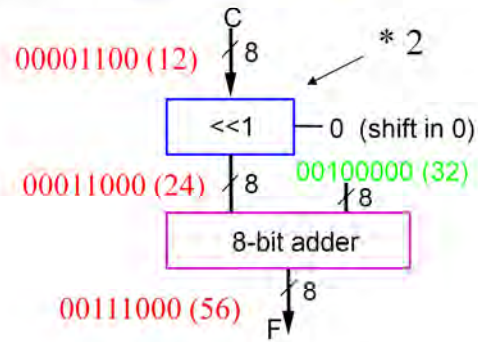- Convert 8-bit Celsius input to 8-bit Fahrenheit output
 - $F = C * 9/5 + 32$
 - Approximate: $F = C * 2 + 32$
 - Use left shift: $F = \text{left_shift}(C) + 32$




Shifter Example: Temperature Averager

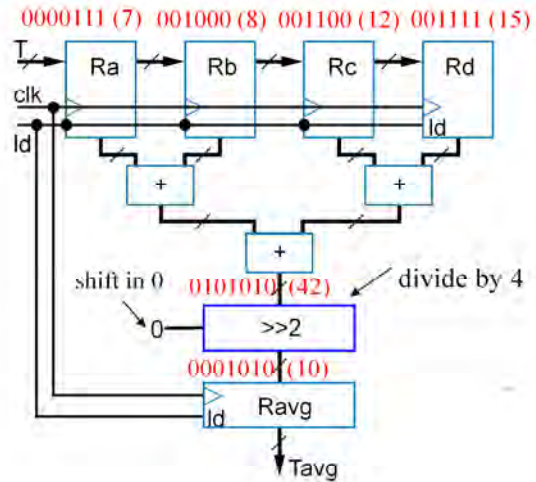- Four registers storing a history of temperatures
- Want to output the average of those temperatures
- Add, then divide by four
 - Same as shift right by 2
 - Use three adders, and right shift by two




Barrel Shifter

- A shifter that can shift by any amount
 - 4-bit barrel left shifter can shift left by 0, 1, 2, or 3 positions
 - 8-bit barrel left shifter can shift left by 0, 1, 2, 3, 4, 5, 6, or 7 positions
 - (Shifting an 8-bit number by 8 positions is pointless -- you just lose all the bits)
- Could design using 8x1 muxes and lots of wires
 - Too many wires
- More elegant design
 - Chain three shifters: 4, 2, and 1
 - Can achieve any shift of 0..7 by enabling the correct combination of those three shifters, i.e., shifts should sum to desired amount

 

Shift by 1 shifter uses 2x1 muxes. 8x1 mux solution for 8-bit barrel shifter: too many wires.



Q: xyz=??? to shift by 5?

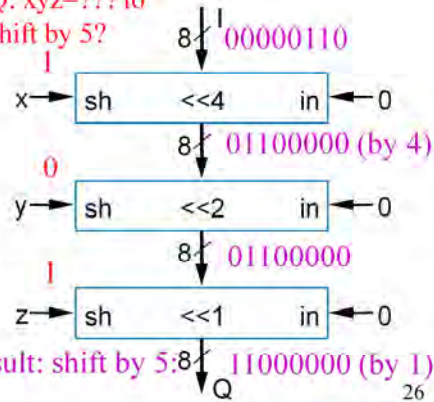

Digital Design
Copyright © 2006
Frank Vahid


Counters

  - ***N-bit up-counter***. N-bit register that can increment (add 1) to its own value on each clock cycle
 - 0000, 0001, 0010, 0011, ..., 1110, 1111, 0000
 - Note how count “rolls over” from 1111 to 0000
 - Terminal (last) count, tc, equals 1 during value just before rollover
- **Internal design**
 - Register, incrementer, and N-input AND gate to detect terminal count



Incrementer

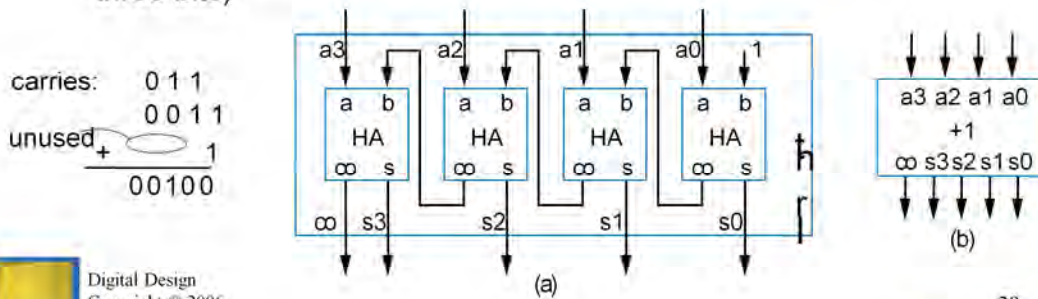- Counter design used incrementer
- Incrementer design
 - Could use carry-ripple adder with B input set to 00...001
 - But when adding 00...001 to another number, the leading 0's obviously don't need to be considered -- so just two bits being added per column
 - Use half-adders (adds two bits) rather than full-adders (adds three bits)



Incrementer



- Can build faster incrementer using combinational logic design process
 - Capture truth table
 - Derive equation for each output
 - $c_0 = a_3a_2a_1a_0$
 - ...
 - $s_0 = a_0'$
 - Results in small and fast circuit
 - Note: works for small N -- larger N leads to exponential growth, like for N-bit adder

Inputs				Outputs				
a3	a2	a1	a0	c0	s3	s2	s1	s0
0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	1	0
0	0	1	0	0	0	0	1	1
0	0	1	1	0	0	1	0	0
0	1	0	0	0	0	1	0	1
0	1	0	1	0	0	1	1	0
0	1	1	0	0	0	1	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	1	0
1	0	1	0	0	1	0	1	1
1	0	1	1	0	1	1	0	0
1	1	0	0	0	1	1	0	1
1	1	0	1	0	1	1	1	0
1	1	1	0	0	1	1	1	1
1	1	1	1	1	0	0	0	0




Counter Example: Mode in Above-Mirror Display

 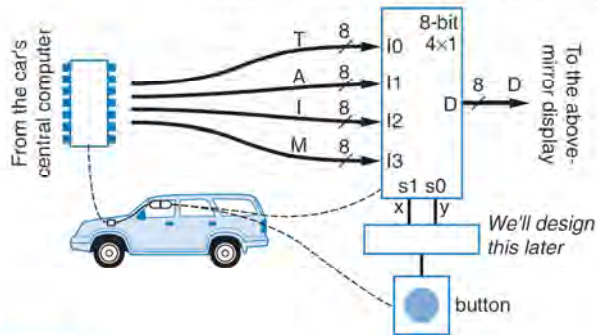- Recall above-mirror display example from Chapter 2
 - Assumed component that incremented xy input each time button pressed: 00, 01, 10, 11, 00, 01, 10, 11, 00, ...
 - Can use 2-bit up-counter
 - Assumes mode=1 for just one clock cycle during each button press
 - Recall "Button press synchronizer" example from Chapter 3




Counter Example: 1 Hz Pulse Generator Using 256 Hz Oscillator

 - Suppose have 256 Hz oscillator, but want 1 Hz pulse
 - 1 Hz is 1 pulse per second -- useful for keeping time
 - Design using 8-bit up-counter, use tc output as pulse
 - Counts from 0 to 255 (256 counts), so pulses tc every 256 cycles




Down-Counter

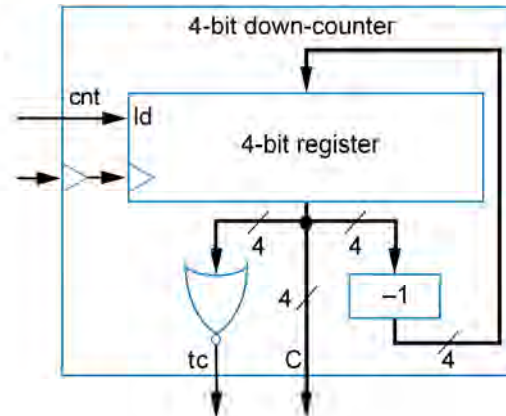- 4-bit down-counter
 - 1111, 1110, 1101, 1100, ..., 0011, 0010, 0001, 0000, 1111, ...
 - Terminal count is 0000
 - Use NOR gate to detect
 - Need decrements (-1) – design like designed incrementer




Up/Down-Counter

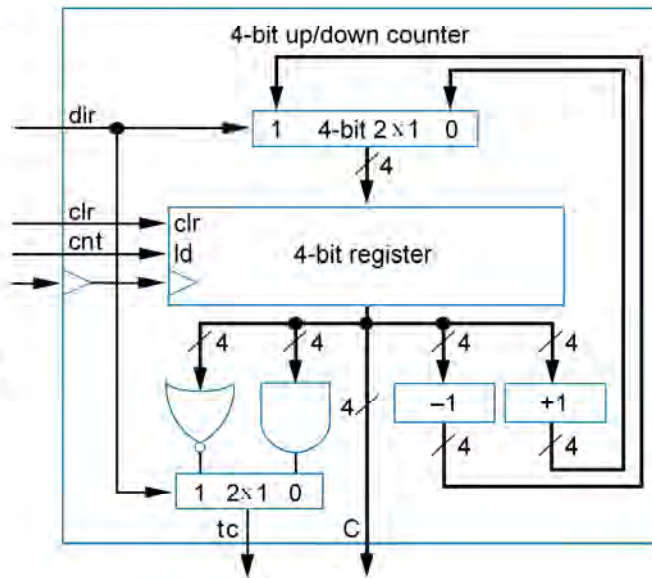- Can count either up or down
 - Includes both incrementer and decremter
 - Use dir input to select, using 2x1: dir=0 means up
 - Likewise, dir selects appropriate terminal count value




Counter Example: Light Sequencer

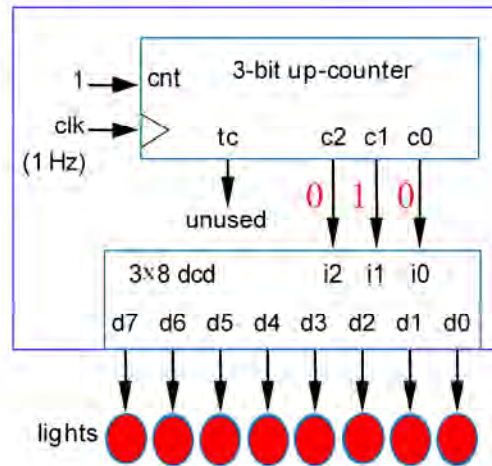- Illuminate 8 lights from right to left, one at a time, one per second
- Use 3-bit up-counter to counter from 0 to 7
- Use 3x8 decoder to illuminate appropriate light
- Note: Used **3-bit** counter with 3x8 decoder
 - NOT an 8-bit counter – why not?




Counter with Parallel Load

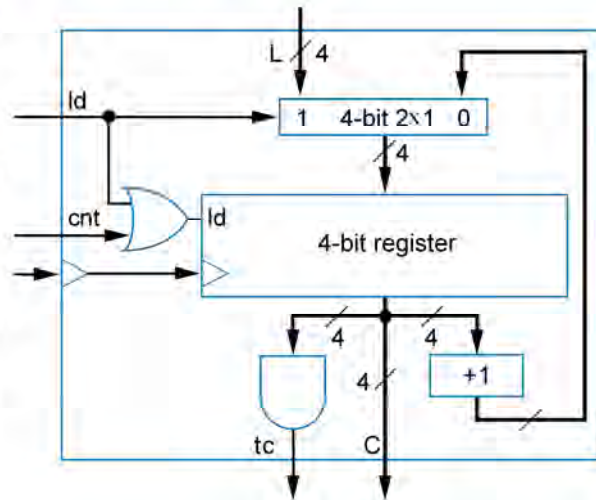- Up-counter that can be loaded with external value
 - Designed using 2x1 mux
 - ld input selects incremented value or external value
 - Load the internal register when loading external value or when counting




Counter with Parallel Load

- Useful to create pulses at specific multiples of clock
 - Not just at N-bit counter's natural wrap-around of 2^N
- Example: Pulse every 9 clock cycles
 - Use 4-bit down-counter with parallel load
 - Set parallel load input to 8 (1000)
 - Use terminal count to reload
 - When count reaches 0, next cycle loads 8.
 - Why load 8 and not 9? Because 0 is included in count sequence:
 - 8, 7, 6, 5, 4, 3, 2, 1, 0 → 9 counts

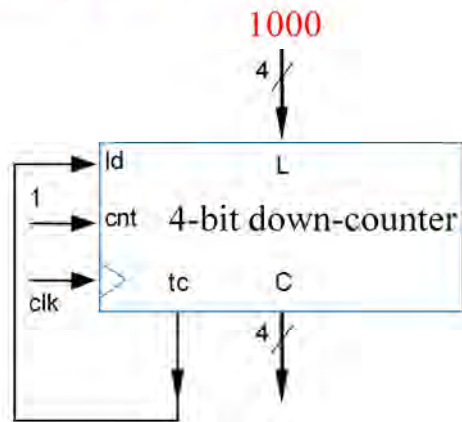

Counter Example: New Year's Eve Countdown Display

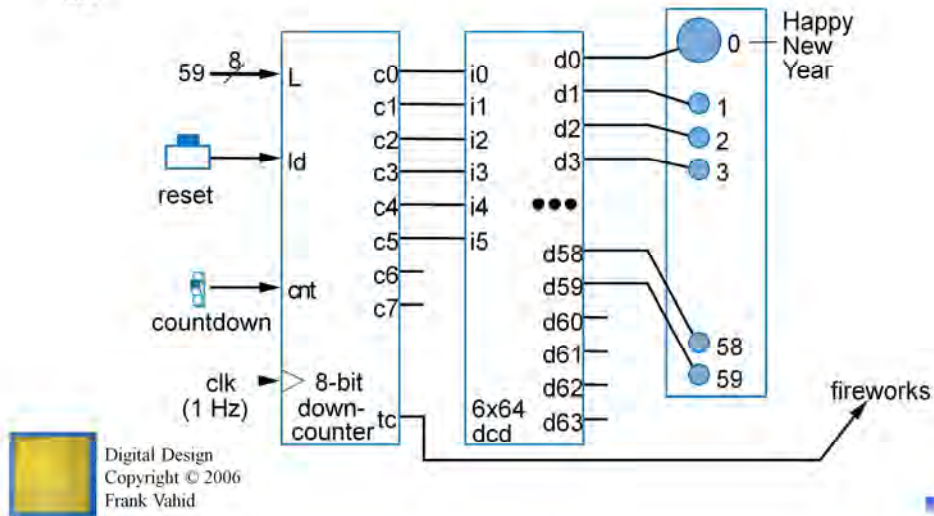
- Chapter 2 example previously used microprocessor to counter from 59 down to 0 in binary
- Can use 8-bit (or 7- or 6-bit) down-counter instead, initially loaded with 59



Digital Design
Copyright © 2006
Frank Vahid


Counter Example: 1 Hz Pulse Generator from 60 Hz Clock

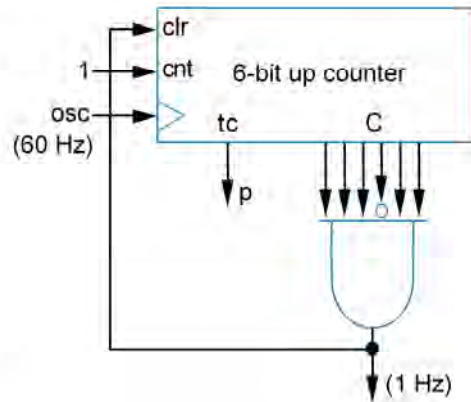- U.S. electricity standard uses 60 Hz signal
 - Device may convert that to 1 Hz signal to count seconds
- Use 6-bit up-counter
 - Can count from 0 to 63
 - Create simple logic to detect 59 (for 60 counts)
 - Use to clear the counter back to 0 (or to load 0)




Timer

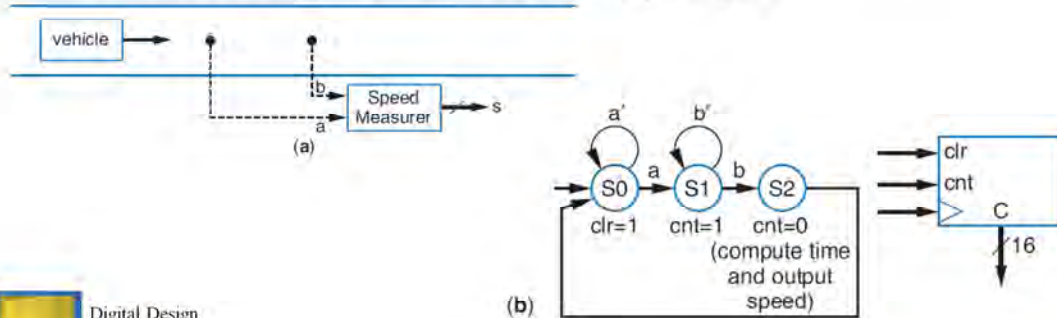- A type of counter used to measure time
 - If we know the counter's clock frequency and the count, we know the time that's been counted
- Example: Compute car's speed using two sensors
 - First sensor (a) clears and starts timer
 - Second sensor (b) stops timer
 - Assuming clock of 1kHz, timer output represents time to travel between sensors. Knowing the distance, we can compute speed




Register Files

 - ***MxN register file*** component provides efficient access to M N -bit-wide registers
 - If we have many registers but only need access one or two at a time, a register file is more efficient
 - Ex: Above-mirror display (earlier example), but this time having 16 32-bit registers
 - Too many wires, and big mux is too slow



Register File

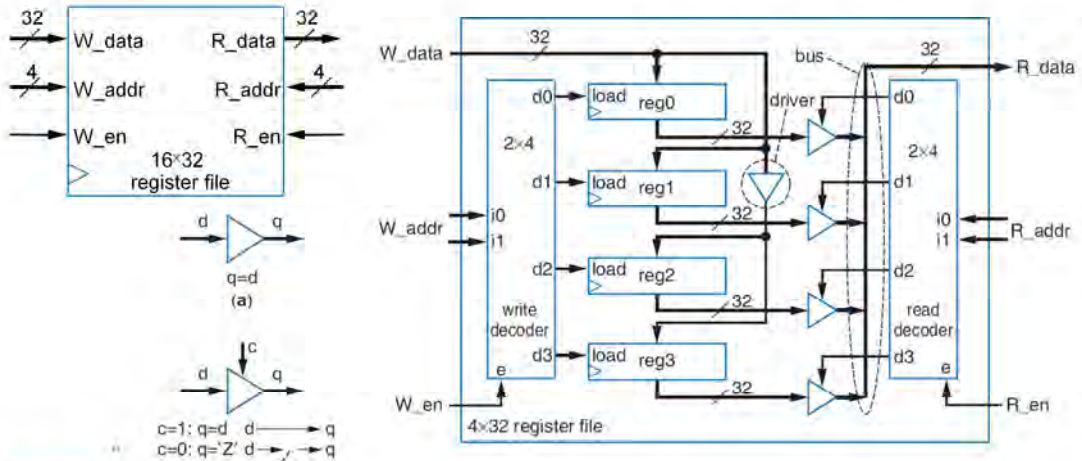
- Instead, want component that has one data input and one data output, and allows us to specify which internal register to write and which to read



Digital Design
Copyright © 2006
Frank Vahid

Register File Timing Diagram

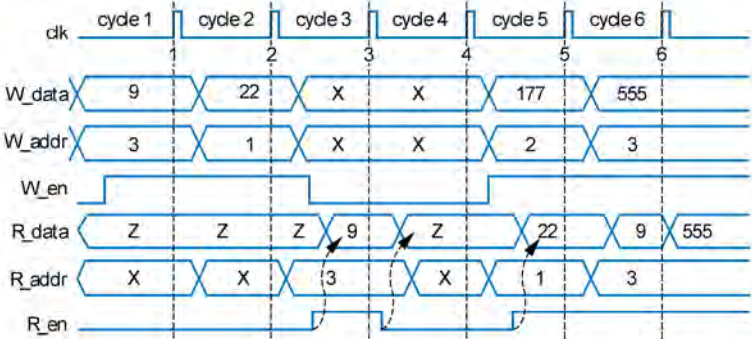- Can write one register and read one register each clock cycle
 - May be same register



0: ?	0: ?	0: ?	0: ?	0: ?	0: ?	0: ?
1: ?	1: ?	1: 22	1: 22	1: 22	1: 22	1: 22
2: ?	2: ?	2: ?	2: ?	2: ?	2: 177	2: 177
3: ?	3: 9	3: 9	3: 9	3: 9	3: 9	3: 555

Register-File Example: Above-Mirror Display

- 16 32-bit registers that can be written by car's computer, and displayed
 - Use 16x32 register file
 - Simple, elegant design
- Register file hides complexity internally
 - And because only one register needs to be written and/or read at a time, internal design is simple

