

10/06/2009 Outline


- Exam #1 - 9 - 10:15 AM Oct 9th Woodward 125
- No class on Oct 12/13 - Fall Break
- Hw 6 due 10/15/2009
- Grades

-
- Mux to build "function lookup"
 - De mux
 - Hardware Description Languages
 - VHDL
 - Verilog
 - System C

A	B	f
0	0	0
0	1	0
1	0	0
1	1	1


$$f = AB$$

(AND)

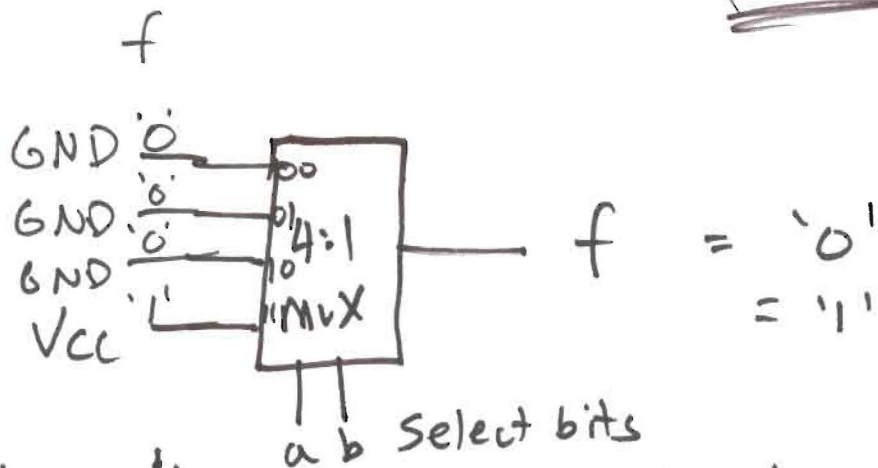


$GND = '0'$
 $Vcc = '1'$

4 input / 1 output
MUX

 

Lookup Table



A	B	f
0	0	0
0	1	1
1	0	1
1	1	1

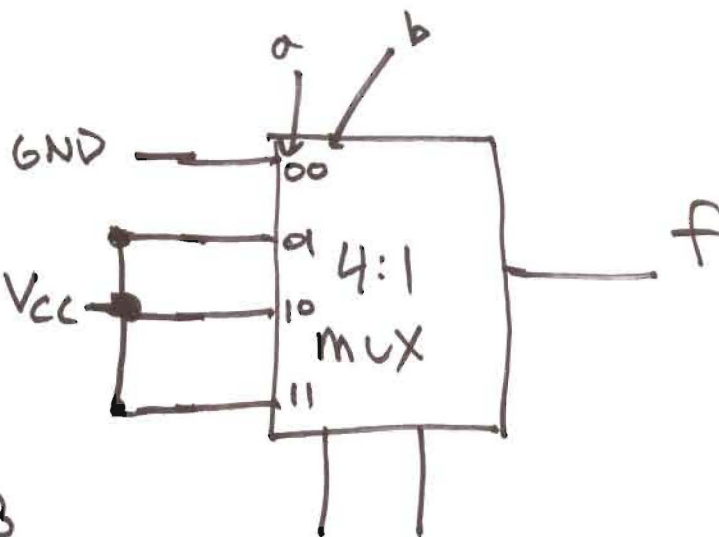

$$f = \bar{A}B + A\bar{B} + AB$$

Inverters

a b
 0 0 - input 0
 0 1 - input 1

 
 


2 inputs
 $\log_2(2) = 1$ select bit

$A=0$
 $f=B$
 $A=1$
 $f=1(A)$

16:1 mux
 $\log_2(16) = 4$
 $2^4 = 16$


A ~~AND~~ Gate from a 2:1 mux

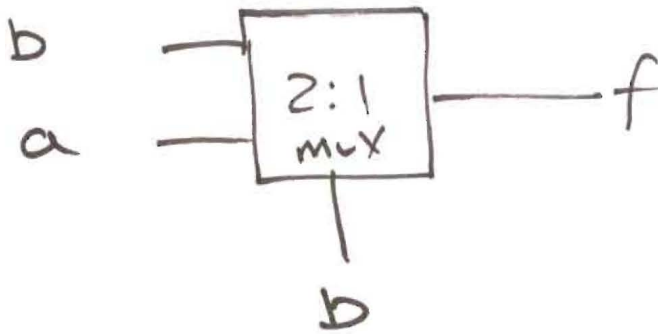 


a	b	f
0	0	0
0	1	0
1	0	0
1	1	1

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


could do it this way...

 


more compact

 



A	B	A AND B
0	0	0
0	1	0
1	0	0
1	1	1

 

 GND = '0'
 VCC = '1'
 "Common Collector Voltage"






A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

  

XNOR

A	B	f
0	0	1
0	1	0
1	0	0
1	1	1

  

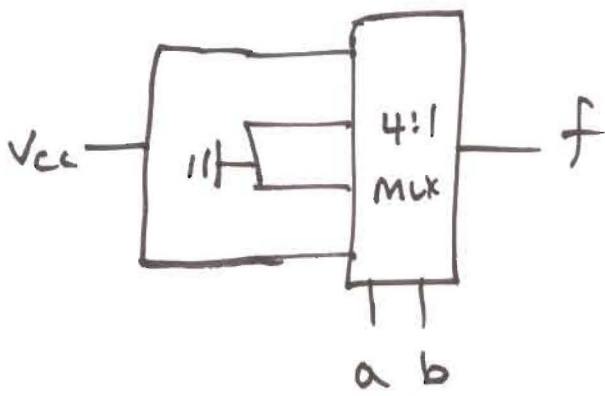

a	b	f
0	0	Vcc = 1
0	1	0
1	0	0
1	1	1

XNOR?




a	b	f
0	0	1
0	1	0
1	0	0
1	1	1

XOR

0	1	0
1	0	0

a	b	f
0	0	Vcc = 1
0	1	0
1	0	0
1	1	1

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

   

Demux

