
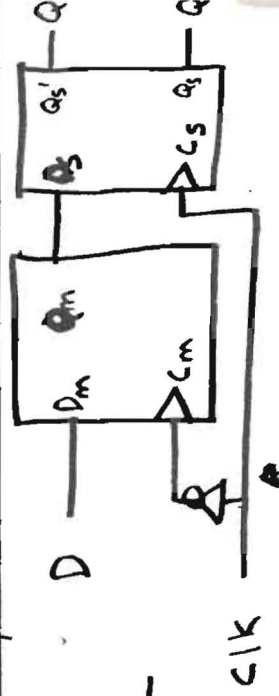


POSITIVE

D Flip Flop with Rising Edge Clock

Example

11/12/09

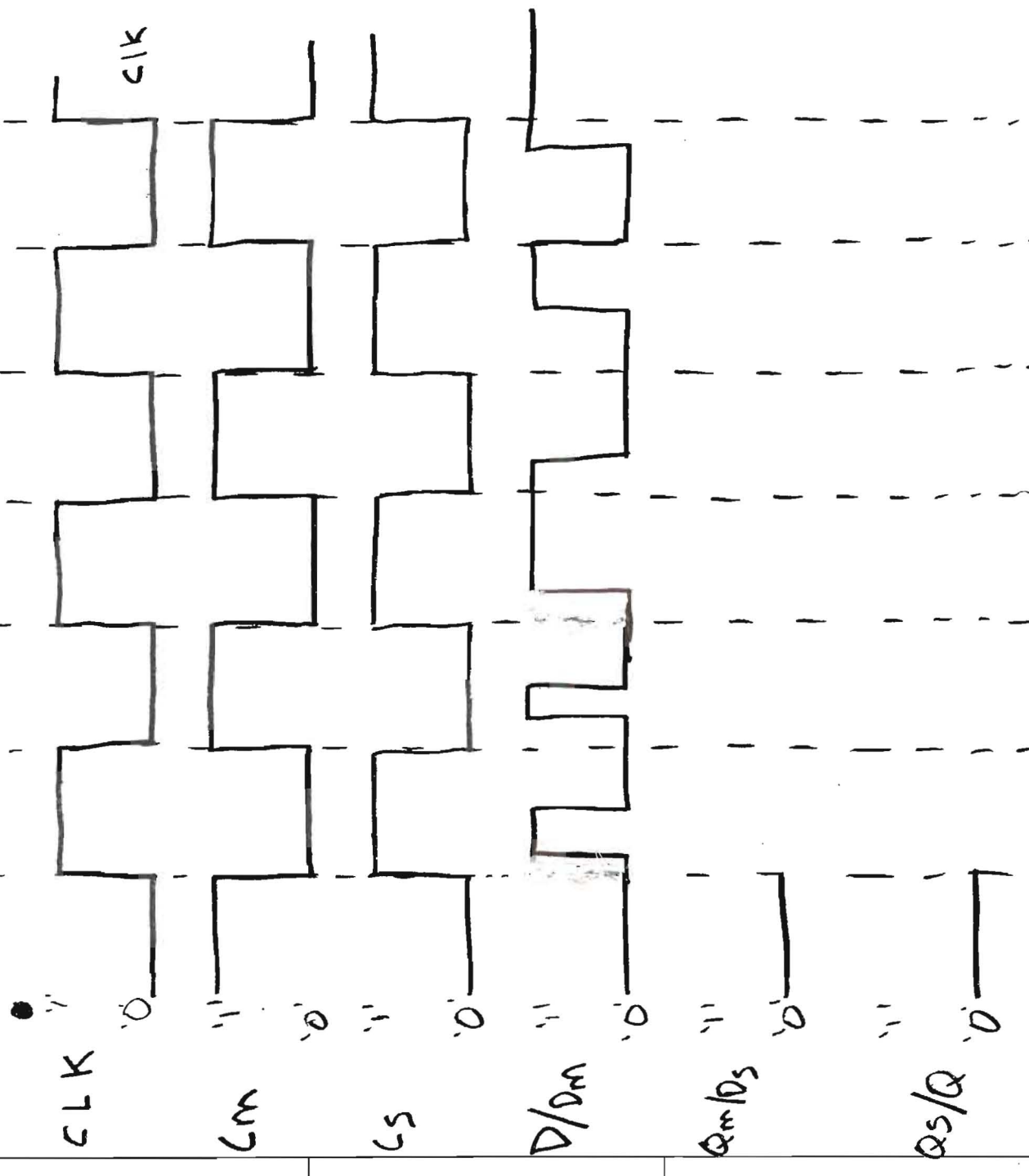

C_m is inverse of CLK

C_s is same as CLK

D Flip Flop w Falling Edge Clock Example

11/12/09

