

Digital Design -

ECGR 2181 Quiz 9

2015-11-03

Name: _____

Student ID: _____

Section: _____

(1 point for clearly printed name)


①

- What is the TIME and DATE of Exam 2? (1 point)

- What is the difference between a Flip Flop and a Latch? (3 points)

 Example of another problem
Falling Edge

- Given the following Clock (CLK) and Data Input (D) draw the D Flip-Flop (Rising Edge) waveform output (Q) (5 points)
, Q starts at 0



~~Digital Design~~ 2015-11-03

Question:

Consider the design on page 23
of the notes. How many NOT gates,
AND gates, and NOR gates are in
the design?

3 registers (Shift)

each register has 5 D flip-flops

each D flip flop has a NOT gate and
2 D latches

each D latch has one NOT gate,
2 AND gates, and 2 NOR gates

$$\text{NOR} = \text{gates} \times \text{latches} \times \text{flip flops} \times \text{registers}$$
$$2 * 2 * 5 * 3 = 60$$

$$\text{AND} = 2 * 2 * 5 * 3 = 60$$

$$\text{NOT} = ((1 * 2) + 1) * 5 + 3 = 45$$

Digital Design

2015-11-03

Combinational \rightarrow Vahid slide 33 ③

Call	Cancel	Q	D
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	1	1

Call	Q	00	01	11	10
Call	0	0	1	0	0
Call	1	1	1	1	1

Call + $\overline{\text{cancel}}$ Q

