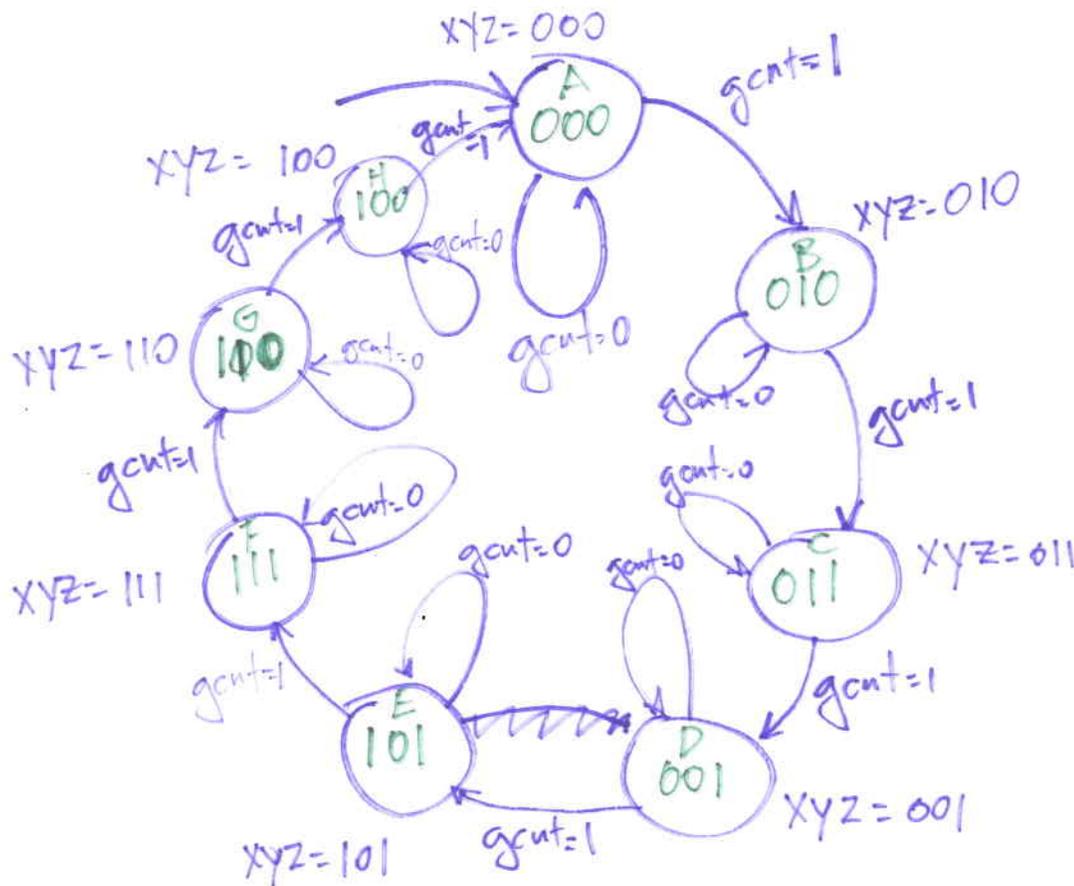


UNCC – ECGR2181- Pop Quiz – December 08, 2015

①

Name: Solution Mosaic User ID Solution  
 Name: \_\_\_\_\_ Mosaic User ID \_\_\_\_\_

1. Draw a state diagram for an FSM with an input gcnt and three outputs x, y, and z. The xyz outputs generate a Gray Code in which exactly one of the three outputs changes from 0 to 1 or from 1 to 0. The Gray Code sequence that the FSM should output is 000, 010, 011, 001, 101, 111, 110, 100, repeat. The output should change only on a rising clock edge and when the input gcnt = 1. Make the initial state 000.



Note: You do not need to give the state a value (i.e. 000) for this quiz.

- Points:
- 1 ~~initial~~ initial state
  - 4 correct transitions on  $gcnt=1$
  - 2 correct transitions on  $gcnt=0$
  - ~~1~~ 2 state names (i.e. '000' or A)
  - 2 outputs XYZ

2

2. Using the process for designing a controller, convert the FSM you created in previous problem to a controller, implementing the controller using a state register and logic gates.

S2	S1	S0	gout	N2	N1	N0	X	Y	Z
0	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0
0	0	1	0	0	0	1	0	0	1
0	0	1	1	1	0	1	0	0	1
0	1	0	0	0	1	0	0	1	0
0	1	0	1	0	1	1	0	1	0
0	1	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	1	1
1	0	0	0	1	0	0	1	0	0
1	0	0	1	0	0	0	1	0	0
1	0	1	0	1	0	1	1	0	1
1	0	1	1	1	1	1	1	0	1
1	1	0	0	1	1	0	1	1	0
1	1	0	1	1	0	0	1	1	0
1	1	1	0	1	1	1	1	1	1
1	1	1	1	1	1	0	1	1	1

Step A  
Truth  
Table

ECGR2181

2015-12-08

3

Step B  
K maps

N2

		S0gcut			
		00	01	11	10
S2S1	00	0	0	1	0
	01	0	0	0	0
	11	1	1	1	1
	10	1	0	1	1

$$N2 = S2S1 + S1'S0gcut + \cancel{S2S1'S0gcut}$$

N1

		S0gcut			
		00	01	11	10
S2S1	00	0	1	0	0
	01	1	1	0	1
	11	1	0	1	1
	10	0	0	1	0

$$N1 = S1gcut' + S2'S0'gcut + S2S0gcut$$

N0

		S0gcut			
		00	01	10	11
S2S1	00	0	0	1	1
	01	0	1	1	1
	11	0	0	0	1
	10	0	0	1	1

$$N0 = S0gcut + S1'S0 + S2'S1gcut'$$

DCGR2181

2015-12-08

4

stop  
Circuit

gent

S2 → X

S1 → Y

S0 → Z

