

Digital Design

Chapter 9: Hardware Description Languages



Slides to accompany the textbook *Digital Design, with RTL Design, VHDL, and Verilog*, 2nd Edition,
by Frank Vahid, John Wiley and Sons Publishers, 2010.
<http://www.ddvahid.com>

Copyright © 2010 Frank Vahid

*Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites.. PowerPoint source (or pdf with animations) may **not** be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.ddvahid.com> for information.*


Introduction

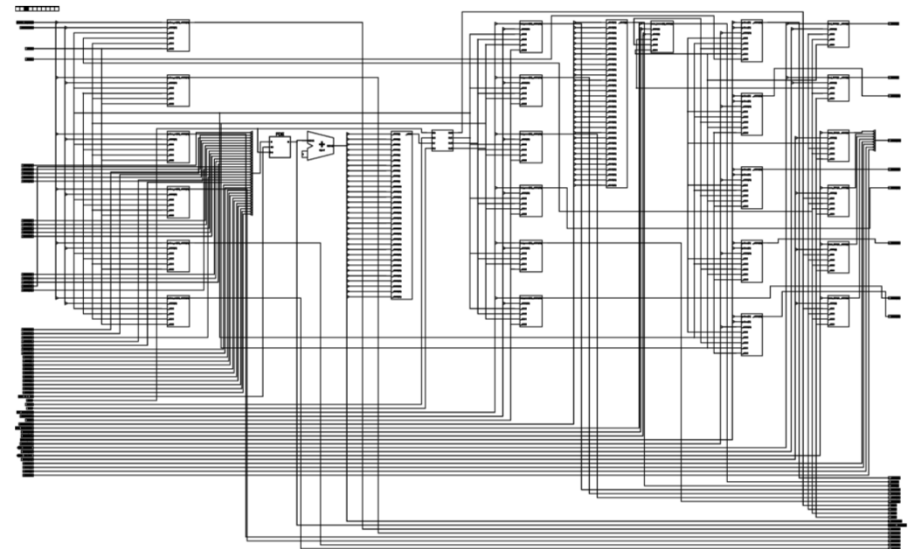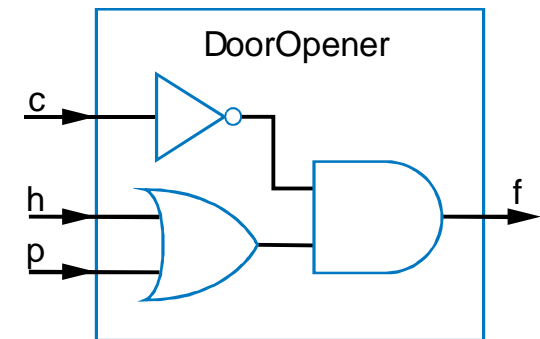- A drawing of a circuit, or *schematic*, contains graphical information about a design
 - Inverter is above the OR gate, AND gate is to the right, etc.
- Such graphical information may not be useful for large designs
- Can use textual language instead



Textual Language – English

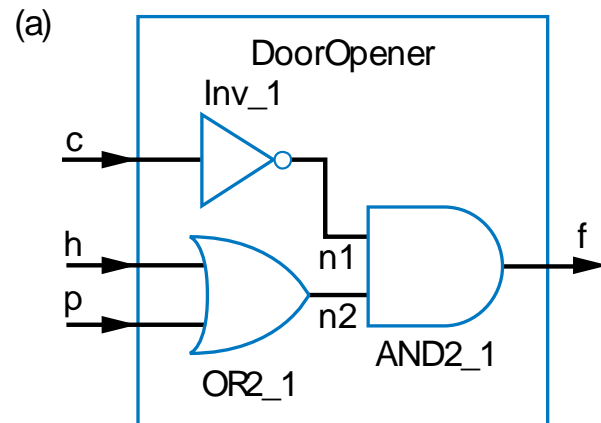- Can describe circuit using English text rather than using a drawing
 - Of course, English isn't a good language for a computer to read
 - Need a more precise, computer-oriented language



- (b)
- We'll now describe a circuit whose name is DoorOpener.
The external inputs are c, h and p, which are bits.
The external output is f, which is a bit.

We assume you know the behavior of these components:

An inverter, which has a bit input x, and bit output F.

A 2-input OR gate, which has inputs x and y, and bit output F.

A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:

An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.

A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.

A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.

That's all.



Computer-Readable Textual Language for Describing Hardware Circuits: HDLs

- Hardware description language (HDL)
 - Intended to describe circuits textually, for a computer to read
 - Evolved starting in the 1970s and 1980s
- Popular languages today include:
 - VHDL –Defined in 1980s by U.S. military; Ada-like language
 - Verilog –Defined in 1980s by a company; C-like language
 - SystemC –Defined in 2000s by several companies; consists of libraries in C++




Combinational Logic Description using Hardware Description Languages ^{9.2}

Description Languages

- **Structure**

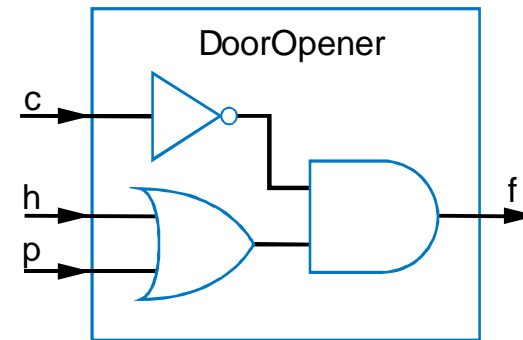- Another word for "circuit"
- An interconnection of components
- Key use of HDLs is to describe structure




Note: The term "instantiate" will be used to indicate adding a new copy of a component to a circuit

The OR component




Three instances of the OR component

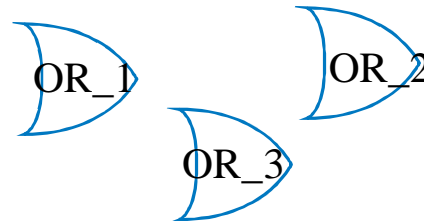

Describing Structure in VHDL

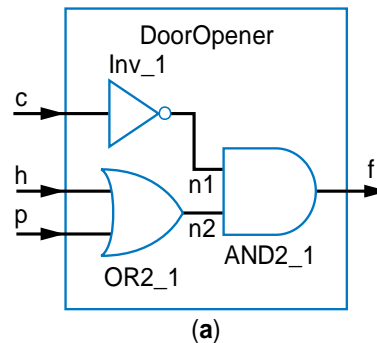- Entity – Defines new item's name & ports (inputs/outputs)
 - std_logic means bit type, defined in ieee library
- Architecture – Describes internals, which we named "Circuit"
 - Declares 3 previously-defined components
 - Declares internal signals
 - Note "--" comment
 - Instantiates and connects those components



(a)

We'll now describe a circuit whose name is DoorOpener.
The external inputs are c, h and p, which are bits.
The external output is f, which is a bit.

We assume you know the behavior of these components:
An inverter, which has a bit input x, and bit output F.
A 2-input OR gate, which has inputs x and y, and bit output F.
A 2-input AND gate, which has bit inputs x and y, and bit output F.

The circuit has internal wires n1 and n2, both bits.

The DoorOpener circuit internally consists of:
An inverter named Inv_1, whose input x connects to external input c, and whose output connects to n1.
A 2-input OR gate named OR2_1, whose inputs connect to external inputs h and p, and whose output connects to n2.
A 2-input AND gate named AND2_1, whose inputs connect to n1 and n2, and whose output connects to external output f.

That's all.

(b)

```

library ieee;
use ieee.std_logic_1164.all;
entity DoorOpener is
    port ( c, h, p: in std_logic;
          f: out std_logic );
end DoorOpener;

architecture Circuit of DoorOpener is
    component Inv
        port ( x: in std_logic;
              F: out std_logic );
    end component;
    component OR2
        port ( x, y: in std_logic;
              F: out std_logic );
    end component;
    component AND2
        port ( x, y: in std_logic;
              F: out std_logic );
    end component;
    signal n1, n2: std_logic; -- internal wires
begin
    Inv_1: Inv port map ( x=>c, F=>n1);
    OR2_1: OR2 port map ( x=>h, y=>p, F=>n2);
    AND2_1: AND2 port map ( x=>n1, y=>n2, F=>f);
end Circuit;
    
```

(c)



Combinational Behavior

- **Combinational behavior**

- Description of desired behavior of combinational circuit without creating circuit itself
- e.g., $F = c' * (h + p)$ can be described as equation rather than circuit
- HDLs support description of combinational behavior



Describing Combinational Behavior in VHDL

- Describing an OR gate's behavior
 - Entity defines input/output ports
 - Architecture
 - Process – Describes behavior
 - Process "sensitive" to x and y
 - » Means behavior only executes when x changes or y changes
 - Behavior assigns a new value to output port F, computed using built-in operator "or"

```
library ieee;
use ieee.std_logic_1164.all;

entity OR2 is
  port (x, y: in std_logic;
        F: out std_logic
        );
end OR2;

architecture behavior of OR2 is
begin
  process (x, y)
  begin
    F <= x or y;
  end process;
end behavior;
```



Describing Combinational Behavior in VHDL

- Describing a custom function's behavior
 - Desired function: $f = c'(h+p)$
 - Entity defines input/output ports (not shown)
 - Architecture
 - Process
 - Sensitive to c, h, and p
 - Assigns a new value to output port f, computed using built-in operators "not", "and", and "or"


```
architecture beh of DoorOpener is
begin
  process(c, h, p)
  begin
    f <= not(c) and (h or p);
  end process;
end beh;
```



Testbenches


- **Testbench**

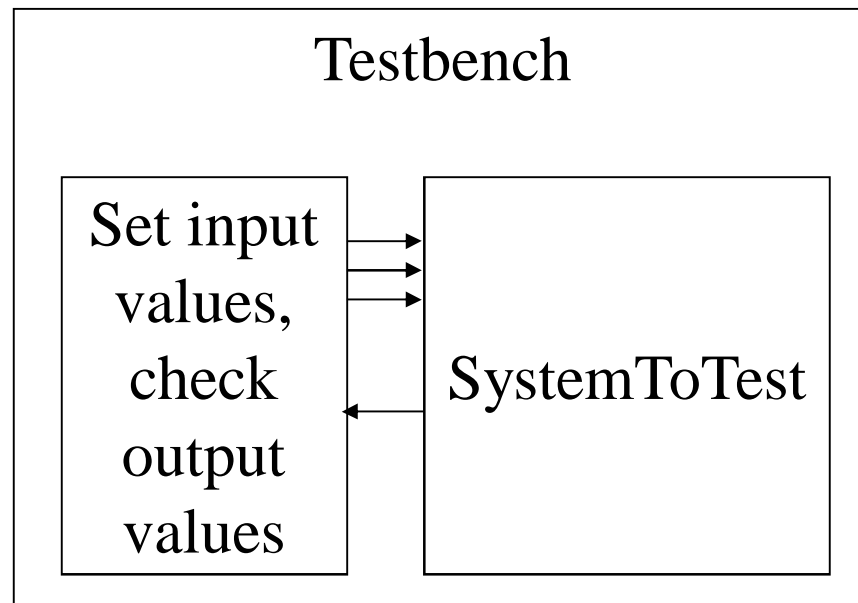- Assigns values to a system's inputs, check that system outputs correct values
- A key use of HDLs is to simulate system to ensure design is correct



Testbench in VHDL

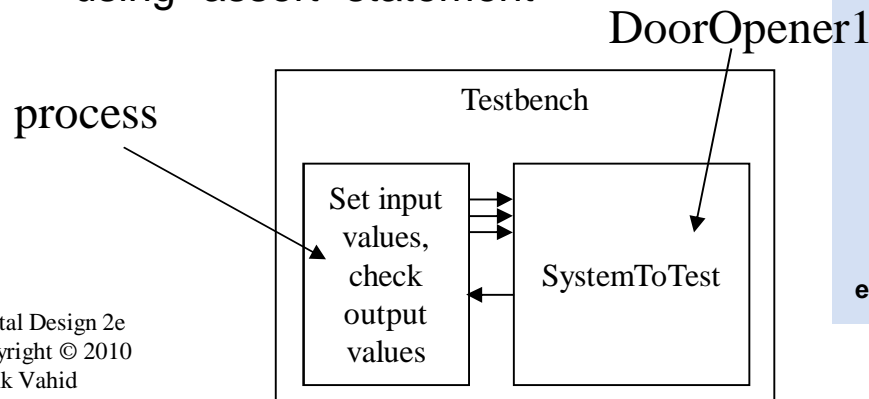- Entity
 - No inputs or outputs
- Architecture
 - Declares component to test, declares signals
 - Instantiates component, connects to signals
 - Process writes input signals, checks output signal
 - Waits a small amount of time after writing input signals
 - Checks for correct output value using "assert" statement



```
library ieee;
use ieee.std_logic_1164.all;

entity Testbench is
end Testbench;

architecture behavior of Testbench is
    component DoorOpener
        port ( c, h, p: in std_logic;
              f: out std_logic
            );
    end component;
    signal c, h, p, f: std_logic;
begin
    DoorOpener1: DoorOpener port map (c, h, p, f);

    process
    begin
        -- case 0
        c <= '0'; h <= '0'; p <= '0';
        wait for 1 ns;
        assert (f='0') report "Case 0 failed";

        -- case 1
        c <= '0'; h <= '0'; p <= '1';
        wait for 1 ns;
        assert (f='1') report "Case 1 failed";
        -- (cases 2-6 omitted from figure)
        -- case 7
        c <= '1'; h <= '1'; p <= '1';
        wait for 1 ns;
        assert (f='0') report "Case 7 failed";

        wait; -- process does not wake up again
    end process;
end behavior;
```

