## **Architecture Research and IC Design for Embedded Ultra – Micro Processor**

-by Rohith Tenneti Seetha Sai



#### Introduction


#### Embedded System Design

- Simplex parallel combinational Circuit
  - ✓ High Speed, small circuit area and high performance Advantage
  - ✓ Complex design needs, debugging Disadvantage

- Use a general processor
  - ✓ Design based on processor is fast and easy to debug Advantage
  - ✓ Area, less cost performance Disadvantage

- Simplification without RAM or ROM access
  - ✓ Immediate and Register addressing modes are considered no access of memory in the Instruction set architecture level
- Registers are mapped as in / out ports
- 16 bit instruction encoding, sixteen 8 bit registers
- three instruction types: double-operand instruction, single-operand instruction and branch instruction.

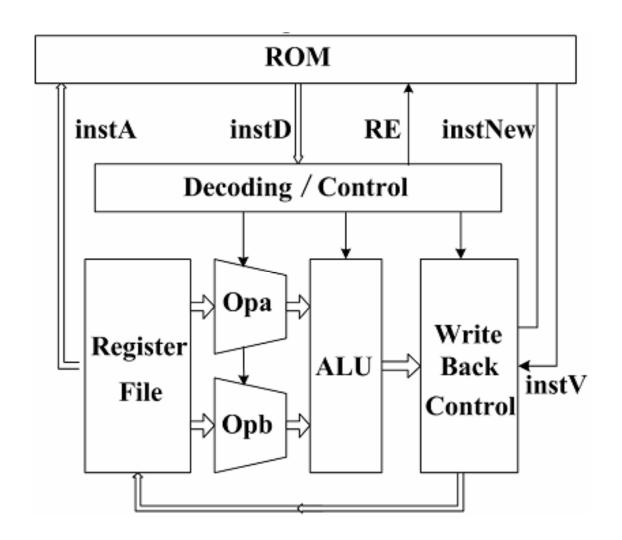
## IC Design of UMP – General Architecture




## **Instruction formats**

Format	instD[15:0]															
	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
	MO V/ADD/S UB/C MP/AND/O R/XO R Ra,Rb															
1a	inselimm	infunc		insela				inselb				xxxx				
	(0)	(000-110)			(0000-1111)				(0000-1111)							
	MO V/ADD/S UB/C MP/AND/O R/XO R Ra,#im m															
1 b	inselimm	infunc			insela				inimm							
	(1)	(00	00-11	0)	(0000-1111)				(00H-FFH)							
	NOT/SHR/SHL Ra    GEIC/SEIC Ra,n															
2	inselimm	infunc			insela				x	inmon	f	х	inoptn		n	
	(0)		(111)		(	0000	-1111	)	^	(0	00-10	)0)	^	(000-111)		
	JMP/JC/J	NC/J	Z/JN	Z #iı	nm											
3	inselimm	i	infunc		v	injpcf			inimm							
	(1)		(111)		Х	(0	00-10	0)		(00H-FFH)						


# **Operand Fetch Logic**

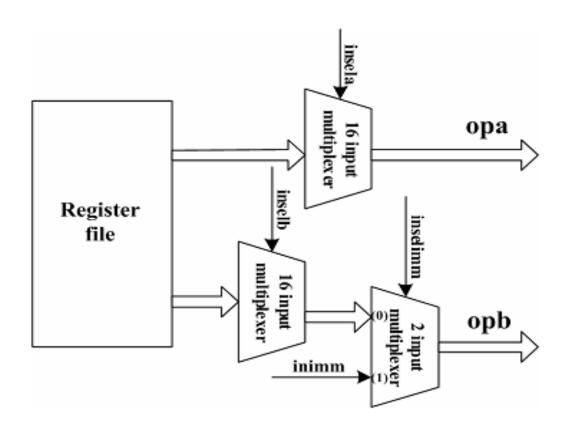


## **Instruction Decoding**

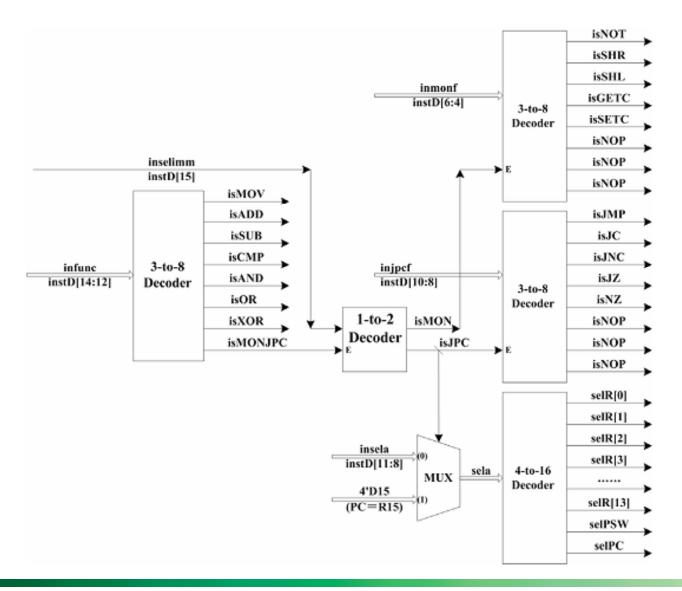

## **Enable Logic**

 

### Write back

 

### **Shoot Questions**

